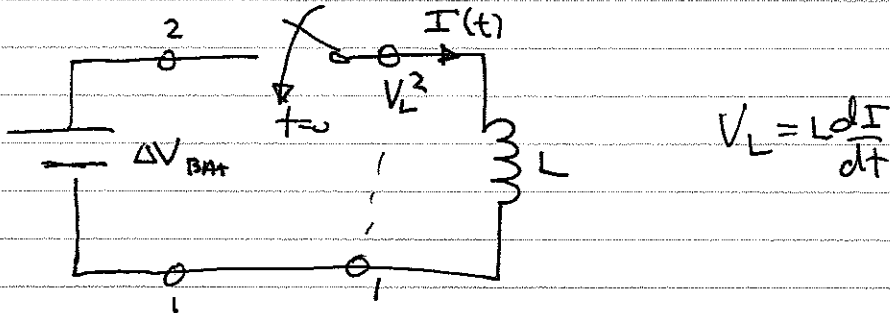


# Inductors in Circuits

34.28

What happens when I connect an inductor to a voltage source




Before switch is closed  $I(t) = 0$ . Once switch is closed  $V_L = \Delta V_{BAT}$  Potential difference between is same for inductor and battery

$$\Delta V_{BAT} = L \frac{dI}{dt}$$

$$I(t) = I(0) + \left( \frac{\Delta V_{BAT}}{L} \right) t$$

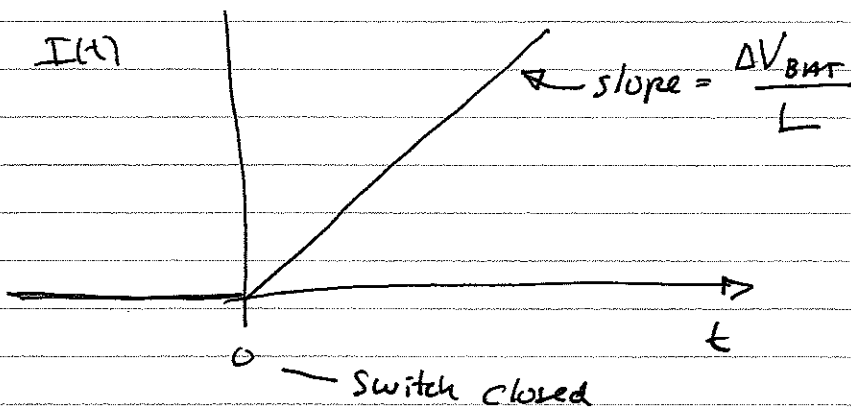initial current  
in this case  $I(0) = 0$




Can I open switch?

ANS NO!
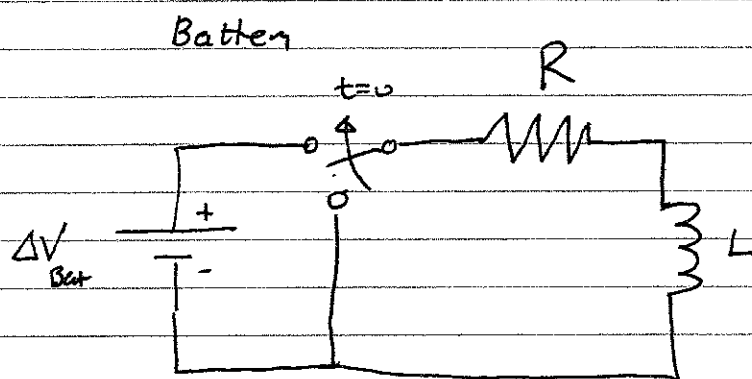
## An L-R circuit

Consider the series connection of  
a resistor and an inductor with a




At  $t=0$  the  
switch is  
closed.

Assume that just  
before the switch  
is closed


Why? All inductors have some resistance,  
battery too.

When switch is closed

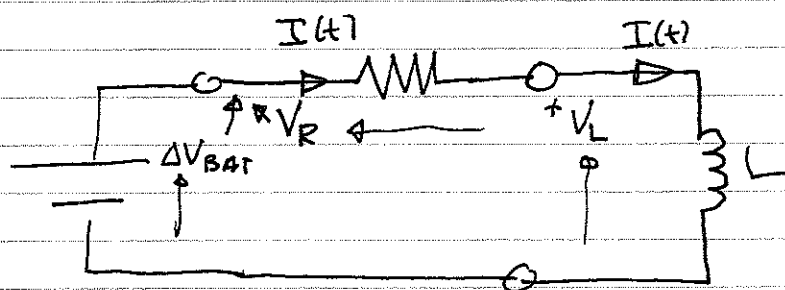

Same current entering  $R$  must also enter  $L$ . Continuity of charge.

What about Voltage

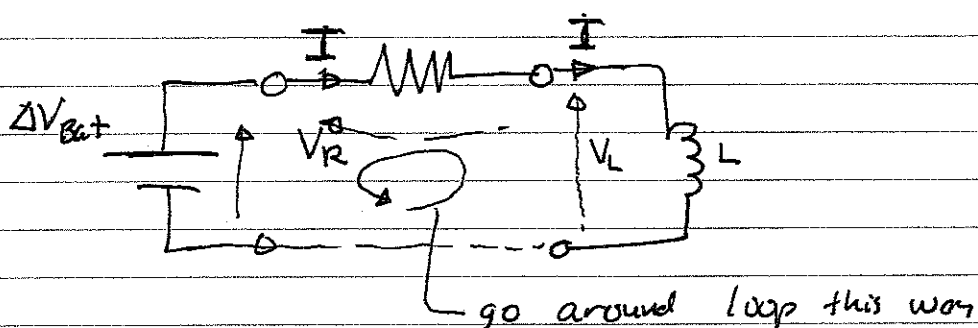

Arrows indicate direction in which voltage is defined for a 2-terminal device.

Kirchoff's Voltage Law: Sum of voltage around a closed loop is ZERO. (Sound familiar?)

opposite arrows

$$V_L + V_R - \Delta V_{BAT} = 0$$

$$L \frac{dI}{dt} + IR - \Delta V_{BAT} = 0$$

differential equation determines

$I(t)$

initial condition  $I(0) = 0$

This is a linear differential  
equation with constant coefficients

Linear: Only first power of unknown  
and its derivatives appear (no  $I^2, I^3$ , etc.)

Constant coefficients: L and R are not  
functions of time.

Solution:

Generally one can find a general  
solution by adding together ~~what~~ a  
"particular" solution and a homogeneous  
solution.

$$I(t) = I_p(t) + I_h(t)$$

The particular solution is any solution that  
satisfies

BC

$$L \frac{dI_p}{dt} + I_p R = \Delta V_{BAT}$$

The homogeneous solution satisfies

$$L \frac{dI_h}{dt} + I_h R = 0$$

You can verify that  $I(t) = I_p(t) + I_h(t)$  satisfies the original equation.

Since  $I_p(t)$  can be any solution let's pick a simple one

$$I_p = \frac{\Delta V_{\text{bat}}}{R} = \text{const}$$

note: in this case  $dI_p/dt = 0$  and particular equation is satisfied.

Now consider homogeneous equation

$$L \frac{dI_h}{dt} + R I_h = 0$$

This is satisfied by the decaying exponential

$$I_h(t) = A e^{-Rt/L}$$

where  $A$  is a constant. ~~So add~~

~~$$I(t) = \frac{\Delta V_{\text{bat}}}{R}$$~~

So, adding particular & homogeneous

$$I(t) = I_p(t) + I_h(t) = \frac{\Delta V_{\text{bat}}}{R} + A e^{-t/\tau}$$

Now, we pick  $A$  to satisfy the initial condition


$$I(0) = 0 \quad I(0) = \frac{\Delta V_{\text{bat}}}{R} + A$$

Therefore  $A = -\frac{\Delta V_{\text{bat}}}{R}$

Solution:

$$I(t) = \frac{\Delta V_{\text{bat}}}{R} (1 - e^{-t/\tau})$$

where  $\tau = (L/R)$

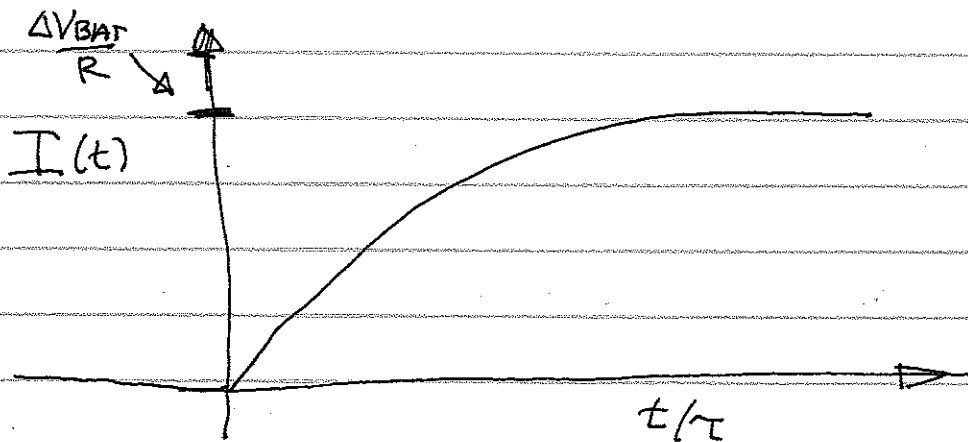

EXAMPLE:  $\Delta V_{\text{bat}} = 1.5 \text{ V}$

$$R = 100 \Omega$$

$$L = 0.1 \text{ henries}$$

$$\tau = L/R = 0.1/100 = .001 \text{ sec} = 1 \text{ msec}$$

$$\Delta V_{\text{bat}}/R = 1.5/100 = .015 \text{ A} = 15 \text{ mA}$$

~~What is  $\tau$ ?~~

$$I(t) = \frac{\Delta V_{\text{Bat}}}{R} (1 - e^{-t/\tau})$$

Voltage across resistor


$$V_R = IR = \Delta V_{\text{Bat}} (1 - e^{-t/\tau})$$

Voltage across inductor

$$V_L = L \frac{dI}{dt} = \frac{L \Delta V_{\text{Bat}}}{R} \frac{d}{dt} (1 - e^{-t/\tau})$$


$$= \frac{L \Delta V_{\text{Bat}}}{R} (-1) \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$
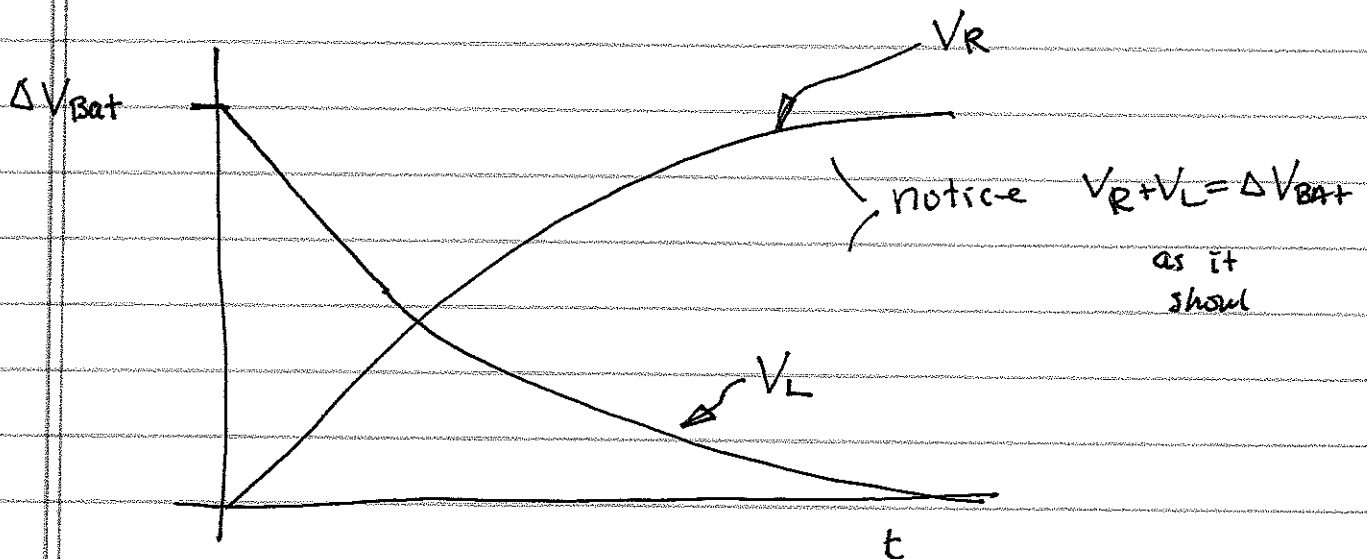
$$= \frac{L}{R\tau} \Delta V_{\text{Bat}} e^{-t/\tau} = \Delta V_{\text{Bat}} e^{-t/\tau}$$





What is going on?

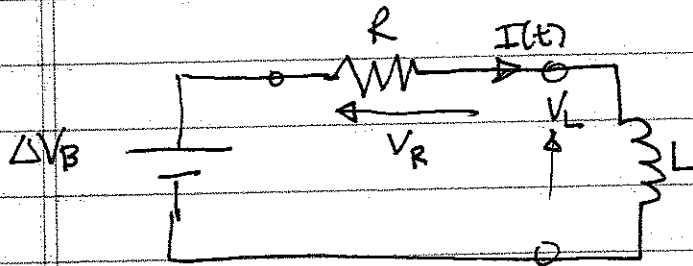

Initially  $I$  is small

( $I$  can't change rapidly  
in an inductor)

$I$  is small, so  $V_R = IR$   
is small.

All the voltage  $\Delta V_{\text{bat}}$  is applied to  
the inductor

$$V_L \approx \Delta V_{\text{bat}}$$

$I(t)$  then begins to increase linearly in  
time. As  $I(t)$  rises so does  $V_R = IR$

This means  $V_L$  must drop. Since  $V_L$   
drops rate of change of current

$$\frac{dI}{dt} = \frac{1}{L} V_L$$


must drop.

$V_L$  drops to zero in several  $\tau = L/R$   
times. Once  $V_L$  is nearly zero.

$I(t)$  stops changing.

In steady state  $I(\infty) = \frac{\Delta V_{\text{bat}}}{R}$

## 34.9 The LC-circuit

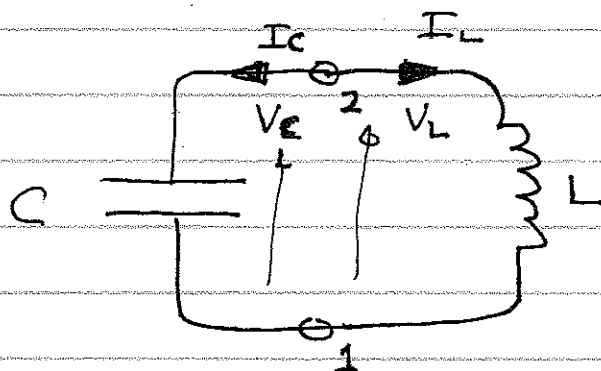

If we label the two terminals the same  
 so that there is a common VOLTAGE

$$V_L = V_C = V(t)$$

Then we must draw the current  
 arrows on the inductor and capacitor  
 pointing in opposite directions

Kirchoff's current law tells us

$$I_C + I_L = 0$$

OR 
$$I_C = -I_L$$

so:

$$V(t) = L \frac{dI_L}{dt} \quad \text{Inductor Law}$$

$$I_C = C \frac{dV(t)}{dt} \quad \text{Capacitor Law}$$

differentiate capacitor law with respect to time

$$\frac{dI_c}{dt} = C \frac{d^2 V(t)}{dt^2} = - \frac{dI_L}{dt} = - \frac{V(t)}{L}$$



So

$$\frac{d^2 V(t)}{dt^2} = - \frac{1}{LC} V(t)$$

This is a second order, linear differential equation with constant coefficients

It requires two initial conditions

These correspond to the initial charge on the capacitor and the initial current in the inductor.


$$Q(0) = C V_c(0) = C V(0)$$

$$I_L(0) = -I_c(0) = -C \left. \frac{dV}{dt} \right|_0$$

THUS:  $V(0) = \frac{Q(0)}{C}$

$$\left. \frac{dV(0)}{dt} \right|_0 = - \frac{I_L(0)}{C}$$

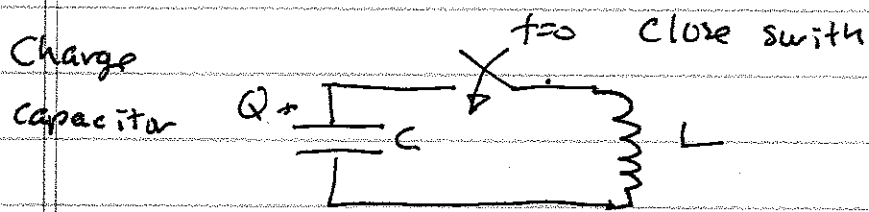
Let's suppose ~~for~~ for simplicity  $I_L(0) = 0$



Solution for  $V(t)$



$$V(t) = V(0) \cos \omega t \quad \leftarrow \text{Verify}$$

where  $\omega = 1/\sqrt{LC}$

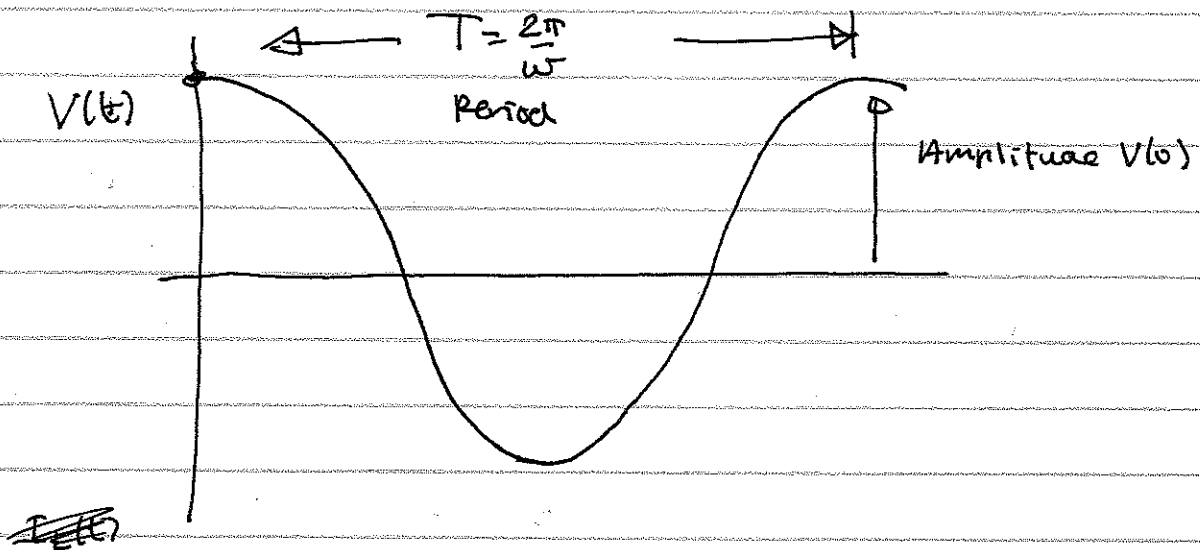

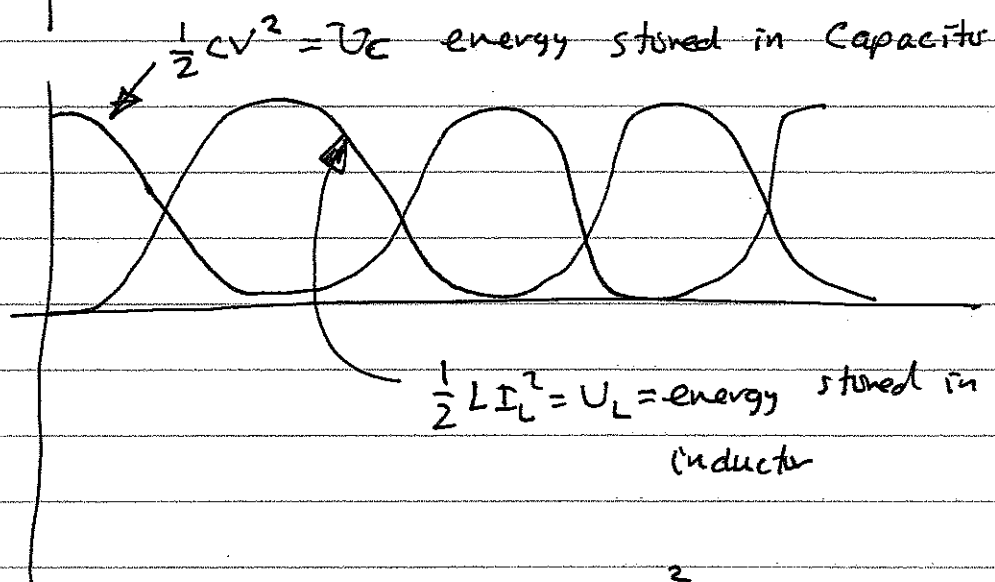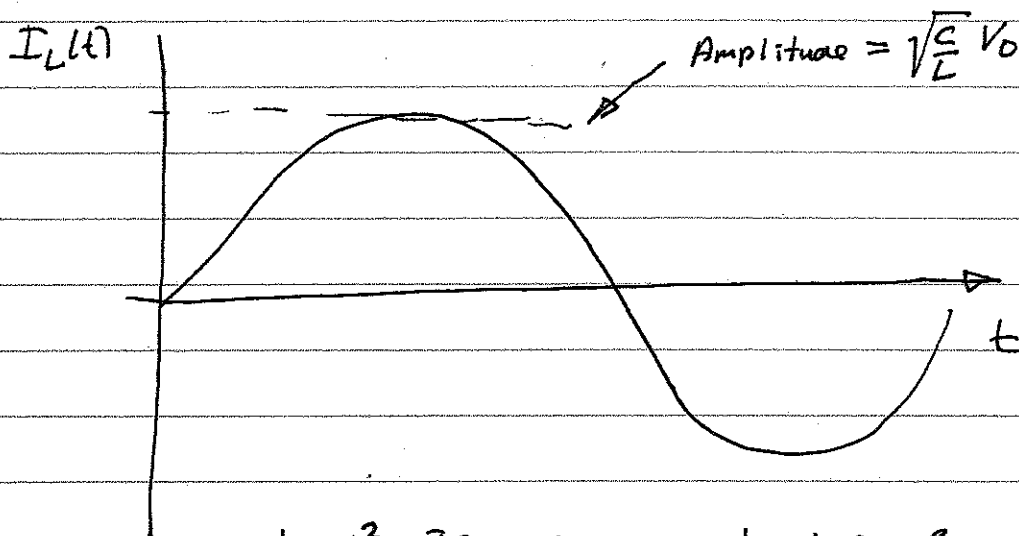34.40

$$I_L(t) = -C \frac{dV}{dt} = C\omega V_0 \sin\omega t = \sqrt{\frac{C}{L}} V_0 \sin\omega t$$



$$U_C + U_L = \text{const} = \frac{1}{2} C V(0)^2$$