

Digital Logic Design

ENEE 244-010x

Lecture 15


Announcements

- Homework 7 due Wednesday 11/4
- Coming up: Midterm on 11/11
 - Topics for Midterm posted online
 - Review problems will be posted by Tuesday night


Agenda

- Last time:
 - Decimal Adders (5.2)
 - Comparators (5.3)
 - Decoders (5.4)
 - Encoders (5.5)
 - Multiplexers (5.6)
- This time:
 - Logic Design with Decoders and Multiplexers (5.4, 5.6)
 - Start Programmable Logic Devices (PLD) (5.7)

Logic Design Using Decoders

 

Logic Diagram

 

Symbol

Inputs			Outputs							
x_2	x_1	x_0	z_0	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Truth Table

Logic Design Using Decoders

- An n -to- 2^n line decoder is a minterm generator.
- By using or-gates in conjunction with an n -to- 2^n line decoder, realizations of Boolean functions are possible.
- Do not correspond to minimal sum-of-products.
- Are simple to produce. Particularly convenient when several functions of the same variable have to be realized.

Minterms using OR Gates

 


Figure 5.19 Realization of the Boolean expressions $f_1(x_2, x_1, x_0) = \sum m(1, 2, 4, 5)$ and $f_2(x_2, x_1, x_0) = \sum m(1, 5, 7)$ with a 3-to-8-

Minterms using NOR Gates


 


Figure 5.20 Realization of the Boolean expressions $f_1(x_2, x_1, x_0) = \Sigma m(0, 1, 3, 4, 5, 6) = \overline{\Sigma m(2, 7)}$ and $f_2(x_2, x_1, x_0) = \Sigma m(1, 2, 3, 4, 6) = \overline{\Sigma m(0, 5, 7)}$ with a 3-to-8-line decoder and two nor-gates.



Logic Design with Multiplexers

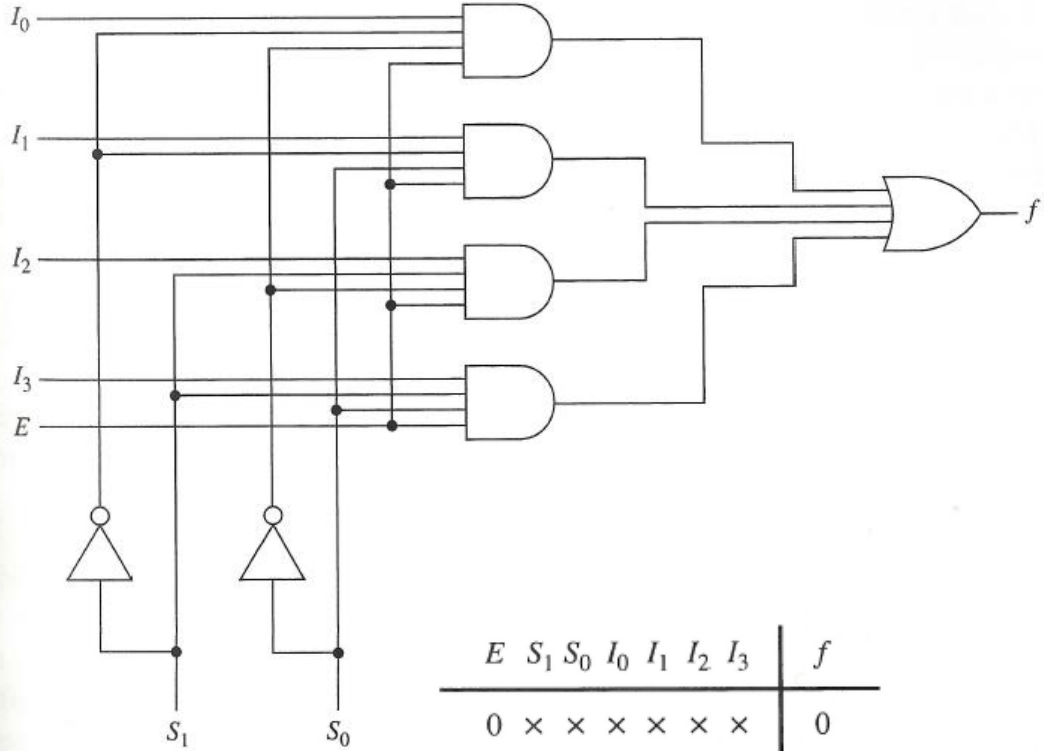

Logic Diagram

E	S_1	S_0	I_0	I_1	I_2	I_3	f
0	x	x	x	x	x	x	0
1	0	0	0	x	x	x	0
1	0	0	1	x	x	x	1
1	0	1	x	0	x	x	0
1	0	1	x	1	x	x	1
1	1	0	x	x	0	x	0
1	1	0	x	x	1	x	1
1	1	1	x	x	x	0	0
1	1	1	x	x	x	1	1

Truth Table

 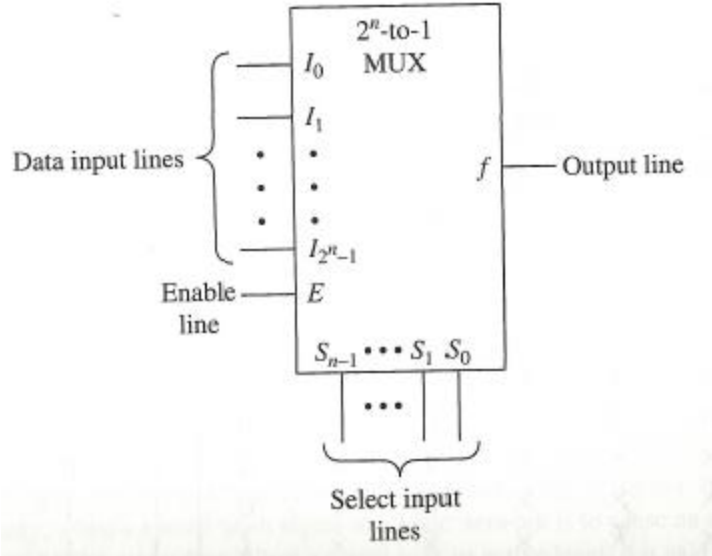

Symbol

Logic Design with Multiplexers

x	y	z	f
0	0	0	f_0
0	0	1	f_1
0	1	0	f_2
0	1	1	f_3
1	0	0	f_4
1	0	1	f_5
1	1	0	f_6
1	1	1	f_7

The Boolean expression corresponding to this truth table can be written as:

$$\begin{aligned} f(x, y, z) &= f_0 \cdot \bar{x} \bar{y} \bar{z} + f_1 \cdot \bar{x} \bar{y} z + f_2 \cdot \bar{x} y \bar{z} + f_3 \cdot \bar{x} y z + f_4 \cdot x \bar{y} \bar{z} \\ &+ f_5 \cdot x \bar{y} z + f_6 \cdot x y \bar{z} + f_7 \cdot x y z. \end{aligned}$$

Logic Design with Multiplexers

- The Boolean expression corresponding to this truth table can be written as:


$$f(x, y, z) = f_0 \cdot \bar{x} \bar{y} \bar{z} + f_1 \cdot \bar{x} \bar{y} z + f_2 \cdot \bar{x} y \bar{z} + f_3 \cdot \bar{x} y z + f_4 \cdot x \bar{y} \bar{z} + f_5 \cdot x \bar{y} z + f_6 \cdot x y \bar{z} + f_7 \cdot x y z.$$

- The Boolean expression for an 8-to-1-line multiplexer is:

$$f = (I_0 \bar{S}_2 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_2 \bar{S}_1 S_0 + I_2 \bar{S}_2 S_1 \bar{S}_0 + I_3 \bar{S}_2 S_1 S_0 + I_4 S_2 \bar{S}_1 \bar{S}_0 + I_5 S_2 \bar{S}_1 S_0 + I_6 S_2 S_1 \bar{S}_0 + I_7 S_2 S_1 S_0).$$


Logic Design with Multiplexers

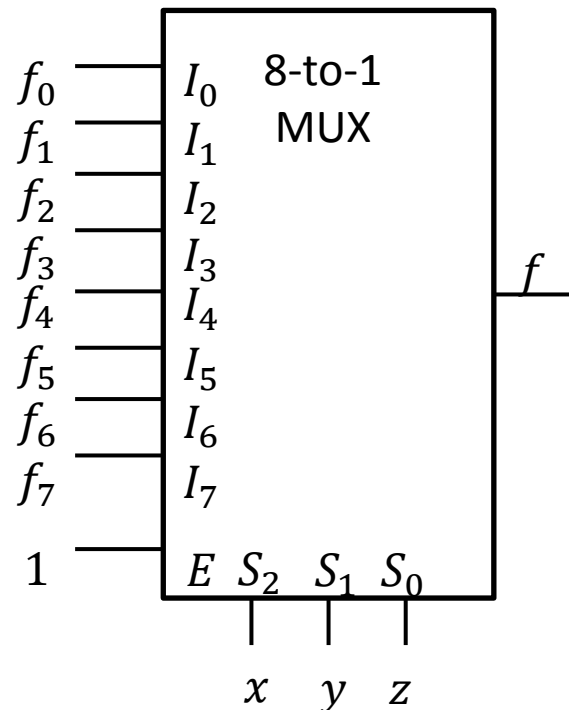- If E is logic-1 then the latter is transformed into the former by replacing I_i with f_i , S_2 with x , S_1 with y , and S_0 with z .
- Placing x, y, z on the select lines S_2, S_1, S_0 , respectively and placing the functional values f_i on data input lines I_i .



Example:

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

Logic Design with Multiplexers

- If at least one input variable of a Boolean function is available in both its complemented and uncomplemented form, any n -variable function is realizable with a 2^{n-1} -to-1-line multiplexer.
- For the case of a 3-variable function, only a 4-to-1 multiplexer is needed.

- $$f(x, y, z) = f_0 \cdot \bar{x} \bar{y} \bar{z} + f_1 \cdot \bar{x} \bar{y} z + f_2 \cdot \bar{x} y \bar{z} + f_3 \cdot \bar{x} y z + f_4 \cdot x \bar{y} \bar{z} + f_5 \cdot x \bar{y} z + f_6 \cdot x y \bar{z} + f_7 \cdot x y z$$
$$= (f_0 \cdot \bar{z} + f_1 \cdot z) \bar{x} \bar{y} + (f_2 \cdot \bar{z} + f_3 \cdot z) \bar{x} y + (f_4 \cdot \bar{z} + f_5 \cdot z) x \bar{y} + (f_6 \cdot \bar{z} + f_7 \cdot z) x y$$

- When $E = 1$, 4-to-1 Multiplexer has the form

$$I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$

Logic Design with Multiplexers

$$f(x, y, z)$$

$$= (f_0 \cdot \bar{z} + f_1 \cdot z)\bar{x}\bar{y} + (f_2 \cdot \bar{z} + f_3 \cdot z)\bar{x}y \\ + (f_4 \cdot \bar{z} + f_5 \cdot z)x\bar{y} + (f_6 \cdot \bar{z} + f_7 \cdot z)xy$$


4-to-1 Multiplexer has the form

$$f = I_0\bar{S}_1\bar{S}_0 + I_1\bar{S}_1S_0 + I_2S_1\bar{S}_0 + I_3S_1S_0$$

- Realization of $f(x, y, z)$ is obtained by placing the x and y variables on the S_1, S_0 select lines, the single variable functions $f_i \cdot \bar{z} + f_j \cdot z$ on the data input lines and let $E = 1$.
- Note: $f_i \cdot \bar{z} + f_j \cdot z$ reduce to 0, 1, z or \bar{z} .


Example

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

Example



x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


Logic Design with Multiplexers and K-maps

- Consider 3-variable Karnaugh map. Assume x is placed on the S_1 line and y is placed on the S_0 line.
- We get that the output is: $I_0\bar{x}\bar{y} + I_1\bar{x}y + I_2x\bar{y} + I_3xy$
- $I_0\bar{x}\bar{y}$ corresponds to those cells in which $x = 0, y = 0$
- $I_1\bar{x}y$ corresponds to those cells in which $x = 0, y = 1$
- $I_2x\bar{y}$ corresponds to those cells in which $x = 1, y = 0$
- I_3xy corresponds to those cells in which $x = 1, y = 1$


K-map representation

  


I_0 map

 

I_1 map

 


I_2 map

 

I_3 map


Example

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

Realization

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


Alternative Structures

$$S_1 = y, S_0 = z$$

yz


00 01 11 10

 

$$S_1 = y$$

yz

00 01 11 10

 

Note that order of variables on input lines matters!

8-to-1-line multiplexers and 4-variable Boolean functions

- Can do the same thing, three variables are placed on select lines, inputs to the data lines are single-variable functions.
- Example:

 


Figure 5.45 Realization of $f(w,x,y,z) = \Sigma m(0,1,5,6,7,9,12,15)$.
 (a) Karnaugh map. (b) Multiplexer realization.

Can we do better?

- By allowing realizations of m -variable functions as inputs to the data input lines, 2^n -to-1-line multiplexers can be used in the realization of $(n + m)$ -variable functions.
- E.g.: input variables w and x are applied to the S_1, S_0 select inputs. Functions of the y and z variables appear at the data input lines.

K-map Structure


 
 
 
 
 







Figure 5.46 Using a four-variable Karnaugh map to obtain a Boolean function realization with a 4-to-1-line multiplexer.

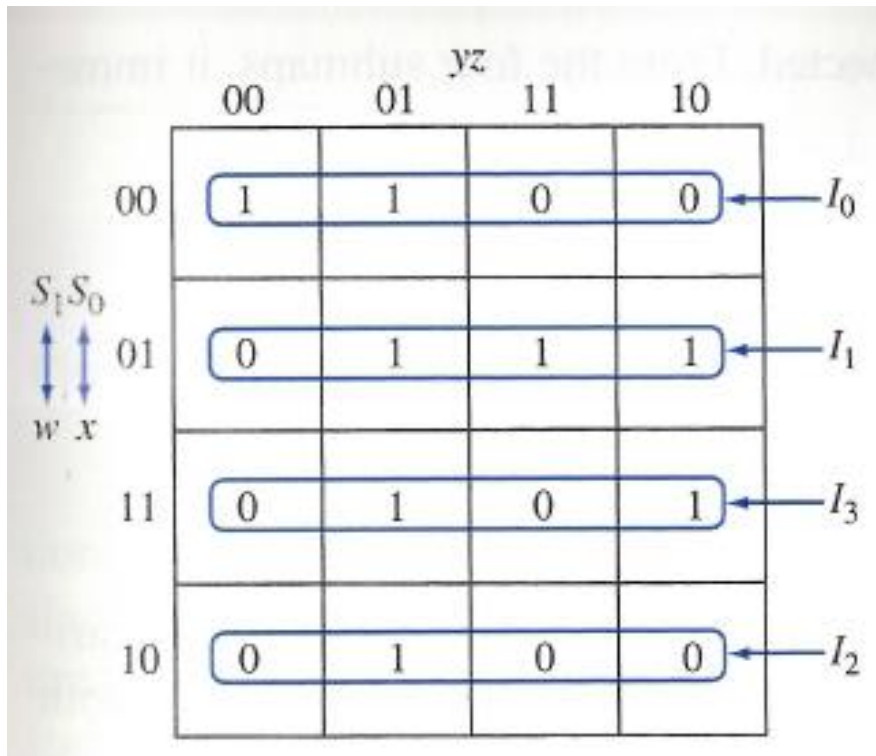Example:


$$f(x, y, z) = \sum m(0,1,5,6,7,9,13,14)$$



Example

     

Example

 

Multiplexer Tree

