

Digital Logic Design

ENEE 244-010x

Lecture 21

Announcements

- No homework over break
 - Homework 9 will be posted on Monday, 11/30.

Agenda


- Last time:
 - Structure and Operation of Clocked Synchronous Sequential Networks (7.1)
 - Analysis of Clocked Synchronous Sequential Networks (7.2)
- This time:
 - Modeling Clocked Synchronous Sequential Network Behavior (7.3)
 - State Table Reduction (7.4)

Modeling clocked synchronous sequential network behavior


- Approach for the synthesis of clocked synchronous sequential networks:
 - State table/state diagram is constructed from word specifications.
 - State reduction technique to obtain a state table with minimum number of states.
 - Transition table is formed by coding the states of the state table.
 - Excitation table is constructed based on the flip-flop types to be used.
 - From the excitation table, the excitation and output expressions for the network are determined.
 - Finally, the logic diagram is drawn.

 Examples of Modeling Step

State Diagram for Mealy serial binary adder



(a)

 

(b)

Figure 7.12 Obtaining the state diagram for a Mealy serial binary adder.
(a) Partial state diagram.
(b) Completed state diagram.

State Diagram for Moore serial binary adder

 



Figure 7.13 State diagram for a Moore serial binary adder.

A Sequence Recognizer

- Network produces a 1 output iff the current input and the previous three inputs correspond to either 0110 or 1001
- 0110/1001 Sequence Recognizer
- The 1 output is to occur at the time of the fourth input of the recognized sequence. Outputs of 0 are to be produced at all other times.
- A Mealy network model is developed since the output is a function of the current input x .
- Network is not required to reset upon the occurrence of the fourth input.
- Sequences may overlap.
- Example:

$x = 0$ 0 1 1 0 1 1 1 0 0 1 0 1 0 1 1 0 0 1 1 0 0 1 0 1
 $z = 0$ 0 0 0 0 1 0 0 0 0 0 1 0 0 0 0 0 1 0 1 0 1 0 1 0 0

A Sequence Recognizer

 

A: No inputs received (initial state).

B: Last input received was 0 but not 10 nor 100.

C: Last input received was 1 but not 01 nor 011.

D: Last two inputs received were 01.

E: Last two inputs received were 10.

F: Last three inputs received were 011.

G: Last three inputs received were 100.

(b)

Figure 7.16 A 0110/1001 sequence recognizer. (a) Beginning the detection of the sequences 0110 or 1001. (b) Definition of states. (c) Completing the detection of the two sequences 0110 or 1001. (d) Completed state diagram.

Another Sequence Recognizer

- An output of 1 is to be produced iff the three input symbols following two consecutive input 0's include at least one 1.
- At all other times the output is to be 0.
- The output of 1 is to be coincident with the third input symbol of the three-input-symbol sequence.
- Upon completing the analysis of the three input symbols following the pair of 0 inputs, the network is to reset itself and await for another pair of 0's and then at least one 1 in the following sequence of three input symbols.
- Since the output is to be coincident with the third input symbol, a Mealy network is implied.
- Example:

$$\begin{array}{l}
 x = 0\ 1\ \mathbf{0\ 0\ 0\ 1\ 0}\ 0\ 1\ \mathbf{0\ 0\ 1\ 0\ 0}\ 1\ 0\ 0\ 0\ 0\ 0\ \mathbf{0\ 0\ 0\ 1\ 1} \\
 z = 0\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 1
 \end{array}$$

A Sequence Recognizer

 


Figure 7.15 State diagram for a sequence recognizer. (a) Detection of two consecutive 0's. (b) Partial analysis of the three-symbol sequence. (c) Completed state diagram. (d) Definition of states.

Final Example

- Single input x and a single output z .
- The output of the network is initially 0.
- Changes on the next input immediately following each even occurrence of $x = 1$.
- The effect of the input is to be delayed by one clock period. The value of x during the next clock period does not affect the output of the network at that time.
- A Moore sequential network is to be realized
- Example:

$x = 0\ 0\ 1\ 1\ 0\ 0\ 0\ 1\ 0\ 1\ 0\ 1\ 1\ 1\ 0$

 a b c

$z = 0\ 0\ 0\ 0\ 1\ 1\ 1\ 1\ 1\ 1\ 0\ 0\ 0\ 1\ 1$

Final Example

 


Figure 7.17 State diagram for the final example.

Table 7.12 State table for Fig. 7.17

Present state	Next state		Output (z)
	Input (x)		
	0	1	
*A	A	B	0
B	B	C	0
C	C	D	1
D	D	A	1

- A: The output changes to 0 since the last occurrence of $x = 1$ was even
- B: The output remains at 0 since the last occurrence of $x = 1$ was odd
- C: The output changes to 1 since the last occurrence of $x = 1$ was even
- D: The output remains at 1 since the last occurrence of $x = 1$ was odd

State Table Reduction

State Table Reduction

- The state table is a description of the terminal behavior of a clocked synchronous sequential network.
- During the process of creating the state table, more states may be defined than are really necessary.
- In analysis of synchronous sequential networks, bin codes for the states were replaced by arbitrary symbols when going from transition table to state table.
- For synthesis, the opposite process is performed: Arbitrary state symbols are replaced with binary codes.
- Smaller number of binary digits necessary -> smaller number of flip-flops.
- Reducing number of states may also simplify the combinational logic.

State Table Reduction Procedure

- 3-step process:
 - Equivalent pairs of states are determined
 - Sets of equivalent states are established
 - Reduced state table is constructed with one state for each of the sets of equivalent states

Determining Equivalent Pairs of States

- Recall that given a state table, an input sequence and some starting state, the resulting output sequence can be determined.
- Assume we run two experiments:
 - One starts in state p
 - The second starts in state q

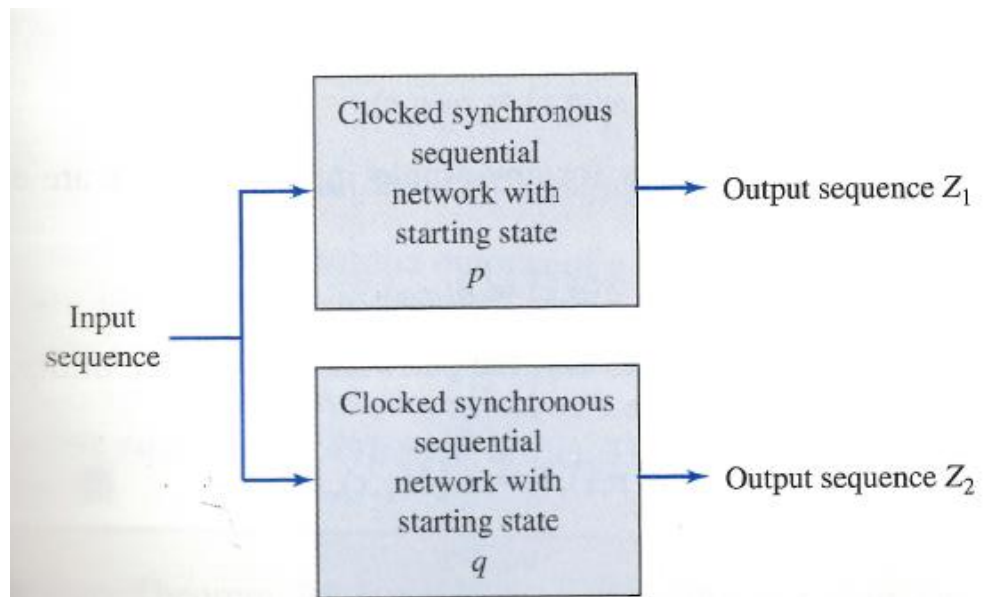


Figure 7.18 Experiment for determining equivalent pairs of states.

Determining Equivalent Pairs of States

- States p and q are said to be equivalent or indistinguishable ($p \equiv q$) iff for all input sequences applied to the two starting states, identical output sequences from both networks result ($Z_1 \equiv Z_2$).
- If states p and q are not equivalent, then they are said to be distinguishable ($p \neq q$).

Determining Equivalent Pairs of States

Theorem:

Two states p and q of a clocked synchronous sequential network are equivalent iff for each combination of values of the input variables

1. Their outputs are identical
2. Their next states are equivalent