

ENEE244-02xx
Digital Logic Design

Lecture 7

Announcements

- Homework 3 due on Wednesday, Oct. 30.
- Midterm on Wednesday, Oct. 8.
- List of topics for Midterm up on course webpage.
 - Review sheet will be posted by end of week.

Agenda

- Last time:
 - Gates and Combinational Networks (3.7)
 - Incomplete Boolean Functions and Don't Care Conditions (3.8)
 - Universal Gates (3.9.3)
- This time:
 - NAND/NOR Gate Realizations (3.9.4-3.9.6)
 - Some examples of Synthesis Procedure
 - The simplification problem (4.1)
 - Prime Implicants (4.2)
 - Prime Implicates (4.3)

NAND-Gate Realizations

- Naïve approach: build network out of AND/OR/NOT gates, use the universal property above to replace each one with several NAND gates.
- A better approach: manipulate Boolean expression into the form $\text{NAND}(A, B, \dots, C)$

NAND-Gate Realizations

- Basic idea:
 - Use the property: $x + y = \overline{(\bar{x})(\bar{y})}$
 - i.e. $x + y = \text{NAND}(\bar{x}, \bar{y})$
- Keep doing this recursively.

NAND-Gate Realizations

- Example:

$$f(w, x, y, z) = \overline{wz} + w\overline{z}(x + \overline{y})$$

$$= \overline{\overline{wz} [w\overline{z}(x + \overline{y})]}$$

– $\overline{(\overline{wz})}$ --already in correct form, equivalent to $NAND(\overline{w}, z)$

– $\overline{w\overline{z}(x + \overline{y})} = NAND(w, \overline{z}, (x + \overline{y}))$

– $x + \overline{y} = \overline{\overline{x}y}$

– $f(w, x, y, z) =$
 $NAND(NAND(\overline{w}, z), NAND(w, \overline{z}, (NAND(\overline{x}, y))))$

NAND-Gate Realizations

- Only works if highest-order operation is an or-operation.
- **Highest-order operation** is the last operation that is performed when the expression is evaluated.
- What to do otherwise? Negate and repeat the procedure for \bar{f} . Then note that
$$f(x_1, \dots, x_n) = \text{NAND}(1, \bar{f}(x_1, \dots, x_n))$$

NAND-Gate Realization

- Example:

$$f(x, y, z) = (x + y)(\bar{y} + z)$$

$$f(x, y, z) = \text{NAND}(1, \overline{f(x, y, z)})$$

$$- \overline{f(x, y, z)} = \overline{(x + y)(\bar{y} + z)} = \text{NAND}(x + y, \bar{y} + z)$$


$$- x + y = \overline{\bar{x} \bar{y}} = \text{NAND}(\bar{x}, \bar{y})$$

$$- \bar{y} + z = \overline{y \bar{z}} = \text{NAND}(y, \bar{z})$$

$$- f(x, y, z) = \text{NAND}(1, \text{NAND}(\text{NAND}(\bar{x}, \bar{y}), \text{NAND}(y, \bar{z})))$$

NAND Implementation Example
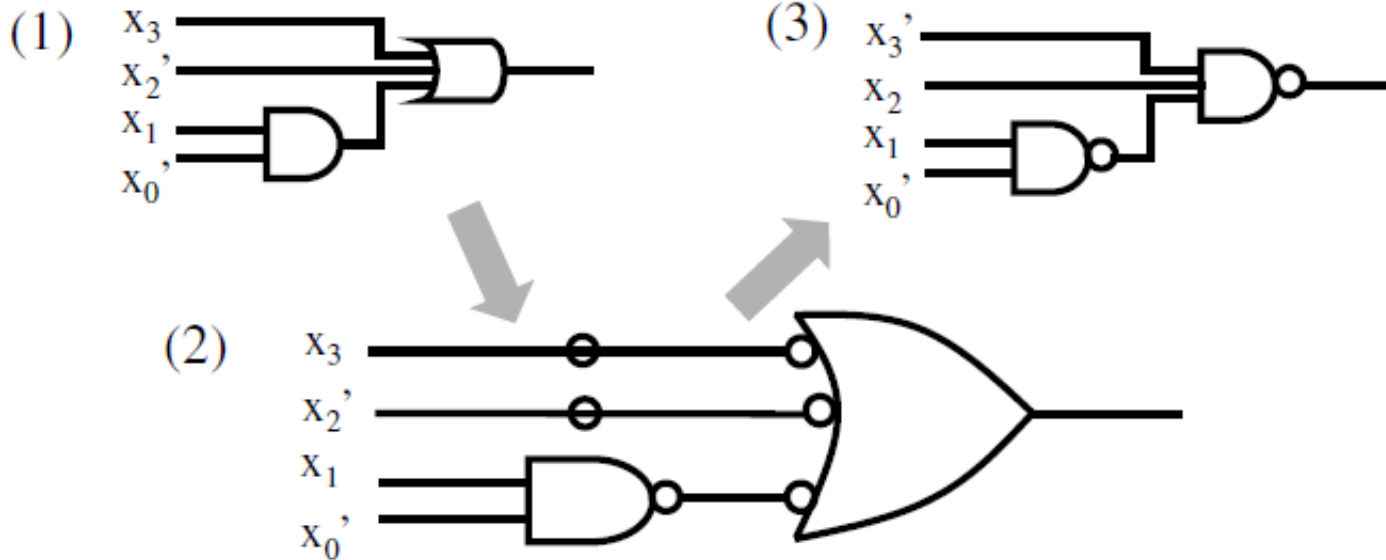
$$f(x_0, x_1, x_2, x_3) = x_3 + \bar{x}_2 + x_1\bar{x}_0$$




General NAND Implementation


- Draw the {AND,OR,NOT} implementation
- AND \Rightarrow AND-NOT-NOT \Rightarrow NAND-NOT
- OR \Rightarrow NOT-NOT-OR \Rightarrow NOT-NAND
- Delete “NOT-NOT”
- NOT \Rightarrow NAND

NAND-Gate Realizations

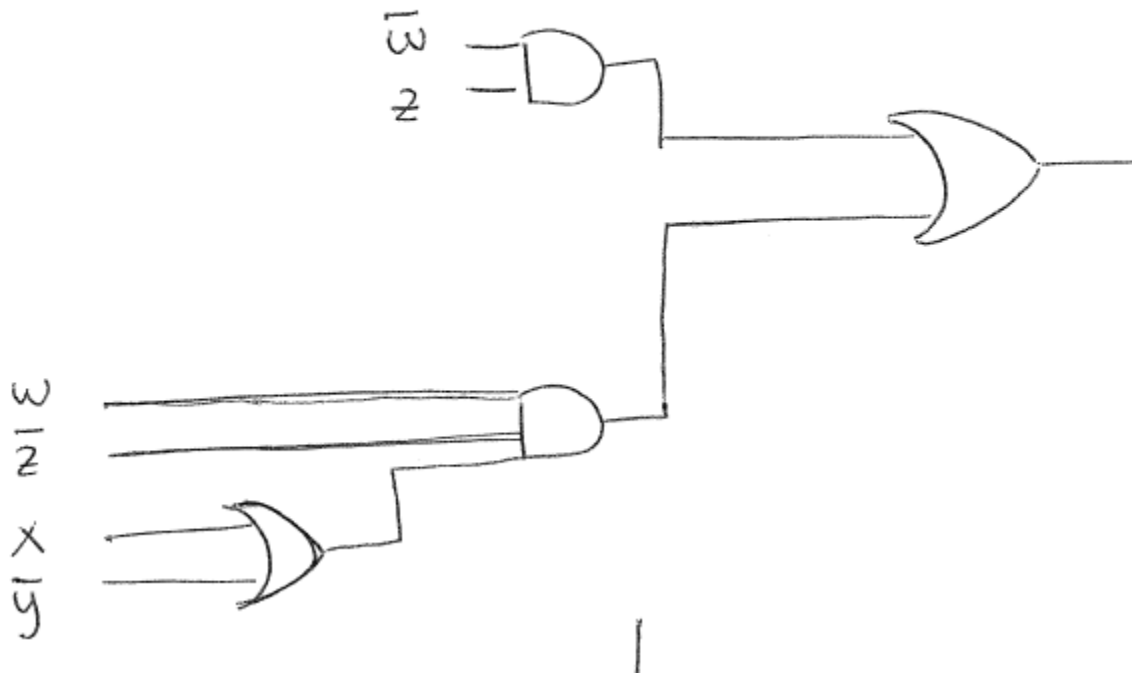
① $f(w, x, y, z) = \bar{w}z + w\bar{z}(x + \bar{y})$



NAND-Gate Realizations

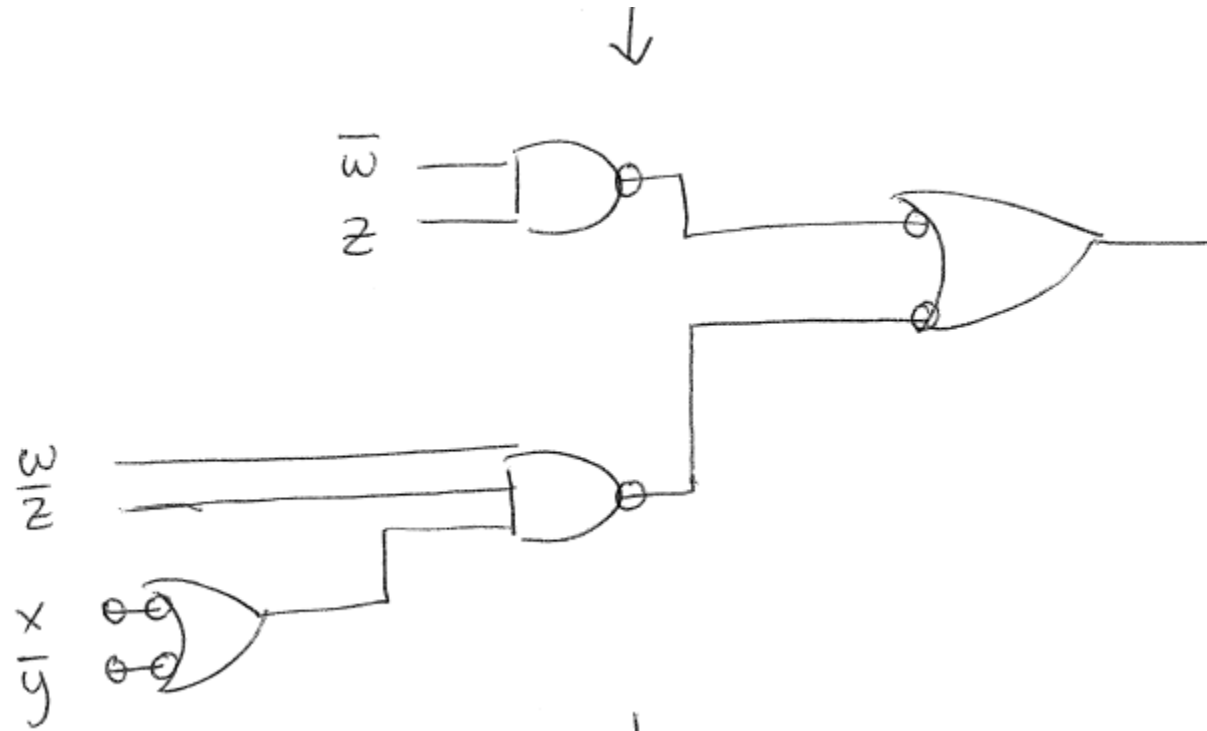


NAND-Gate Realizations

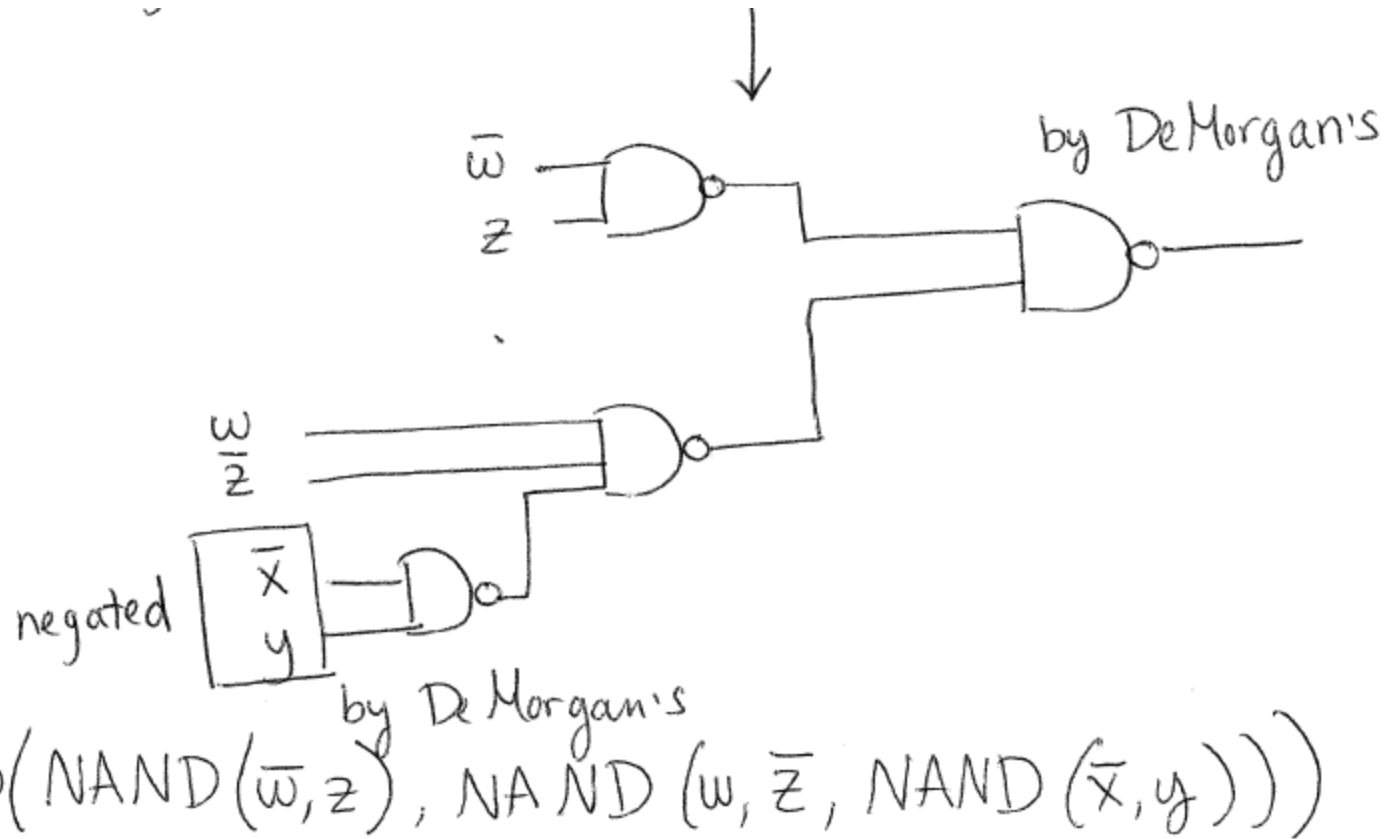


NAND-Gate Realizations


② $f(x, y, z) = (x + y)(\bar{y} + z)$

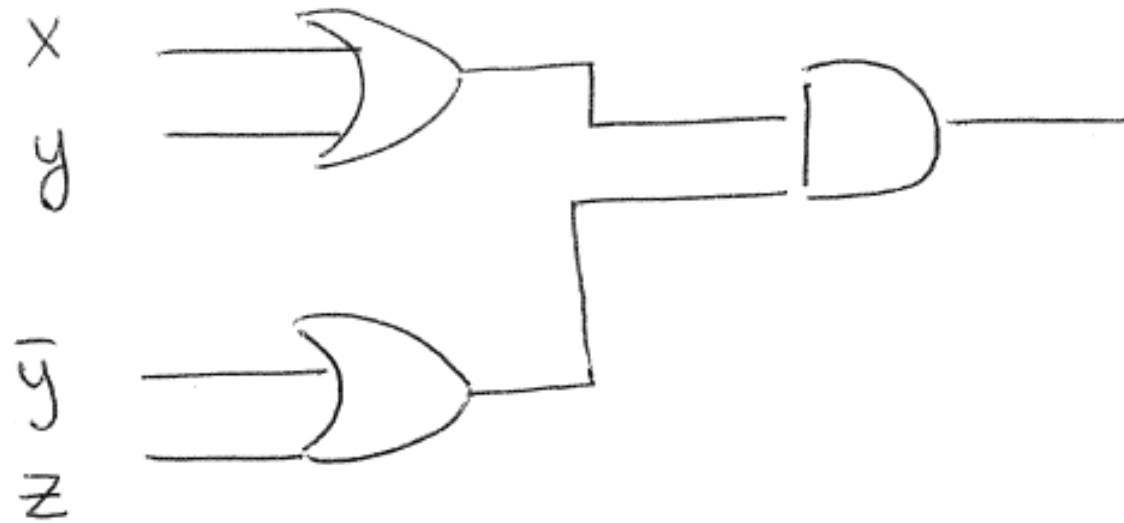

NAND-Gate Realizations

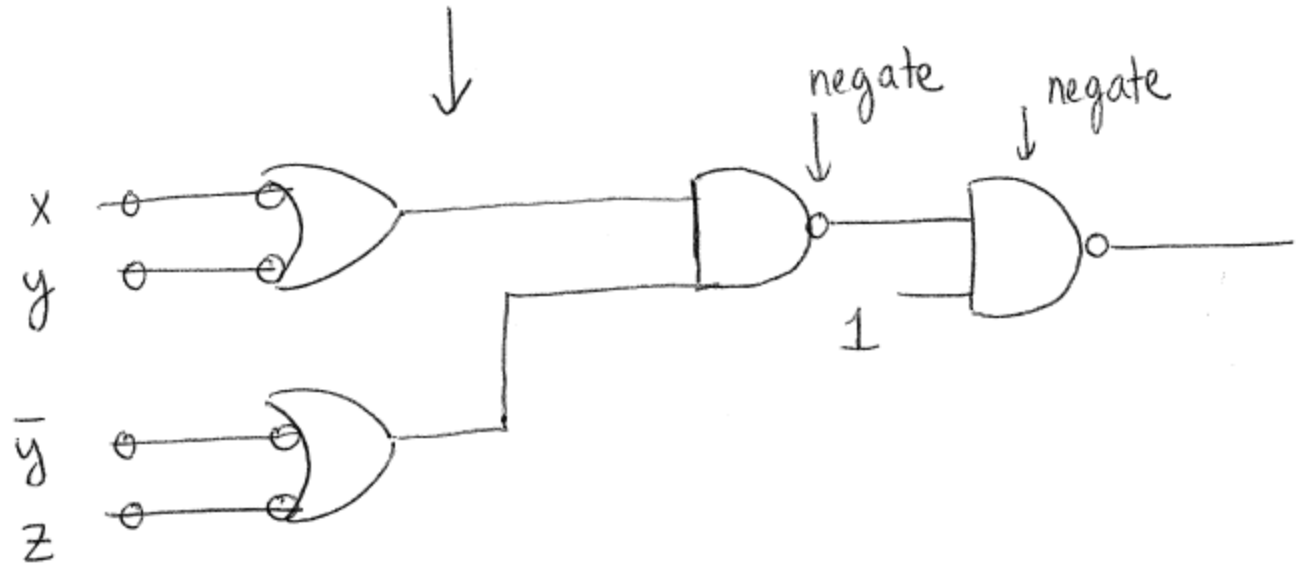

NAND-Gate Realizations

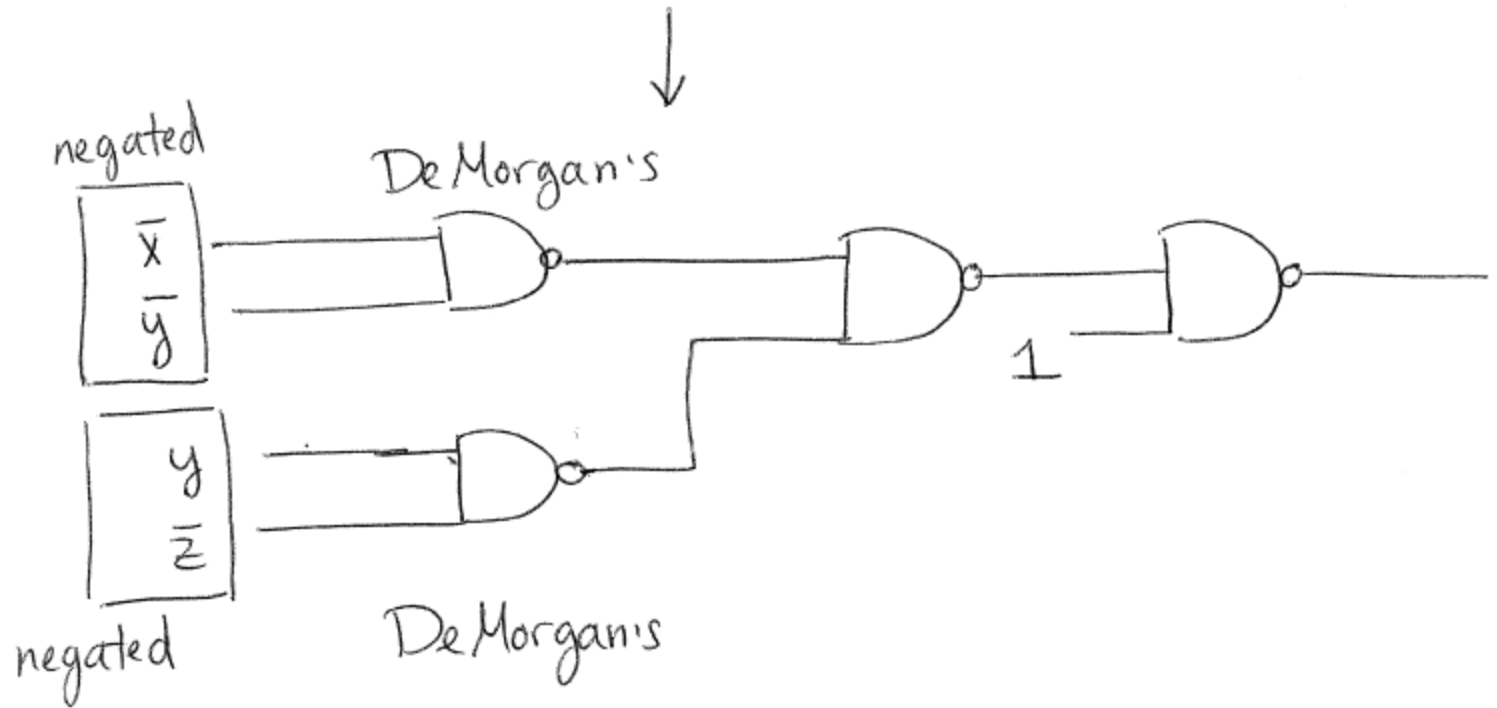

$$\text{NAND}(1, \text{NAND}(\text{NAND}(\bar{x}, \bar{y}), \text{NAND}(y, \bar{z})))$$

NOR-Gate Realizations

- Essentially the same procedure. See Section 3.9.5 in the textbook.

In-Class Exercise

See handout (lec_7.pdf)

Synthesis Procedure Examples

Synthesis Procedure

- High-level description: A function with finite domain and range.
- Binary-level: All input-output variables are binary.

Example 1

A system takes one decimal digit and outputs 0 on even number and 1 on odd number.

- High-level:

- Input: $x \in \{0,1,2,3,4,5,6,7,8,9\}$

- Output: $z \in \{0,1\}$

- Function:

$$z = F(x) = \begin{cases} 0 & x=0,2,4,6,8 \\ 1 & x=1,3,5,7,9 \end{cases}$$

x	0	1	2	3	4	5	6	7	8	9
z	0	1	0	1	0	1	0	1	0	1

Example 1 (cont'd)

- Binary-level (using BCD)

- Input variables: x_3, x_2, x_1, x_0

- Output variables: z

- Functions:

$$z(x_3, x_2, x_1, x_0) = x_0$$



x	$x_3x_2x_1x_0$	z
0	0 0 0 0	0
1	0 0 0 1	1
2	0 0 1 0	0
3	0 0 1 1	1
4	0 1 0 0	0
5	0 1 0 1	1
6	0 1 1 0	0
7	0 1 1 1	1
8	1 0 0 0	0
9	1 0 0 1	1

Example 2

A system takes one decimal digit and outputs its 9's complement.

- High-level:
 - Input: $x \in \{0,1,2,3,4,5,6,7,8,9\}$
 - Output: $z \in \{0,1,2,3,4,5,6,7,8,9\}$
 - Function: $z = F(x) = 9 - x$

x	0	1	2	3	4	5	6	7	8	9
z	9	8	7	6	5	4	3	2	1	0

Example 2 (cont'd)

- Binary-level (using BCD)

- Input variables: x_0, x_1, x_2, x_3
- Output variables: z_0, z_1, z_2, z_3
- Functions: (sum of minterms)

$$z_3(x_3, x_2, x_1, x_0) = \sum m(0, 1)$$

$$z_2(x_3, x_2, x_1, x_0) = \sum m(2, 3, 4, 5)$$

$$z_1(x_3, x_2, x_1, x_0) = \sum m(2, 3, 6, 7)$$

$$z_0(x_3, x_2, x_1, x_0) = \sum m(0, 2, 4, 6, 8)$$



X	$x_3x_2x_1x_0$	$z_3z_2z_1z_0$	Z
0	0 0 0 0	1 0 0 1	9
1	0 0 0 1	1 0 0 0	8
2	0 0 1 0	0 1 1 1	7
3	0 0 1 1	0 1 1 0	6
4	0 1 0 0	0 1 0 1	5
5	0 1 0 1	0 1 0 0	4
6	0 1 1 0	0 0 1 1	3
7	0 1 1 1	0 0 1 0	2
8	1 0 0 0	0 0 0 1	1
9	1 0 0 1	0 0 0 0	0