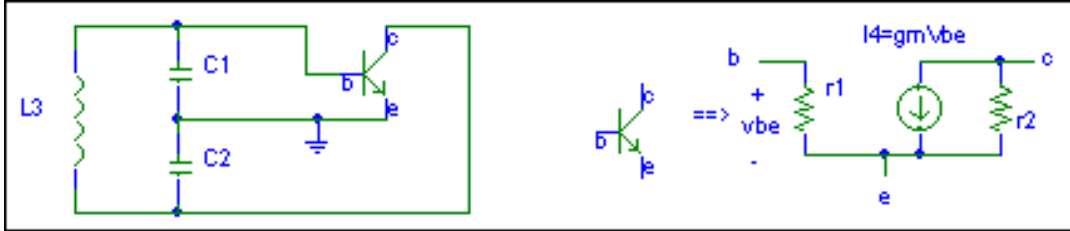


ENEE 610 Final Exam; 12/19/05

Open book & notes. Only signed work, which designates all the work is your own, will be graded.

1. (50 points)

For the following small signal version of a Colpitts oscillator, use the BJT transistor equivalent circuit shown on the right.



a. Draw an oriented graph numbering branches as per the element numbering and nodes $0=e=\text{ground}$, $1=b$, $2=c$; orient all branches to point toward the lower numbered node. For this include $C1$ and $r1$ together in branch 1, so $y1(s)=g1+sC1$, and $C2$ and $r2$ in branch 2 as $y2(s)=g2+sC2$.

b. Choose branches 1 and 2 for the tree and give the cut set and tie set matrices.

c. Give the branch by branch admittance and use the cut set matrix to find the (2×2) nodal admittance matrix, $Y(s)$. Check by finding the (3×3) indefinite admittance $Y_{ind}(s)$ and then grounding the e node (chosen as node 3 prior to **becoming 0 when** grounding).

d. Give the even and odd parts of $\det[Y(s)]$. For the circuit to be an oscillator both of these should be 0 at the oscillation frequency $s=j\omega_0$.

e. The two equations of part d determine a bias collector current, I_c , since $g_m=I_c/V_T$, $g_1=(1/r1)=g_\pi=I_c/(\alpha V_T)$, $g_2=(1/r2)=g_o=I_c/V_A$. Determine I_c in terms of α , V_T , V_A , L , $C1$ and $C2$. [the normal $g_\pi=I_c/(\{\beta+1\}V_T)$ but for this problem $I_c/(\alpha V_T)$ is used].

f. Choose $\alpha=0.999$, $V_A=100$, $V_T=0.026$, $L3=5\text{nHy}$, $C1=5\text{pFd}$ with $0.01 < (C2/C1) < 100$, and make reasonable approximations to determine for which $C2$ the circuit will oscillate and find I_c and ω_0 for those $C2$.

2. (50 points)

a. For what values of the real parameters a and b is the admittance $y(s)=[(s^2+a)(s^2+b)/[as(s^2+1)]]$ positive-real?

b. For $b=1/a$ determine for which a this $y(s)$ is lossless and give a second Foster synthesis with a as a parameter. Give also a first Cauey synthesis of this $y(s)$ when $b=1/a$

c. Using the second Foster expansion show that any rational lossless driving point admittance satisfies $y_{LC}(s)=sf(s^2)$ and exhibit $f(s)$ [not $f(s^2)$] as a partial fraction expansion. In a lossless second Foster synthesis of $y_{LC}(s)$, if each inductor is replaced by a resistor then we obtain an RC second Foster synthesis of $y_{RC}(s)$. Give $y_{RC}(s)$ in terms of $f(s)$ and from that give a partial fraction type expansion for $y_{RC}(s)$ and then in turn an RC synthesis.

d. Give the necessary and sufficient conditions that a rational $y(s)$ (with real coefficients) is the driving point admittance of an RC circuit.

e. For such a $y_{RC}(s)$ determine the location of its even part, $Ev[y_{RC}(s)]$, poles and the relation to them of the even part zeros. Sketch $Ev[y_{RC}(s)]$ for real s {hint; look at $dEv[y]/ds$ }