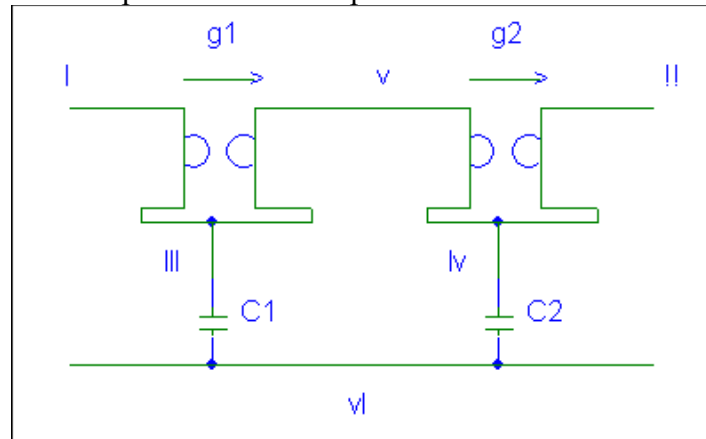


1. (50 points)


For the following circuit

- find the indefinite admittance using the node numbers given
- ground the bottom node to get the definite 5x5 admittance
- use the result to eliminate internal nodes III, IV, and V. in two different ways
 - by eliminating first node III, then IV and then V
 - by eliminating all three at one time
 discuss the advantage of one method over the other
- Call the resulting 2-port admittance Y . Load port 2 in a resistor of resistance r and find the input admittance at port 1.



2. (50 points)

Consider the following circuit.

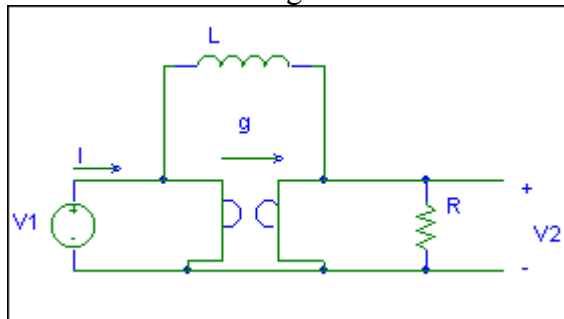

- Draw the adjoint to the non-source portion of the circuit and set up sources on the adjoint in order to calculate the derivative of the transfer function $V2/V1(s)$ with respect to the resistance R and also with respect to L . Calculate these derivatives using the adjoint and check by direct differentiation of the transfer function.
- For the 2-port formed by the gyrator and the inductor, find the input admittance $y(s)$ when loaded by a load of admittance $y_L(s)$ and then find $y_L(s)$ in terms of $y(s)$. Check in the case that $y_L(s)=1/R$ (as shown in the above circuit diagram).
- Form the even part of $y(s)$ for a general load $y_L(s)$ and for the resistor load shown. From the latter find the zeros of the even part of $y(s)$ when $L=2$, $g=3$, $R=5$.