

ENEE 303 Fall 2012 – Midterm Exam Th 10/25/12

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

For the following problems $V_{DD}=V_{CC}=10V$.


For the npn transistors: $\beta = 99$, $V_A=100V$, $C_{\pi}= 20pFd$, $C_{\mu}= 0$; bias $V_{BE}=0.7$

For the NMOS transistors: $K_P=4 \times 10^{-4}$, $V_{TO}=1$, $LAMBDA=0.01$, $W/L=1$

For PMOS transistors: $K_P=2 \times 10^{-4}$, $V_{TO}=-1$, $LAMBDA=0.01$, W/L depends on problem

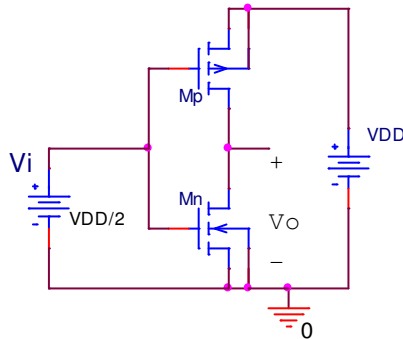1. (30 points, 20 min)


- Give the value of W/L needed for M_p such that $V_o = V_i$
- Find numerically the range of V_o for which both transistors are in saturation.
- From b) find numerically the range of W/L of M_p for which both transistors are in saturation.



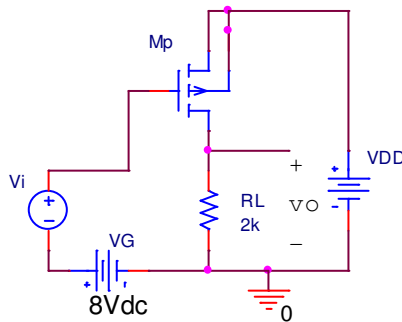2. (25 points, 15 min)

For the following circuit assume that $W/L (=2 \times 125/27)$ is chosen such that V_o is biased to $V_o = 2V$

- Give numerically the transistor's source current I_S , g_m and g_o .
- Draw the small signal equivalent circuit including C_{gs} & C_{gd} using generic symbols (= without numerical values).
- Find (without numerical values) the small signal voltage gain, $v_o/v_i(s)$ and give its poles and zeros.
- Evaluate numerically the poles and zeros when $C_{gs}=C_{gd}=5pFd$.



Continued on next page

3. (45 points, 25 min)

The following two circuits are identical except that one uses a BJT and the other a MOSFET (and possibly different R_b).

Note that the bias current sources have the value of 2mA with 3V across them (held by the bypass capacitors to give $V_S=V_E=3$).

Assume that the coupling and bypass capacitances, C_i and C_{bp} , are extremely large and C_{bp} always holds its initial voltage of 3V.

- Find the bias voltages V_o (with respect to ground) and compare,
- Find the resistor, R_b , values to obtain the desired bias.
- Find the g_m for both and compare; do the same for g_o .

