

EE 303 Midterm Continuation F2012


#1. a) as $V_G = V_D = V_{DD}/2 = 5 = |V_{DS}| = |V_{GS}| \Rightarrow |V_{DS}| > |V_{GS}| - |V_{TO}| \Rightarrow$ saturation of M_p & M_n

$$\Rightarrow I_{Dn} = -I_{Dp} = \frac{K_p W}{L} (V_{GSn} - V_{TO})^2 (1 + \lambda_n V_{DSn})$$

$$= \frac{4 \times 10^{-9} \times 1 \times (5-1)^2 (1 + 0.01 \times 5)}{2} = 2 \times 10^{-4} \times 16 \times 1.05 = 33.6 \times 10^{-4}$$

$$= 3.36 \text{ mA}$$

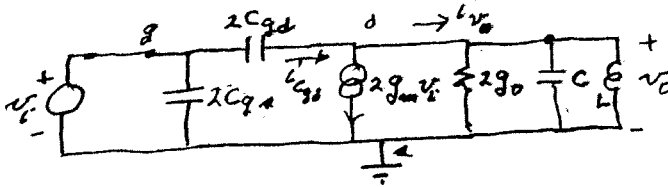b) M_n & M_p become in parallel and have equal g_m, g_o and C 's these become double.



c) $i_{C_{gd}} = 2C_{gd} \dot{v}_i - 2C_{gd} \dot{v}_o$; $i_{v_o} = i_{C_{gd}} - 2g_m v_i = (2g_o + sC + \frac{1}{sL}) v_o$

$\therefore (2g_o + sC + \frac{1}{sL}) v_o = 2C_{gd} \dot{v}_i - 2C_{gd} \dot{v}_o - 2g_m v_i$

$\Rightarrow (2g_o + sC + \frac{1}{sL} + 2C_{gd} s) v_o = (2C_{gd} s - 2g_m) v_i$

$\Rightarrow \frac{v_o(s)}{v_i(s)} = \frac{2sL(C_{gd} s - g_m)}{(C + 2C_{gd})L s^2 + 2g_o L s + 1}$

d) since $C = C_{gd}$, $\frac{v_o}{v_i} = \frac{2sL(C + g_m/C)}{3CLs^2 + 2g_o L s + 1} = \frac{2sL(C + g_m/C)}{3CL(s^2 + \frac{2g_o}{3C}s + \frac{1}{3CL})}$

$= \frac{2}{3} \cdot \frac{s(C + g_m/C)}{s^2 + \frac{2g_o}{3C}s + \frac{1}{3CL}}$; denominator factors
 $s_{1,2} = -\frac{g_o}{C} \pm \frac{1}{2} \sqrt{4(\frac{g_o}{C})^2 - 4 \frac{1}{3CL}}$
 $= -\frac{g_o}{C} [1 \pm \sqrt{1 - \frac{C}{3Lg_o^2}}]$

zeros: $s = 0, g_m/C$

poles: $s = -\frac{g_o}{C} [1 + \sqrt{1 - \frac{C}{3Lg_o^2}}], -\frac{g_o}{C} [1 - \sqrt{1 - \frac{C}{3Lg_o^2}}]$

Numerically need $g_m = \frac{I_{Dn}}{2(V_{GSn} - V_{TO})} = \frac{2 \times 16 \times 1.05 \times 10^{-4}}{2 \times 4} = 4.2 \times 10^{-7}$; $g_o = \frac{\lambda I_{Dn}}{(1 + \lambda V_{DSn})} = \frac{10^{-2} \times 2 \times 16 \times 1.05 \times 10^{-4}}{1.05} = 32 \times 10^{-6}$

$\therefore g_m/C = \frac{4.2 \times 10^{-7}}{10 \times 10^{-12}} = 4.2 \times 10^5$

$g_o/C = \frac{32 \times 10^{-6}}{10 \times 10^{-12}} = 32 \times 10^5$; $\frac{C}{3Lg_o^2} = \frac{1}{3 \times 10 \times 10^{-12} \times 9 \times 32 \times 10^5} = \frac{1}{3 \times 10^8 \times 32 \times 10^{-6} \times 32 \times 10^5} = \frac{10^9}{3 \times 32^2}$

$\Rightarrow - (g_o/C) [1 \pm \sqrt{1 - \frac{C}{3Lg_o^2}}] \approx -32 \times 10^5 [1 \pm \sqrt{1 - \frac{10^9}{3 \times 32^2}}]$

\therefore zero @ $s = 0, +4.2 \times 10^5$

poles @ $s = -32 \times 10^5 [1 + j \frac{3.15 \times 10^9}{32}], -32 \times 10^5 [1 - j \frac{3.15 \times 10^9}{32}]$
 $= -32 \times 10^5 \pm j 3.15 \times 10^9$

#2. If in saturation

$$a) I_S = \frac{K_P W}{2 L} (|V_{GS_p}| - |V_{TO_p}|)^2 (1 + \lambda |V_{DS_p}|) = \frac{4 \times 10^{-4}}{2} \cdot 1 \cdot (V_{DD} - V_G - 1)^2 (1 + \lambda [V_{DD} - V_G])$$


But $I_S = 2 \times 10^{-3} \Rightarrow V_G = I_S \cdot R_L = 2 \times 10^{-3} \times 1 \times 10^3 = 2V$

$$\Rightarrow I_S = 2 \times 10^{-3} = 2 \times 10^{-4} (10 - V_G - 1)^2 (1 + 0.01 [10 - 2]) = 2 \times 10^{-4} (9 - V_G)^2 (1 + 0.08)$$

$$\Rightarrow (9 - V_G)^2 = \frac{10}{1.08} \Rightarrow 9 - V_G = \pm \sqrt{\frac{10}{1.08}} \Rightarrow \text{need } + \text{ as } V_{SG} = 9 - V_G > 0$$

$$\Rightarrow V_G = 9 - \sqrt{\frac{10}{1.08}} ; \text{ check for saturation } V_{SG} - 1 = \sqrt{\frac{10}{1.08}} - 1 = < V_{S0} = 8$$

$$= 9 - 3.043 = 5.957$$

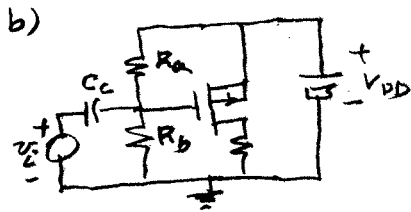


Need C_C large $\rightarrow \infty$


Need $\frac{R_b}{R_a + R_b} V_{DD} = V_G = \frac{1}{1 + R_a/R_b} \cdot V_{DD}$

$$\Rightarrow 1 + \frac{R_a}{R_b} = \frac{V_{DD}}{V_G} \Rightarrow \frac{R_a}{R_b} = \frac{V_{DD}}{V_G} - 1 = \frac{10}{5.957} - 1 \approx 0.68$$

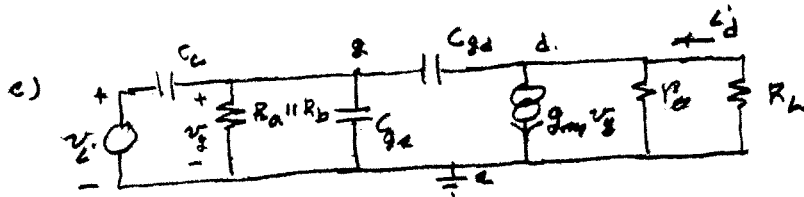Choose R_b large, say $10 \text{ Meg}\Omega \Rightarrow R_a = 6.8 \text{ Meg}\Omega$
if $R_b = 10 \text{ Meg}\Omega$



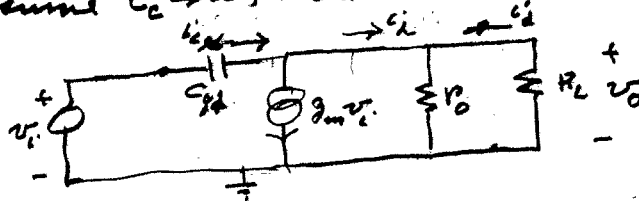d) assume $C_C \rightarrow \infty$, then the circuit is



Now $i_d = -v_o/R_L$
 $= -G_L v_o$

$i_{Cgd} = \alpha Cgd (v_i - v_o)$; $i_L = (g_o + G_L) v_o$
 $= i_{Cgd} - g_m v_i$

$$\Rightarrow (g_o + G_L) v_o = (\alpha Cgd - g_m) v_i - \alpha Cgd v_o$$

$$\Rightarrow v_o = \frac{(\alpha Cgd - g_m)}{\alpha Cgd + g_o + G_L} \cdot v_i$$

$$\Rightarrow \frac{i_d}{v_i} = -G_L \cdot \frac{\alpha - g_m/Cgd}{\alpha + (g_o + G_L)/Cgd}$$

zeros: @ $\omega = g_m/Cgd$
poles: @ $\omega = -(g_o + G_L)/Cgd$