

b), @ $t=0$, M_p is ohmic as $V_{gs}=10$, $V_{sd}=0$ while @ $t=1$, $v_i = v_o = 5 \Rightarrow |V_{gs}| - |V_{tp}| < |V_{sd}|$ & between $t=0$ & $t=1$, M_p switches from ohmic to saturation, this being when $|V_{gs}| - |V_{tp}| = |V_{sd}| \Rightarrow V_{DD} - v_i - |V_{tp}| = V_{DD} - v_o$ and

$$i_{SDp} = \frac{K_p}{2} \left(\frac{W}{L} \right) (V_{DD} - v_o)^2 [1 + \lambda (V_{DD} - v_o)] \quad \text{so we need } v_o \text{ some}$$

$$= i_{DSM}$$

i. need regime of M_n at $v_i = v_o - |V_{tp}| = v_o - V_{tpn}$ or $v_i - V_{tpn} = v_o - 2V_{tpn} < v_o$
 $\equiv V_{gsn} - V_{tpn} < V_{DSn} \Rightarrow M_n \text{ saturation}$

$$= i_{DSM} = \frac{K_n}{2} \left(\frac{W}{L} \right) (v_o - 2V_{tpn})^2 (1 + \lambda v_o)$$

as $\lambda v_o < 10^{-5}$ can ignore, $\Rightarrow i_{SDp} = i_{DSM} \Rightarrow (V_{DD} - v_o)^2 = (v_o - 2V_{tpn})^2$

use $\pm \sqrt{\quad}$ as M_p & M_n are on $\Rightarrow V_{DD} - v_o = v_o - 2V_{tpn} \Rightarrow 2v_o = V_{DD} + 2V_{tpn}$

from $v_i = v_o - |V_{tp}| \Rightarrow v_i = \frac{(V_{DD} + 2V_{tpn})}{2} - V_{tpn} = V_{DD}/2$

$$\Rightarrow v_i = 5V$$

#2. as $v_{DS} = v_{GS} > v_{GS} - V_{TO}$ both M_{n1} & M_{n2} are in saturation with bias current $I_B \Rightarrow$


$$I_B = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS}) \approx \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{TO})^2$$

$$\Rightarrow V_{GS} - V_{TO} = + \sqrt{\frac{I_B}{\frac{K_P \cdot W}{2 \cdot L}}} = \sqrt{\frac{6 \times 10^{-4}}{\frac{3}{2} \times 10^{-4}}} = \sqrt{4} = 2V$$

We need $g_m = \frac{\partial i_{DS}}{\partial v_{GS}} = 2 \frac{I_B}{(V_{GS} - V_{TO})} = \frac{2 \times 0.6 \times 10^{-3}}{2} = 6 \times 10^{-4}$

Here $g_o = \frac{\partial i_{DS}}{\partial v_{DS}} = \frac{I_B}{\lambda} \cdot \frac{1}{(1 + \lambda V_{DS})} \approx 0$

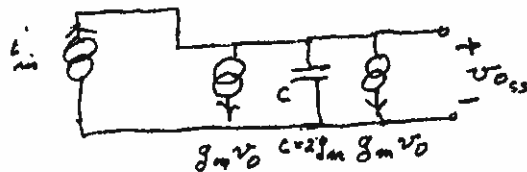The equivalent circuit for small signal i_{in} is



By KCL: $i_{in} = 2g_m v_{oss} + C \frac{dv_{oss}}{dt} = \left(\frac{dv_{oss}}{dt} + v_{oss} \right) 2g_m = 2 \times 10^{-4} \sin t$

$$\Rightarrow \frac{dv_{oss}}{dt} + v_{oss} = \frac{2 \sin t}{2 \times 6} = \frac{1}{6} \sin t$$

to solve:

Let $v_{oss}(t) = A \cos t + B \sin t \Rightarrow \frac{dv}{dt} = -A \sin t + B \cos t$

$$\Rightarrow (-A + B) \sin t + (A + B) \cos t = \frac{1}{6} \sin t \Rightarrow$$

$$A + B = 0 \Rightarrow B = -A \quad \& \quad -A + B = -2A = \frac{1}{6} \Rightarrow A = -\frac{1}{12}, \quad B = \frac{1}{12} = 0.0833$$

$$\Rightarrow v_{oss}(t) = (-\sin t + \cos t) \frac{1}{12}$$

The total $v_o(t)$ includes bias, $V_{o,DC} = V_{GS} = 2 + V_{TO} = 3$

$$\Rightarrow v_o(t) = 3 + \frac{1}{12} (-\sin t + \cos t)$$


3.

a). $i = v(1 + \sin 2\pi v)$, an increasing sin with v .


Key values: @ $v=0$, $i=0$, @ $v=\frac{1}{4}$, $i=\frac{1}{4}(1+1)=\frac{1}{2}$

@ $v=\frac{1}{2}$, $i=\frac{1}{2}(1+0)=\frac{1}{2}$, @ $v=\frac{3}{4}$, $i=\frac{3}{4}(1-1)=0$

@ $v=1$, $i=1(1+0)=1$

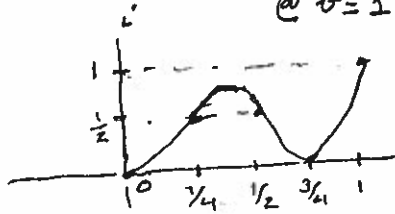

b) $g = \left. \frac{\partial i}{\partial v} \right|_Q = (1 + \sin 2\pi v) + v(2\pi \cos 2\pi v) = 1 + \sin 2\pi v + 2\pi v \cos 2\pi v$

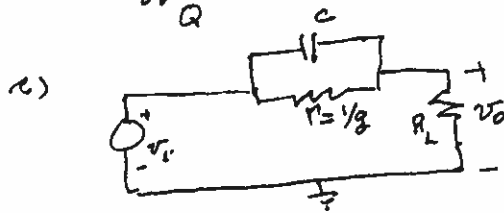

by voltage divider action

$$v_o = \frac{R_L}{R_L + \frac{1}{\frac{1}{3} + \frac{1}{sC}}} v_i = \frac{sC + 3}{4C + (3 + G_L)} v_i$$

$$\Rightarrow T(s) = \frac{s + 3/C}{4 + (3 + G_L)/C}$$

d) if Q point $v_Q = \frac{1}{2} \Rightarrow i_Q = \frac{1}{2} \Rightarrow R_L$ for

$$\frac{-1}{R_L} = \text{slope} = \frac{0 - 1 \text{ amp}}{1 \text{ v} - 0 \text{ v}} = -1$$

$$\Rightarrow R_L = 1 \Omega$$

and $g = 1 + \sin 2\pi \cdot \frac{1}{2} + 2\pi \cdot \frac{1}{2} \cos 2\pi \cdot \frac{1}{2} = 1 - \pi < 0$

$$\therefore T(s) = \frac{s + (1-\pi)/C}{4 + (1-\pi)/C} = \frac{s - 2.14}{s - 1.14}$$

zero at $s = \pi - 1 \Rightarrow$
 pole at $s = \pi - 2 \quad | > 0 \Rightarrow$ unstable \Rightarrow will oscillate between equilibria

