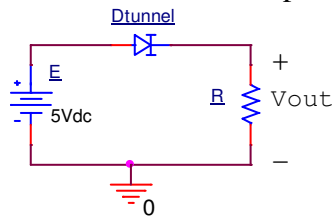


Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

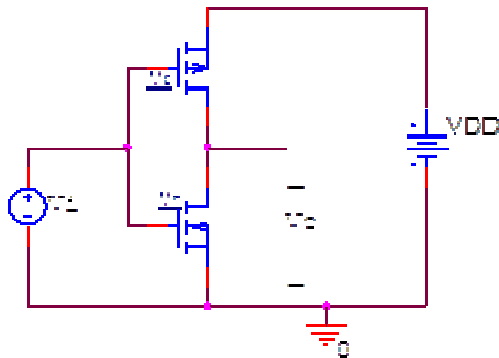3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



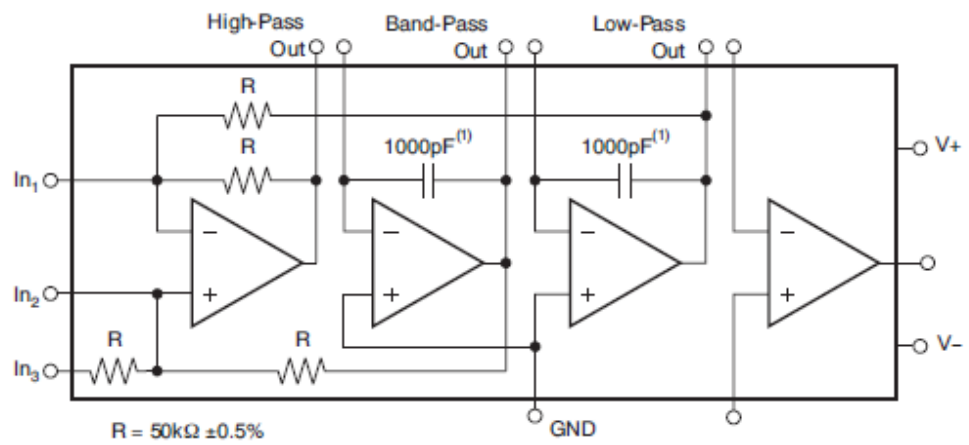


NOTE: (1) $\pm 0.5\%$.

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

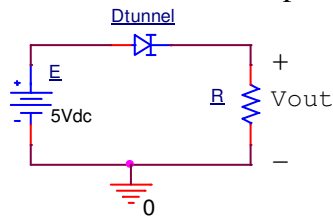1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

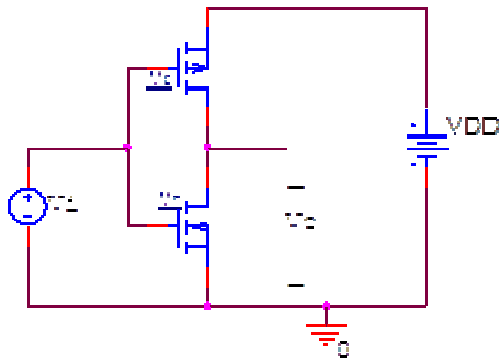3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



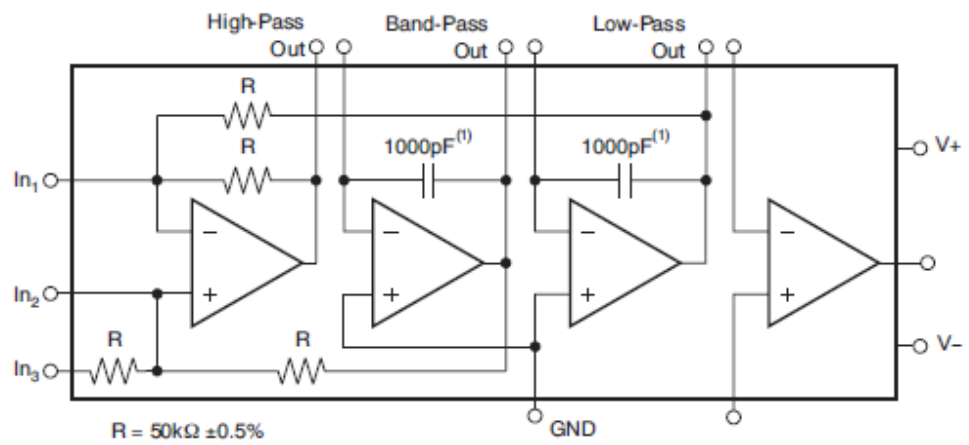


NOTE: (1) $\pm 0.5\%$.

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

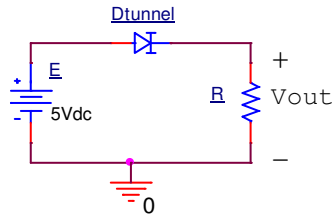1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
 and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

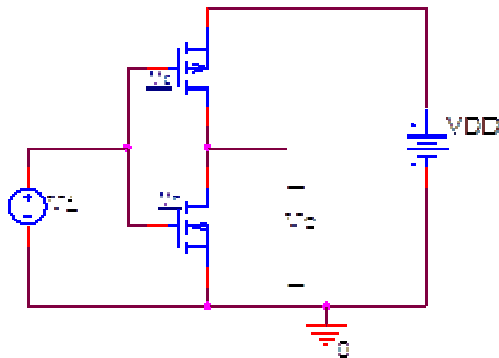3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



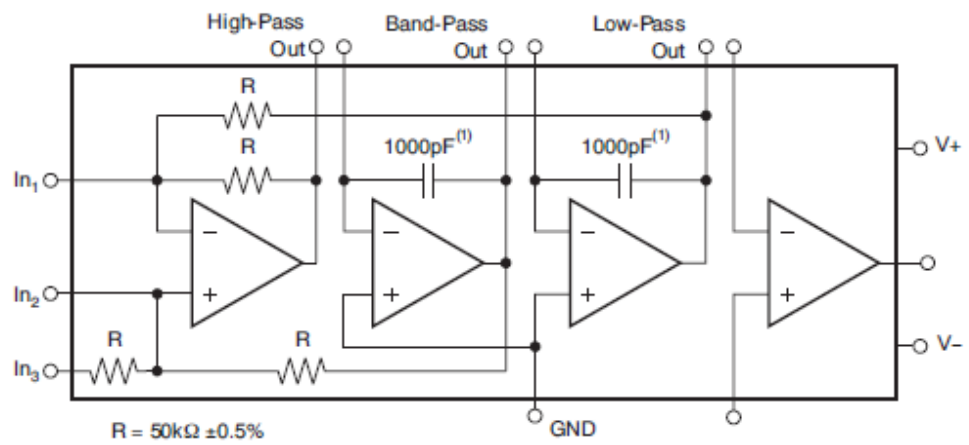


NOTE: (1) $\pm 0.5\%$.

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

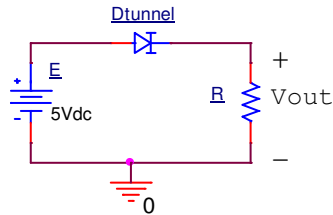1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
 and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

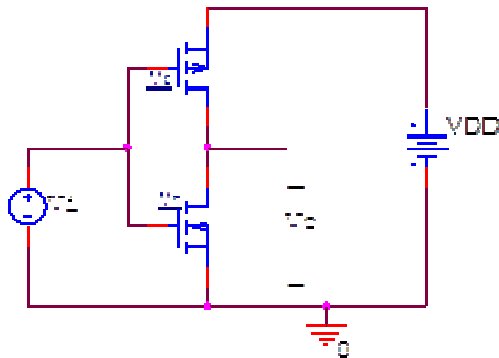3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



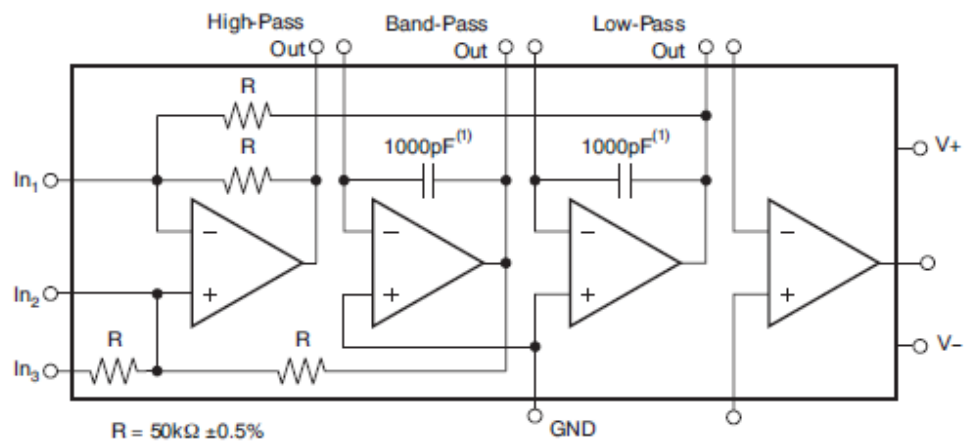


NOTE: (1) $\pm 0.5\%$.

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

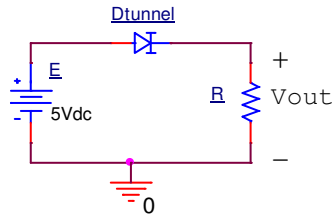1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
 and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

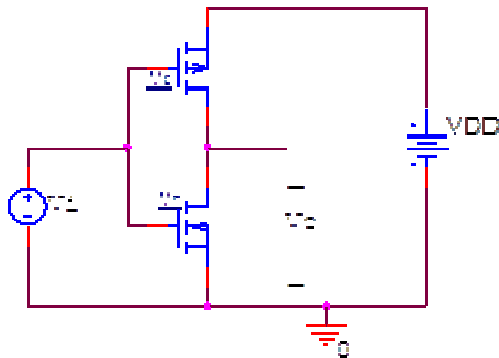3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



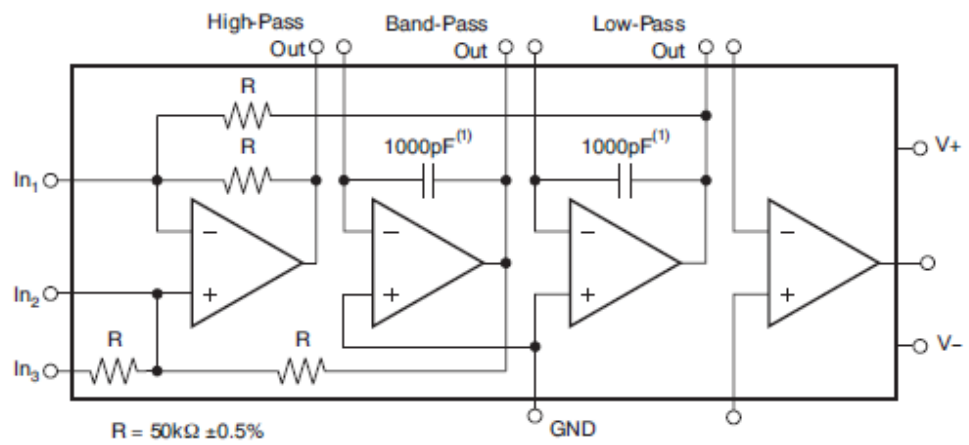


NOTE: (1) $\pm 0.5\%$.

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

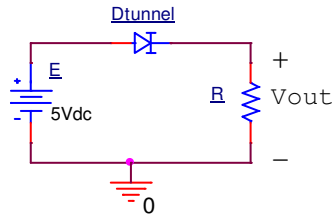1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
 and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

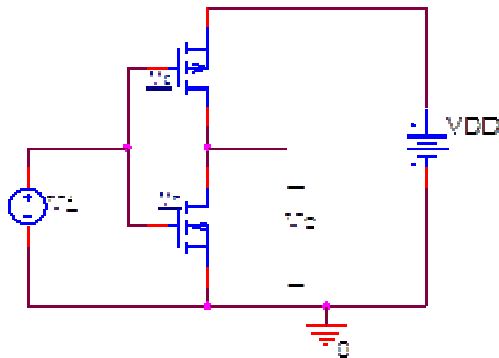3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



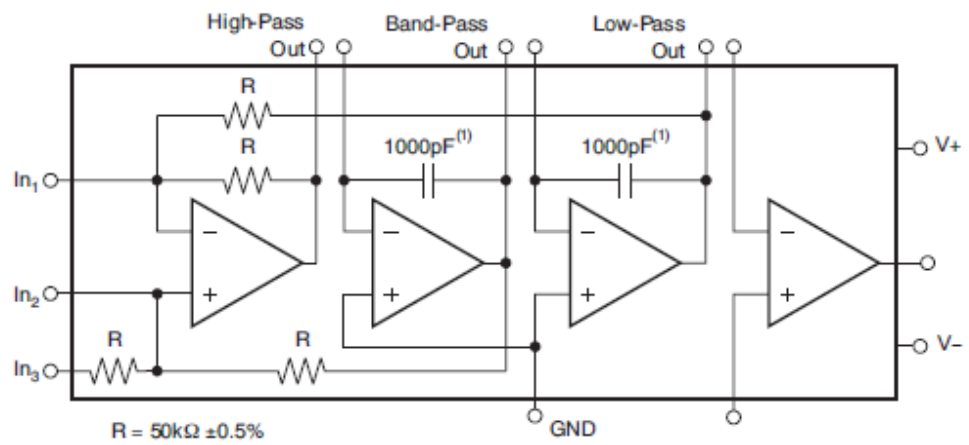


NOTE: (1) $\pm 0.5\%$.

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

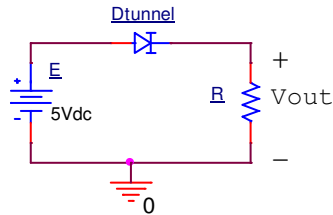1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
 and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

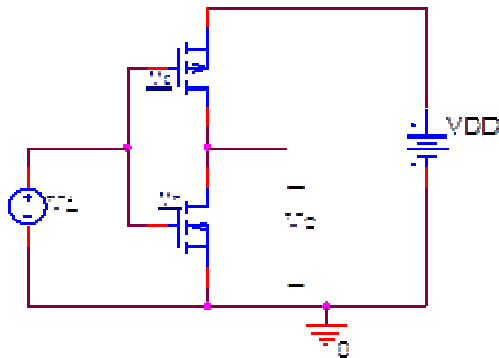3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



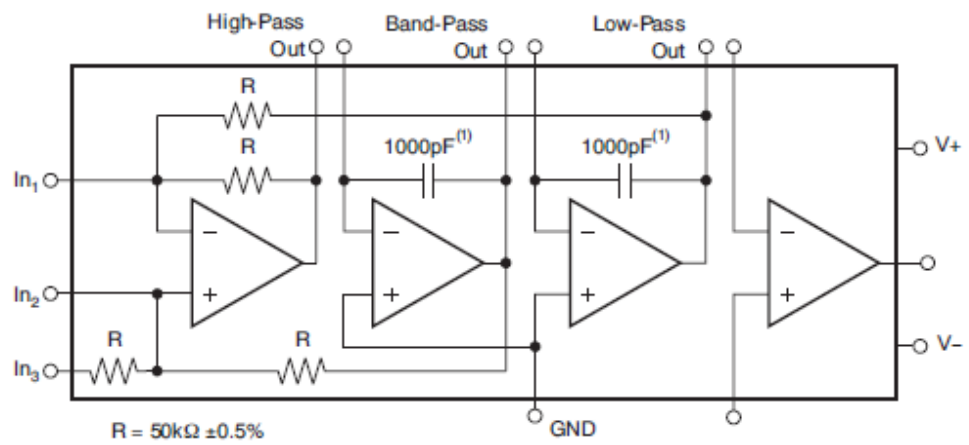


NOTE: (1) $\pm 0.5\%$.

Open book open notes but not open computers; 100 points total (75 minutes); if stuck go on to the next problem. Good luck

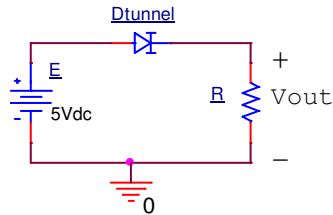1. (30 points, 20 min)

For the following tunnel diode circuit assume the tunnel diode is described by

$$i = [3 + 4(v-0.5)(v-1)(v-1.5)]10^{-3}$$
 and the bias supply voltage is $E=5V$. [i is the current entering the anode and v is the voltage of the anode with respect to the cathode]




- Sketch the diode i vs. v curve with a load line passing through the bias $V=1V$ point.
 - Find the value of the resistance R for the diode bias voltage to be $1V$.
 - Give the bias current.
 - Give the output voltage V_{out} .
 - Find the incremental diode conductance, g_d , at the bias point.
 - If a small voltage, $v_i(t)=0.001\cos(2\pi t)$, is inserted in series with E find the resulting current through the tunnel diode.
2. (30 points, 20 min)


Submit, on the attached page, a TI UAF42 designed for a low pass, inverting pole-pair, filter for the natural frequency of $\omega_n/(2\pi) = f_n=3KHz$, a $Q=100$, and a DC gain of -1 . Use the simplest configuration possible.

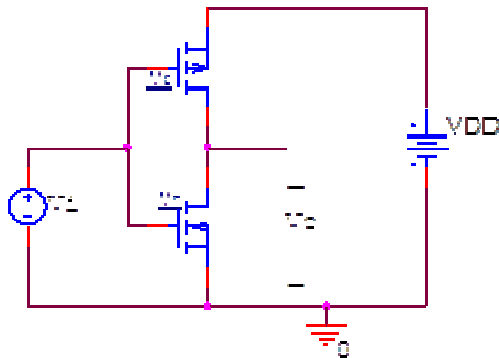3. (40 points, 25 min)

For the following ternary gate, assume M_p and M_n are fully complementary with $LAMBDA=0$, nonzero $C_{gs}=C_{gd}$ and V_{DD} large enough for proper operation.

- Draw the equivalent circuit (sources and capacitors) for the circuit when biased at $V_i = V_{DD}/2$
- When changed at $t=0$ (for all positive time) to $v_i=(1.001)V_{DD}/2$, give the differential equation for $v_o(t)$.



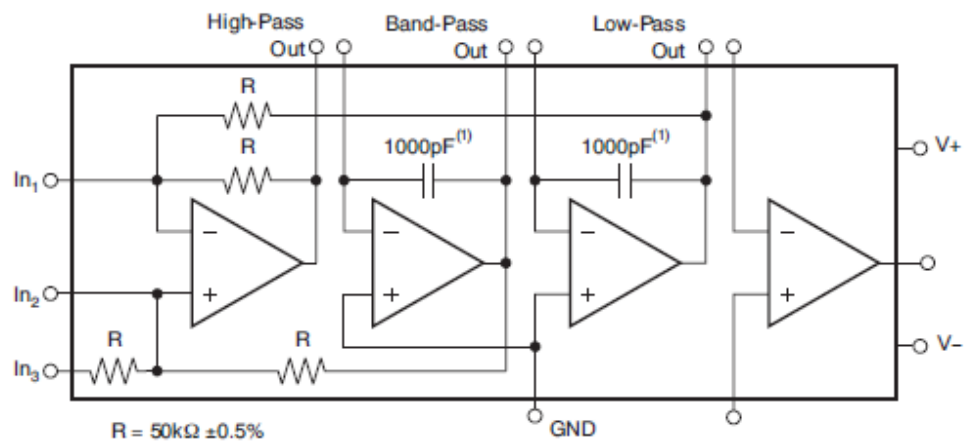

NOTE: (1) $\pm 0.5\%$.