


Homework 2

Question 1


a)

PSpice Schematic

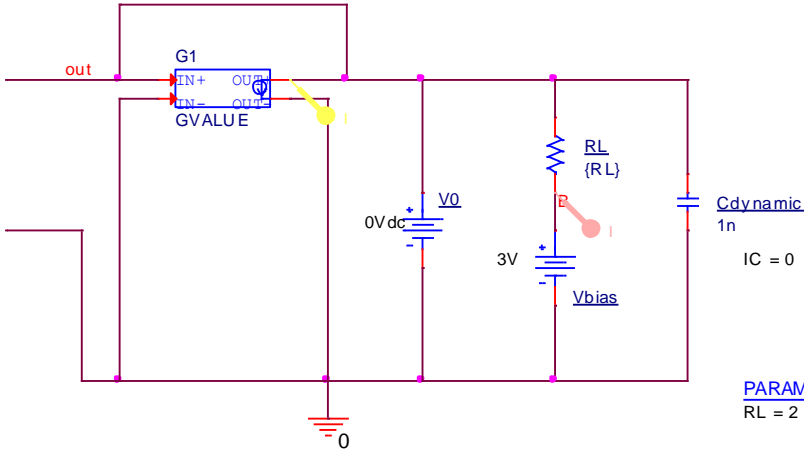
$$\text{SQRT}(27) * V(\%IN+, \%IN-) * (V(\%IN+, \%IN-)-1) * (V(\%IN+, \%IN-)-2)$$



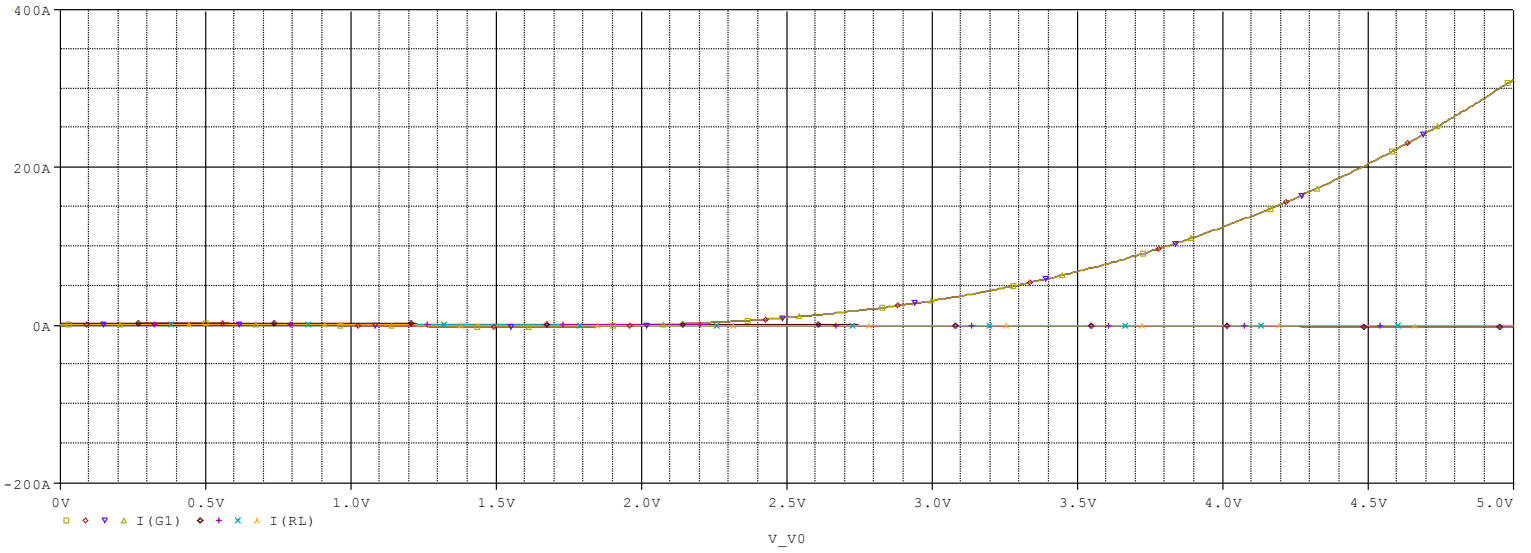Plot of diode current and load line (VO : 0 to 5V)




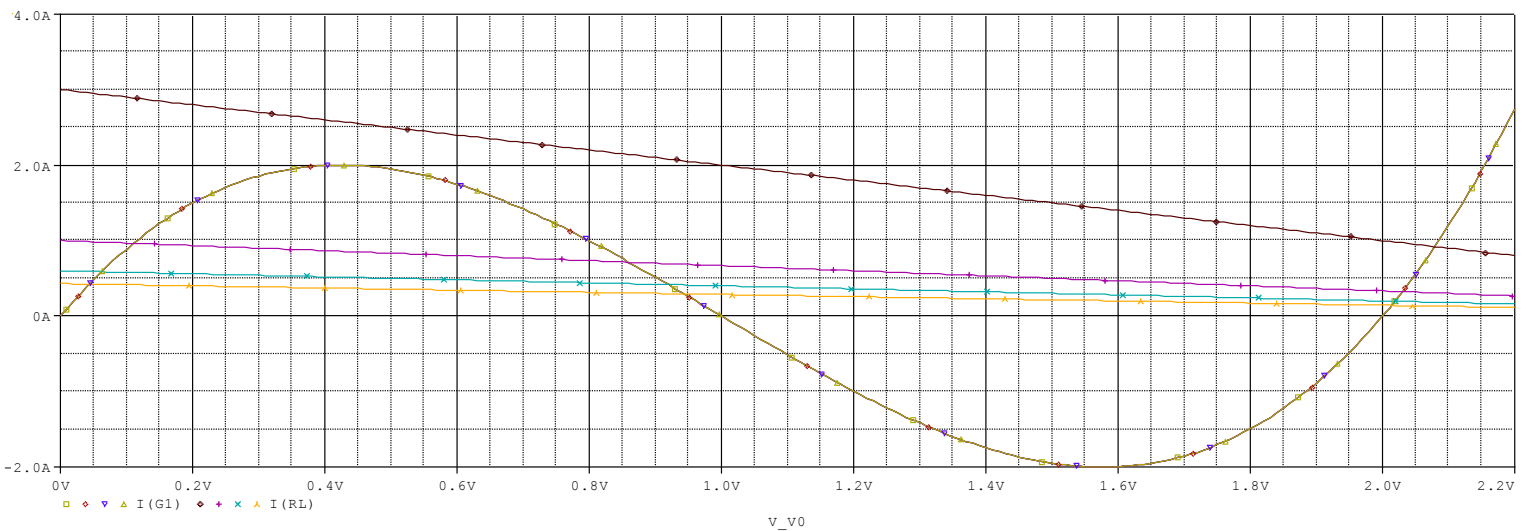Plot of diode current and load line (VO : 0 to 2.2V)




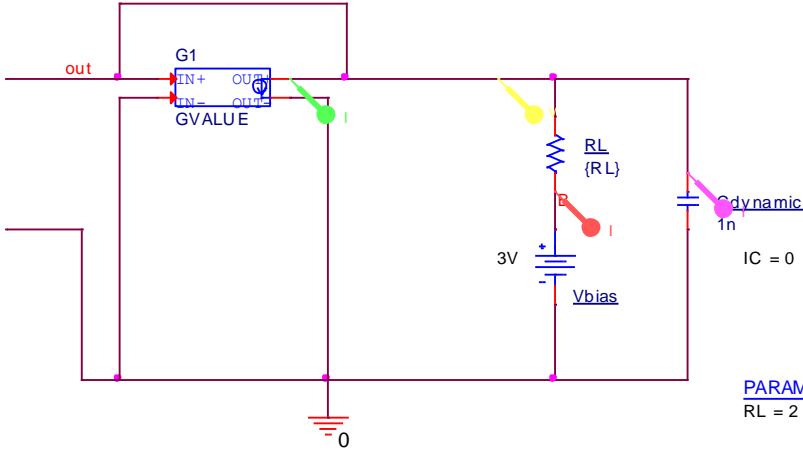b)
Updated schematic with VO removed


$$\text{SQRT}(27) * V(\%IN+, \%IN-) * (V(\%IN+, \%IN-) - 1) * (V(\%IN+, \%IN-) - 2)$$



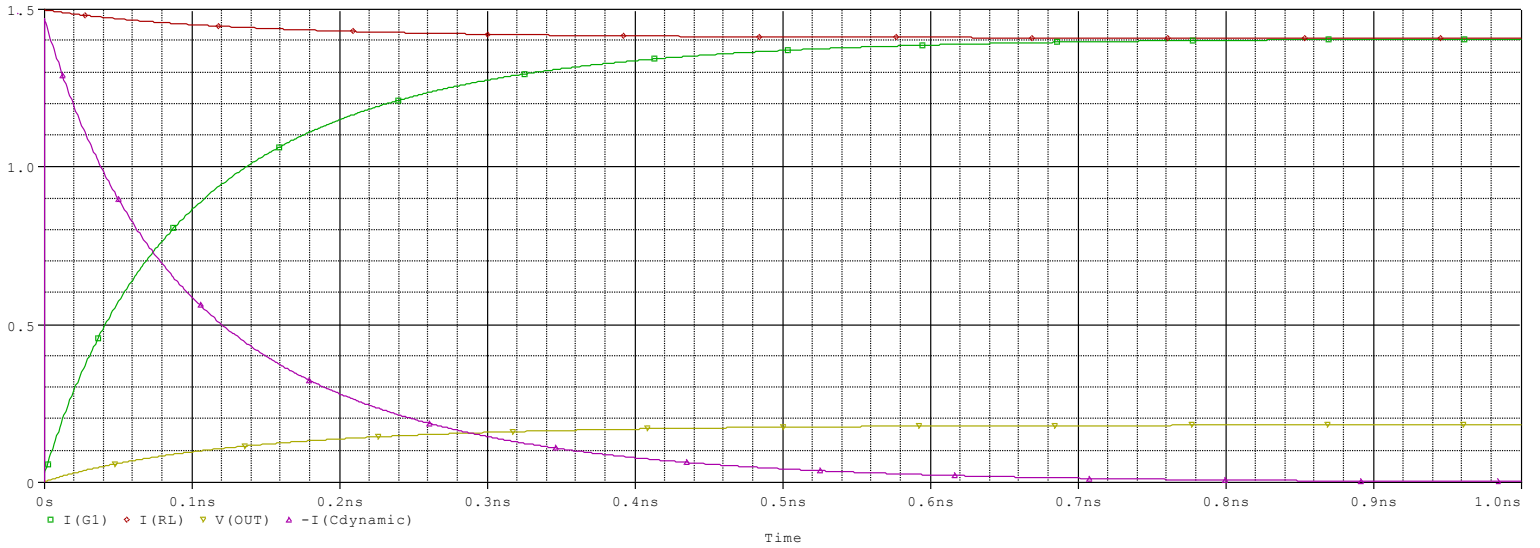Plot of transient run data (I_{RL}, I_C, I_D, V_{Out} vs. Time)




Plot of transient run data (I_C vs. V_{Out})

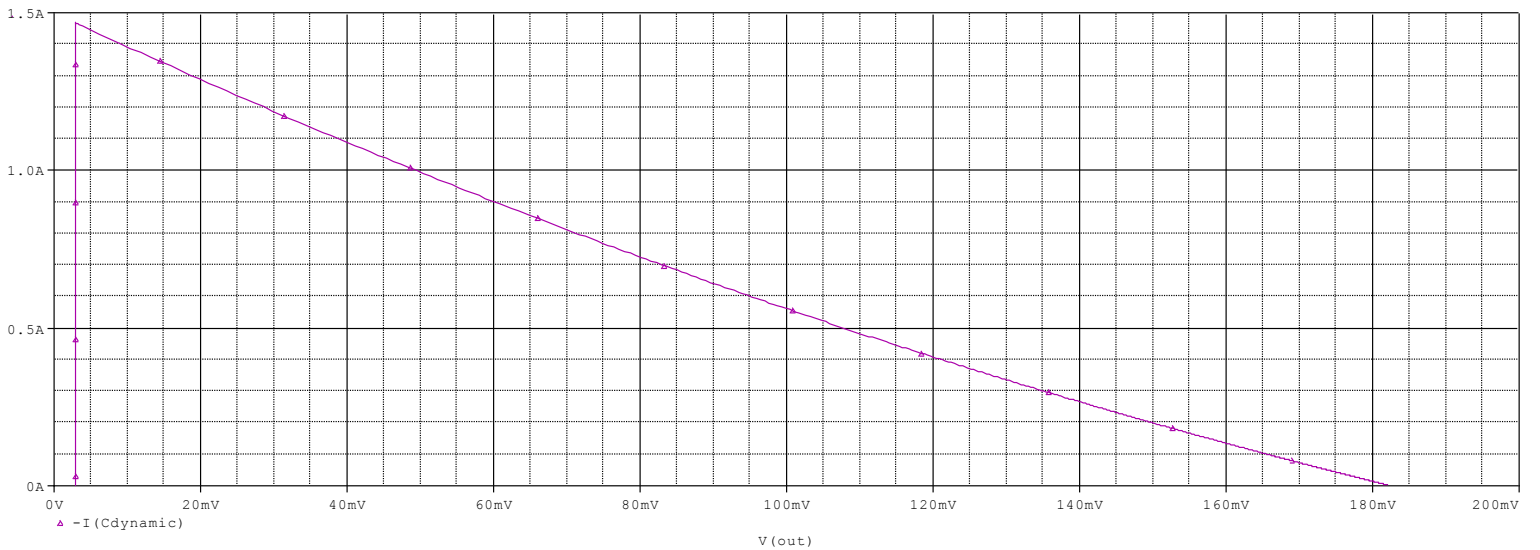


Problem 2


a) Original Circuit

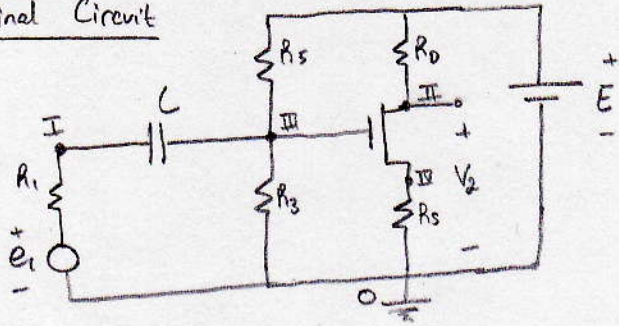

Small-signal equivalent

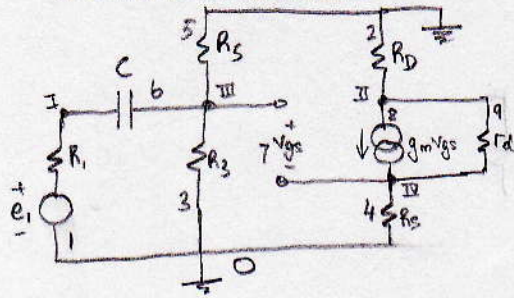

b) Oriented Graph

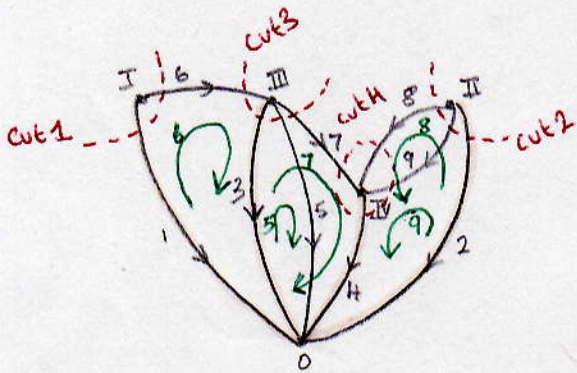

— = tree branches ($b_1 \rightarrow b_{11}$)

c)

KVL

$$\begin{aligned}
 0 &= -V_{b3} + V_{b5} \\
 0 &= -V_{b1} + V_{b3} + V_{b6} \\
 0 &= -V_{b3} + V_{b4} + V_{b7} \\
 0 &= -V_{b2} + V_{b4} + V_{b8} \\
 0 &= -V_{b2} + V_{b4} + V_{b9}
 \end{aligned}$$

KCL

$$\begin{aligned}
 0 &= i_{b1} + i_{b6} \\
 0 &= i_{b2} + i_{b8} + i_{b9} \\
 0 &= i_{b3} + i_{b5} - i_{b6} + i_{b7} \\
 0 &= i_{b4} - i_{b7} - i_{b8} - i_{b9}
 \end{aligned}$$


$$C = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 & 1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & -1 & -1 \end{bmatrix}$$

Cut-set matrix

$$T = \begin{bmatrix} 0 & 0 & -1 & 0 & 1 & 0 & 0 & 0 & 0 \\ -1 & 0 & 1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$


Tie-set matrix

d) Branch admittances

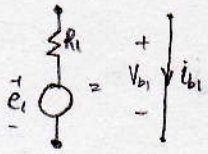


$$i_{b1} = G_1 V_{b1}$$

$$G_1 = \frac{1}{R_1}$$

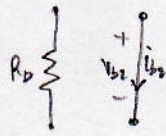


$$i_{b2} = G_2 V_{b2}$$

$$G_2 = \frac{1}{R_2}$$

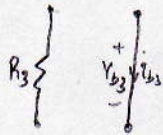


$$i_{b3} = G_3 V_{b3}$$

$$G_3 = \frac{1}{R_3}$$

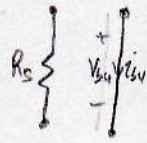


$$i_{b4} = G_4 V_{b4}$$

$$G_4 = \frac{1}{R_4}$$

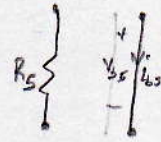


$$i_{b5} = G_5 V_{b5}$$


$$G_5 = \frac{1}{R_5}$$

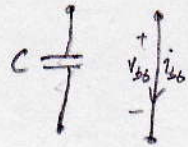

$$i_{b6} = sC V_{b6}$$

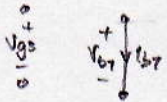

$$i_{b7} = 0$$

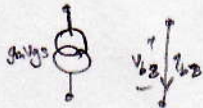

$$i_{b8} = g_m V_{b7}$$



$$i_{b9} = g_d V_{b9}$$

$$g_d = \frac{1}{r_d}$$

$$\begin{bmatrix} i_{b1} \\ i_{b2} \\ i_{b3} \\ i_{b4} \\ i_{b5} \\ i_{b6} \\ i_{b7} \\ i_{b8} \\ i_{b9} \end{bmatrix} = \begin{bmatrix} G_1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & G_2 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & G_3 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & G_4 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & G_5 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & sC & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & g_m & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & g_d \end{bmatrix} \begin{bmatrix} V_{b1} \\ V_{b2} \\ V_{b3} \\ V_{b4} \\ V_{b5} \\ V_{b6} \\ V_{b7} \\ V_{b8} \\ V_{b9} \end{bmatrix}$$

Y_{bxb} = Branch-by-branch admittance matrix.