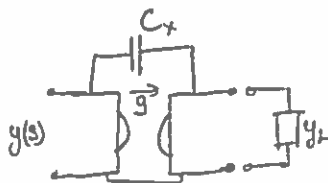


Problem 1

$$y(s) = \frac{as + b}{s + c}$$

From lecture:



$$g^2 = y(k)^2 \quad C_x = \frac{y(k)}{k}$$

→ Choose k such that $E_v\{y(s)\} = 2E_v\{y_L(s)\} = 0$

$$2E_v\{y(s)\} = \frac{as+b}{s+c} + \frac{b-as}{c-s} = \frac{2bc - 2as^2}{c^2 - s^2} = 0$$

$$\Rightarrow as^2 = bc$$

$$\Rightarrow s = k = \sqrt{\frac{bc}{a}} \quad \therefore y(k) = \frac{\sqrt{abc} + b}{\sqrt{\frac{bc}{a}} + c}$$

→ From Richards function:


$$y_L(s) = y(k) \frac{sy(s) - ky(k)}{sy(k) - ky(s)} \implies \text{simplify using } k, y(k) \implies \boxed{y_L(s) = a}$$

→ Find g, C_x :

$$g^2 = y(k)^2 = \left(\frac{\sqrt{abc} + b}{\sqrt{\frac{bc}{a}} + c} \right)^2 = \frac{ab}{c} \implies \boxed{g = \sqrt{\frac{ab}{c}}}$$

$$C_x = \frac{y(k)}{k} = \frac{\sqrt{abc} + b}{\sqrt{\frac{bc}{a}} + c} \times \frac{1}{\sqrt{\frac{bc}{a}}} \implies \boxed{C_x = \frac{a}{c}}$$

Resulting circuit:

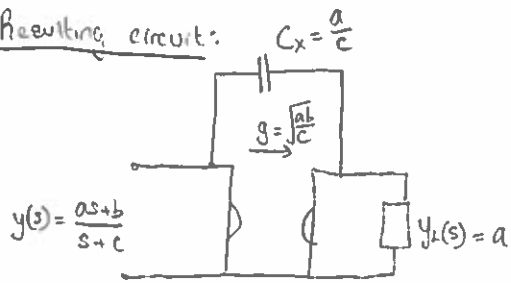

• if $a=0$, $g=0$, $Y_L=0$, $C_x=0$

→ no current at the ports so we get an open circuit

• if $c=0$, $g=\infty$, $C_x=\infty$

→ the upper output terminals are shorted ($Z_C = \frac{1}{\infty} = 0$) and with $g \rightarrow \infty$, the entire device is shorted to bottom terminal


• if $a=-b=c=-1$, $g=1$, $Y_L=-1$, $C_x=1$

→ the load and device is a negative resistor

• if $a=-b=-c=-1$, $g=\sqrt{-1}$, $Y_L=-1$, $C_x=-1$

→ we get both a negative capacitor and resistor with ϕ now introducing a phase shift

Problem 2

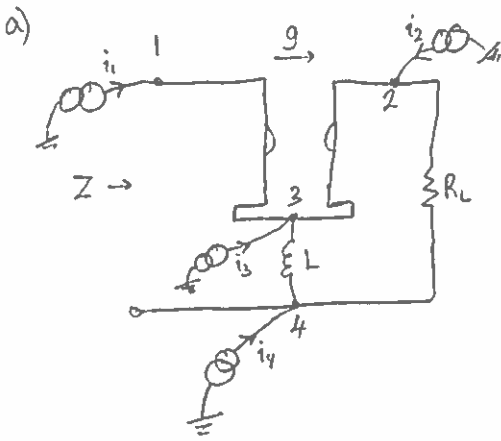

Writing current equations:

$$\left. \begin{aligned} i_1 &= g(v_2 - v_3) \\ i_2 &= -g(v_1 - v_3) + G_L(v_2 - v_4) \\ i_3 &= -g(v_2 - v_3) + g(v_1 - v_3) + \frac{1}{sL}(v_3 - v_4) \end{aligned} \right\} i = Y_{\text{indef}} v$$

$G_L = 1/R_L$

From these equations write indefinite admittance matrix

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & g & -g & 0 \\ -g & G_L & g & -G_L \\ g & -g & Y_{sL} & -\frac{1}{sL} \\ 0 & -G_L & \frac{1}{sL} & G_L + \frac{1}{sL} \end{bmatrix}}_{Y_{\text{indef}}} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$

last row obtained from
sum along columns = 0

b) Grounding node 4:

$$\therefore Y_{\text{indef}} = \begin{bmatrix} 0 & g & -g \\ -g & G_L & g \\ g & -g & Y_{sL} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

Eliminate node 3:


$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} \Rightarrow i_3 = Y_{21} v_1 + Y_{22} v_3 = 0 \Rightarrow v_3 = -Y_{22}^{-1} Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y_{11} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_{12} v_3 = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}}_{Y_2} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow Y_2 = \begin{bmatrix} 0 & g \\ -g & G_L \end{bmatrix} - \begin{bmatrix} -g \\ g \end{bmatrix} sL \begin{bmatrix} g & -g \end{bmatrix} = \begin{bmatrix} sLg^2 & g - sLg^2 \\ -g - sLg^2 & G_L + sLg^2 \end{bmatrix}$$

Eliminate node 2:

Similarly: $i_1 = Y_{11} v_1 + Y_{12} v_2 = (Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}) v_1 = \left[sLg^2 - (g - sLg^2) \frac{1}{G_L + sLg^2} (-g - sLg^2) \right] v_1$
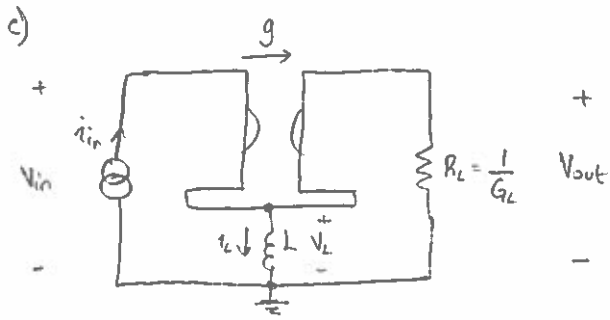
$$\Rightarrow y(s) = \frac{i_1}{v_1} = \frac{g^2(1 + sL G_L)}{G_L + sL g^2}$$



KCL/KVL Equations

$$\left. \begin{aligned} i_{in} &= g(v_{out} - v_L) \\ i_L &= i_{in} - g(v_{in} - v_L) = i_{in} - \frac{v_{out}}{R_L} \\ v_L &= L \frac{di_L}{dt} \end{aligned} \right\} \begin{aligned} v_L &= v_{out} - \frac{1}{g} i_{in} \\ v_{out} &= (i_{in} - i_L) R_L \end{aligned}$$

$$L \frac{di_L}{dt} = v_{out} - \frac{1}{g} i_{in} = (i_{in} - i_L) R_L - \frac{1}{g} i_{in} = -R_L i_L + \left(R_L - \frac{1}{g}\right) i_{in}$$

$$\Rightarrow \frac{di_L}{dt} = \frac{-R_L}{L} i_L + \frac{1}{L} \left(R_L - \frac{1}{g}\right) i_{in} \Rightarrow \dot{x} = Ax + Bu \quad \left. \begin{aligned} A &= \frac{-R_L}{L} & B &= \frac{1}{L} \left(R_L - \frac{1}{g}\right) \\ C &= -R_L & D &= R_L \end{aligned} \right\}$$

$$v_{out} = -i_L R_L + R_L i_{in} \Rightarrow y = Cx + Du$$

$$\frac{v_{out}}{i_{in}} = T(s) = C(s - A)^{-1} B + D$$

$$= -R_L \left(\frac{1}{s + R_L/L} \right) \frac{1}{L} \left(R_L - \frac{1}{g}\right) + R_L$$

$$T(s) = \frac{R_L \left(\frac{1}{g} + sL \right)}{sL + R_L}$$