

Homework 5Problem 1

$$\frac{d^3 z}{dt^3} + 5 \frac{d^2 z}{dt^2} + 6 \frac{dz}{dt} + 7z = 3V \quad i = 2V - 3 \frac{dz}{dt}$$

i)

Let  $z_1 = z$

$z_2 = \dot{z}_1 = \dot{z}$

$z_3 = \dot{z}_2 = \ddot{z} = \ddot{z}$

$z_4 = \dot{z}_3 = \ddot{z}_2 = \dot{z}_3 = \ddot{z}_3 = -5\ddot{z}_3 - 6\dot{z}_3 - 7z_3 + 3V$

$$\Rightarrow \begin{bmatrix} \dot{z}_1 \\ \dot{z}_2 \\ \dot{z}_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -7 & -6 & -5 \end{bmatrix} \begin{bmatrix} z_1 \\ z_2 \\ z_3 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 3 \end{bmatrix} V$$

$$i = \begin{bmatrix} 0 & -3 & 0 \end{bmatrix} \begin{bmatrix} z_1 \\ z_2 \\ z_3 \end{bmatrix} + 2V$$

b) The state variable equations are of the form:

$$\left. \begin{aligned} \dot{z} &= AZ + BU \\ y &= CZ + DU \end{aligned} \right\} \begin{aligned} y &= i(s) = \text{output} \\ u &= V(s) = \text{input} \end{aligned}$$


$$\begin{aligned} \therefore \frac{i(s)}{V(s)} = \frac{y}{u} = T(s) &= C(sI_3 - A)^{-1}B + D \\ &= \begin{bmatrix} 0 & -3 & 0 \end{bmatrix} \begin{bmatrix} s & -1 & 0 \\ 0 & s & -1 \\ 7 & 6 & 5 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 0 \\ 3 \end{bmatrix} + 2 \end{aligned}$$

$$\frac{i(s)}{V(s)} = T(s) = \frac{2s^3 + 10s^2 + 3s + 14}{s^3 + 5s^2 + 6s + 7}$$

Zeros:

$$2s^3 + 10s^2 + 3s + 14 = 0 \quad \Rightarrow \quad s = -4.981, -0.095 + 1.1854i, -0.095 - 1.1854i$$

c) Constant coupling admittance matrix

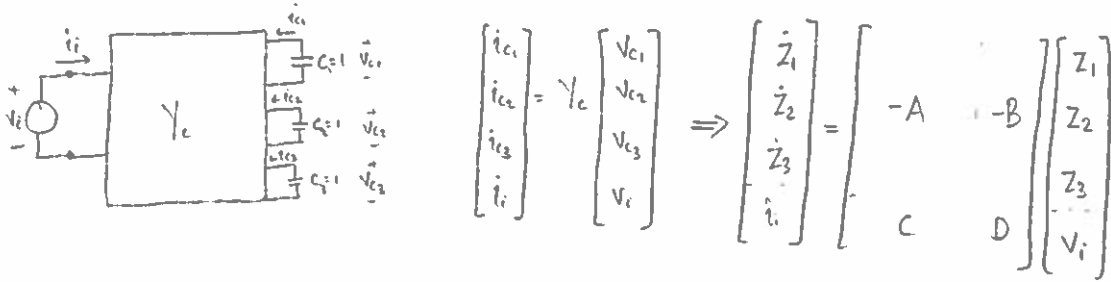

$$\therefore Y_c = \begin{bmatrix} 0 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 \\ 7 & 6 & 5 & -3 \\ 0 & -3 & 0 & 2 \end{bmatrix}$$

## Problem 2


a) The degree 4 transfer function will be of the form:

$$T(s) = \frac{A}{(s-s_0)(s-s_1)(s-s_2)(s-s_3)}$$

Poles are found as:

$$s = e^{j\left[\frac{2k+1}{2}\pi + \frac{2k+1}{2n}\pi\right]} = e^{j(2k+1)\frac{5\pi}{8}} \quad n=4$$

k	$s_k$
0	$e^{j5\pi/8}$
1	$e^{j15\pi/8} = -j^{1/2}e$
-1	$e^{-j5\pi/8}$
2	$e^{j25\pi/8} = e^{j9\pi/8}$
-2	$e^{-j15\pi/8} = j^{1/2}e$
3	$e^{j35\pi/8} = e^{j3\pi/8}$
-3	$e^{-j25\pi/8} = e^{-j\pi/8}$
4	$e^{j45\pi/8} = e^{j\pi/8}$

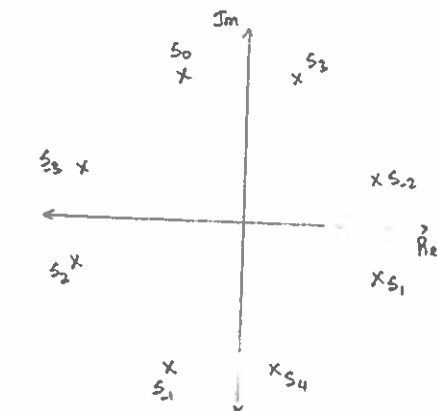

Choose poles in LHP

$$\therefore \text{poles: } s_0 = e^{j\frac{5\pi}{8}} \quad s_1 = e^{-j\frac{5\pi}{8}} \quad s_2 = e^{j\frac{\pi}{8}} \quad s_3 = e^{-j\frac{\pi}{8}}$$

$$\therefore T(s) = \frac{1}{(s - e^{j\frac{5\pi}{8}})(s - e^{-j\frac{5\pi}{8}})(s - e^{j\frac{\pi}{8}})(s - e^{-j\frac{\pi}{8}})}$$

b) Poles:  $s_0 = e^{j\frac{5\pi}{8}} \quad s_1 = e^{-j\frac{5\pi}{8}} \quad s_2 = e^{j\frac{\pi}{8}} \quad s_3 = e^{-j\frac{\pi}{8}}$  Zeros:  $\pm \infty$

c)  $\omega_c = 2\pi f_c = 4000\pi \text{ rad/s}^1$

$$\therefore \text{Denormalized } T(s) \Rightarrow T_{dn}(s) = \frac{15}{\left(\frac{s}{4000\pi} - e^{j\frac{5\pi}{8}}\right)\left(\frac{s}{4000\pi} - e^{-j\frac{5\pi}{8}}\right)\left(\frac{s}{4000\pi} - e^{j\frac{\pi}{8}}\right)\left(\frac{s}{4000\pi} - e^{-j\frac{\pi}{8}}\right)}$$

Poles are scaled:  $s = 4000\pi e^{j\frac{5\pi}{8}}, 4000\pi e^{-j\frac{5\pi}{8}}, 4000\pi e^{j\frac{\pi}{8}}, 4000\pi e^{-j\frac{\pi}{8}}$

Zeros:  $\pm \infty$

b) Expanding out  $T(s)$  from part (a), we obtain:

$$T(s) = \frac{1}{(s^2 + 0.76548s + 1)(s^2 + 1.8478s + 1)}$$

To make a bandpass filter,  $s \rightarrow 2p + \frac{1}{2p}$

$$\begin{aligned} \therefore T_{bp}(p) &= \frac{1}{\left[ \left( 2p + \frac{1}{2p} \right)^2 + 0.7654 \left( 2p + \frac{1}{2p} \right) + 1 \right] \left[ \left( 2p + \frac{1}{2p} \right)^2 + 1.8478 \left( 2p + \frac{1}{2p} \right) + 1 \right]} \\ &= \frac{16p^4}{(16p^4 + 6.123p^3 + 12p^2 + 1.531p + 1)(16p^4 + 14.782p^3 + 12p^2 + 3.696p + 1)} \end{aligned}$$

Zeros: Four repeated  $p=0$

Poles:  $(16p^4 + 6.123p^3 + 12p^2 + 1.531p + 1)(16p^4 + 14.782p^3 + 12p^2 + 3.696p + 1) = 0$

$$\Rightarrow p = \begin{cases} -0.2794 \pm 0.5519i \\ -0.1825 \pm 0.3606i \\ -0.1363 \pm 0.7749i \\ -0.0550 \pm 0.3129i \end{cases}$$

By making the conversion from low pass to band pass, capacitors and inductors in the circuit would need to be modified to reflect the high pass component e.g. a capacitor may need to be replaced with a parallel network of  $L_s$  and  $C_s$  and inductors with a series network of  $L_s$  and  $C_s$ . If OTAs are involved we may now need cascaded OTAs to get the band pass component.