

Problem 1

a) Synthesize  $y(s) = \frac{5s^3 + 21s}{s^4 + 8s^2 + 15}$

1<sup>st</sup> Foster

$$Z(s) = \frac{(s^2+3)(s^2+5)}{s(5s^2+21)} = \frac{k_0}{s} + k_\infty s + \frac{2k_2 s}{5s^2+21}$$


$$Z(s) s(5s^2+21) = k_0(5s^2+21) + k_\infty s^2(5s^2+21) + 2k_2 s^2 = (s^2+3)(s^2+5) = F(s)$$

$$F(s) \Big|_{s=0} \Rightarrow 21k_0 = 15 \Rightarrow k_0 = \frac{5}{7}$$

$$F(s) \Big|_{s=-\frac{21}{5}} \Rightarrow 2k_2 \left(\frac{-21}{5}\right) = \frac{-24}{25} \Rightarrow 2k_2 = \frac{8}{35}$$

$$k_\infty = \frac{(s^2+3)(s^2+5) - 2k_2 s^2 - k_0(5s^2+21)}{s^2(5s^2+21)} \Big|_{s=\infty} \Rightarrow k_\infty = \frac{1}{5}$$
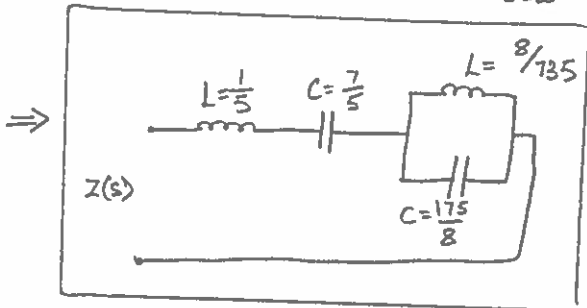
$$\left. \begin{aligned} Z(s) &= \frac{5}{7s} + \frac{1}{5}s + \frac{8/35 s}{5s^2+21} \\ &= \frac{5}{7s} + \frac{1}{5}s + \frac{1}{\frac{175}{8}s + \frac{735}{8s}} \end{aligned} \right\}$$



2<sup>nd</sup> Foster.

$$y(s) = \frac{s(5s^2+21s)}{(s^2+3)(s^2+5)} = \frac{k_0}{s} + k_\infty s + \frac{2k_2 s}{s^2+3} + \frac{2k_4 s}{s^2+5}$$

$$y(s)(s^2+3)(s^2+5)s = k_0(s^2+3)(s^2+5) + k_\infty s^2(s^2+3)(s^2+5) + 2k_2 s^2(s^2+5) + 2k_4 s^2(s^2+3) = s^2(5s^2+21) = F(s)$$


$$F(s) \Big|_{s=0} \Rightarrow k_0 = 0$$

$$\text{Solve for } k_\infty \Big|_{s=\infty} \Rightarrow k_\infty = 0$$

$$F(s) \Big|_{s^2=-5} \Rightarrow 2k_4 = 2$$

$$F(s) \Big|_{s^2=-3} \Rightarrow 2k_2 = 2$$
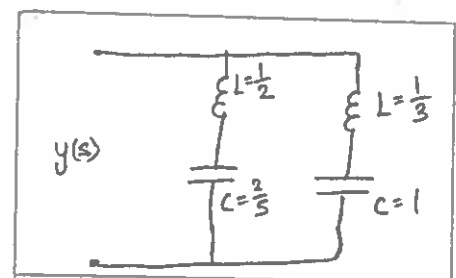
$$\left. \begin{aligned} y(s) &= \frac{3s}{s^2+3} + \frac{2s}{s^2+5} \\ &= \frac{1}{\frac{1}{3}s + \frac{1}{s}} + \frac{1}{\frac{1}{2}s + \frac{5}{2s}} \end{aligned} \right\}$$




1<sup>st</sup> Case

$$y(s) = \frac{5s^3 + 21s}{s^4 + 8s^2 + 15} \quad Z(s) = \frac{s^4 + 8s^2 + 15}{5s^3 + 21s}$$

$$\begin{array}{r} \frac{1}{5}s \\ \hline 5s^3 + 21s \overline{) s^4 + 8s^2 + 15} \\ \underline{s^4 + \frac{21}{5}s^2} \phantom{+ 15} \\ \phantom{s^4 +} \frac{25}{19}s^2 + 15 \\ \phantom{s^4 +} \frac{19}{5}s^2 + 15 \\ \hline \phantom{s^4 +} \frac{25}{19}s^2 + 21s \\ \phantom{s^4 +} \frac{361}{19}s \\ \phantom{s^4 +} \frac{24}{19}s \\ \phantom{s^4 +} \frac{19}{5}s^2 + 15 \\ \hline \phantom{s^4 +} \frac{19}{5}s^2 \\ \phantom{s^4 +} 15 \\ \phantom{s^4 +} \frac{8}{9}s \\ \phantom{s^4 +} \frac{24}{19}s \\ \phantom{s^4 +} \frac{24}{19}s \\ \hline \phantom{s^4 +} 0 \end{array}$$
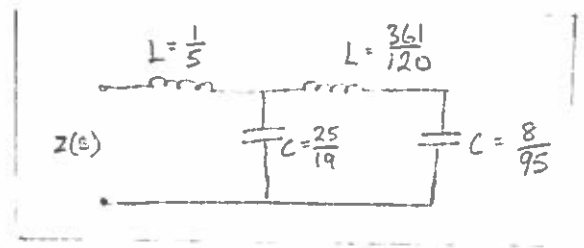
$$Z(s) = \frac{1}{5}s + \frac{1}{\frac{25}{19}s + \frac{361}{120} + \frac{1}{\frac{8}{95}s}}$$




2<sup>nd</sup> Case

$$Z(s) = \frac{15 + 8s^2 + s^4}{21s + 5s^3}$$

$$\begin{array}{r} \frac{15}{21s} \\ \hline 21s + 5s^3 \overline{) 15 + 8s^2 + s^4} \\ \underline{15 + \frac{75}{21}s^2} \phantom{+ s^4} \\ \phantom{15 +} \frac{31}{7}s^2 + s^4 \\ \phantom{15 +} \frac{147}{31}s^3 \\ \phantom{15 +} \frac{961}{56s} \\ \phantom{15 +} \frac{8}{21}s^3 \\ \phantom{15 +} \frac{31}{7}s^2 + s^4 \\ \hline \phantom{15 +} \frac{31}{7}s^2 \\ \phantom{15 +} \frac{8}{31}s^3 \\ \phantom{15 +} \frac{8}{31}s^3 \\ \hline \phantom{15 +} 0 \end{array}$$
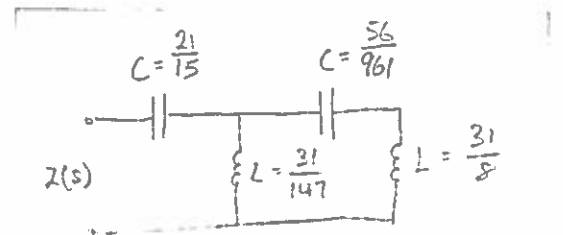
$$Z(s) = \frac{15}{21s} + \frac{1}{\frac{147}{31s} + \frac{961}{56s} + \frac{1}{\frac{8}{31}s}}$$




b) Synthesize  $Z(s) = \frac{5s^3 + 21s}{s^4 + 8s^2 + 15}$

1<sup>st</sup> Foster

Since  $Z(s)$  of (b) is equal to  $y(s)$  of (a), we can use previously derived result

$\Rightarrow$  from 2<sup>nd</sup> Foster of (a):

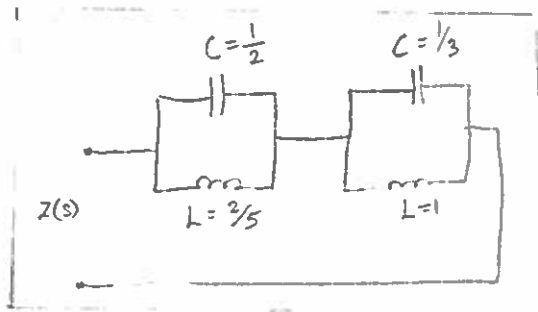
$$Z(s) = \frac{1}{\frac{1}{3}s + \frac{1}{s}} + \frac{1}{\frac{1}{2}s + \frac{5}{2s}}$$



2<sup>nd</sup> Foster

$\Rightarrow$  from 1<sup>st</sup> Foster of (a):

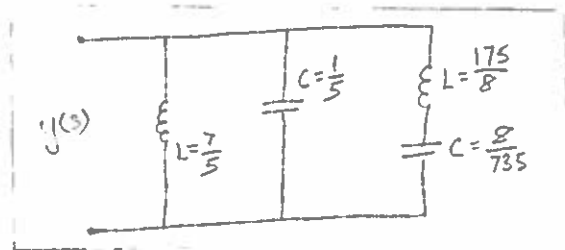
$$y(s) = \frac{5}{7s} + \frac{1}{5}s + \frac{1}{\frac{175}{8}s + \frac{735}{8s}}$$



1<sup>st</sup> Cauer

$\Rightarrow$  from 1<sup>st</sup> Cauer of (a):

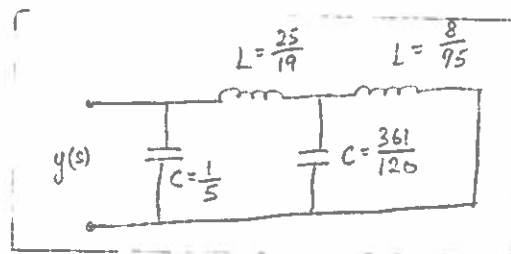
$$y(s) = \frac{1}{5}s + \frac{1}{\frac{25}{19}s + \frac{1}{\frac{361}{120}s + \frac{1}{\frac{8}{95}s}}}}$$



2<sup>nd</sup> Cauer

$\Rightarrow$  from 2<sup>nd</sup> Cauer of (a):
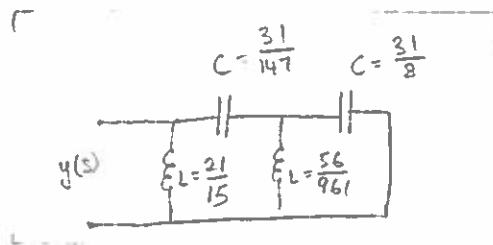
$$y(s) = \frac{15}{21s} + \frac{1}{\frac{147}{31s} + \frac{1}{\frac{961}{56s} + \frac{1}{\frac{8}{31s}}}}$$



## Comparison of (a), (b)

Since  $Z(s)$  of (a) and (b) are inverses of each other, the forms of the synthesized circuits are similar.  $C$  and  $L$  values are interchanged between the two admittances and series/parallel connections have been inverted as well

c) Synthesize  $Y(s) = \frac{5s}{s^2+7}$  using Richards extractions at  $k=1, -1$


$$Y_R(s) = \frac{sY(s) - kY(k)}{sY(k) - kY(s)} \Rightarrow Z_R(s) = \frac{kZ(s) - sZ(k)}{kZ(k) - sZ(s)} \Rightarrow Z(s) = \frac{1}{\frac{1}{Z_R(s)Z(k)} + \frac{s}{kZ(k)}} + \frac{1}{\frac{k}{sZ(k)} + \frac{Z_R(s)}{Z(k)}}$$

[Richards in  $Y$ ]
[Richards in  $Z$ ]
[Solve for  $Z(s)$ ]

$k=1$

$$Z(s) = \frac{s^2+7}{5s} \quad Z(s=k=1) = \frac{8}{5} \Rightarrow Z_R(s) = \frac{\frac{s^2+7}{5s} - s \frac{8}{5}}{\frac{8}{5} - s \frac{(s^2+7)}{5s}} = \frac{7}{s}$$


$$\therefore Z(s) = \frac{1}{\frac{1}{\left(\frac{7}{s}\right) \frac{8}{5}} + \frac{s}{\frac{8}{5}}} + \frac{1}{\frac{1}{s \frac{8}{5}} + \frac{7/s}{8/5}} = \frac{7}{5s} + \frac{1}{5}s$$

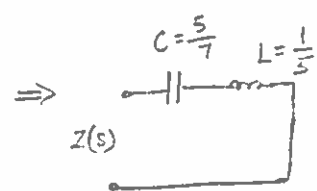$\Rightarrow$  

d)  $k=-1$

$$Z(s=k=-1) = \frac{-8}{5} \quad Z_R(s) = \frac{-\frac{s^2+7}{5s} + s \frac{8}{5}}{\frac{8}{5} - s \frac{(s^2+7)}{5s}} = \frac{-7}{s}$$


$$\therefore Z(s) = \frac{1}{\frac{1}{\left(\frac{-7}{s}\right) \left(\frac{-8}{5}\right)} + \frac{s}{(-1) \left(\frac{-8}{5}\right)}} + \frac{1}{\frac{-1}{-s \frac{8}{5}} + \frac{-7/s}{-8/5}} = \frac{7}{5s} + \frac{1}{5}s$$

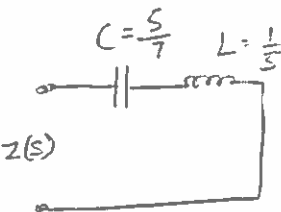$\Rightarrow$  

Extractions at  $k=1$  and  $k=-1$  yield the same result

Alternative for 1c, 1d

c)  $y(s) = \frac{5s}{s^2+7}$

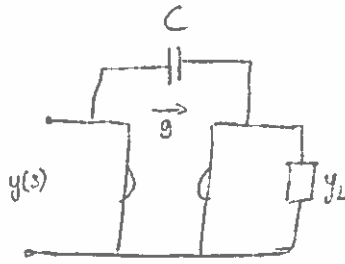

$$C = \frac{y(k)}{k} \quad g^2 = y(k)^2$$


$k=1$

$$y_L = y(k) \left[ \frac{s y(s) - k y(k)}{s y(k) - k y(s)} \right] = \frac{5}{8} \frac{s \frac{5s}{s^2+7} - \frac{5}{8}}{s \frac{5}{8} - \frac{5s}{s^2+7}} = \frac{35}{8s} \Rightarrow Z_L = \frac{8}{35} s = sL$$

$$y(k=1) = \frac{5}{8}$$

$$g = \pm \frac{5}{8}$$

$\Rightarrow$

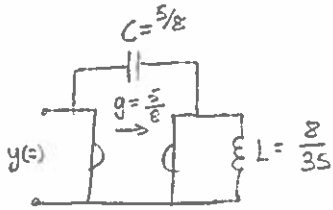


d)  $k=-1$

$$y(k=-1) = -\frac{5}{8}$$

$$y_L = \frac{35}{8s}$$

$$g = \pm \frac{5}{8}$$

$\Rightarrow$

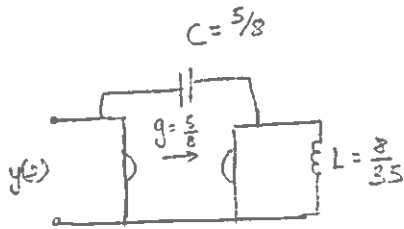

• Extractions at  $k=1$  and  $k=-1$  yield the same result

## Problem 2

a) Synthesize transfer function of a lossless ladder 2-port

$$Y_{21}(s) = \frac{V_2}{V_1} = \frac{k}{s^3 + 2s^2 + 2s + 1}$$

• Numerator is even  $\therefore$  divide out odd part of denominator:


$$\frac{V_2}{V_1} = \frac{\frac{k}{s^2 + 2s}}{1 + \frac{2s^2 + 1}{s^2 + 2s}} = \frac{-Y_{21}}{1 + Y_{22}}$$

• Synthesize  $Y_{22}$ :

$$Z_{22} = \frac{s^2 + 2s}{2s^2 + 1}$$


$$\begin{array}{r} \frac{1}{2}s \\ \hline 2s^2 + 1 \quad \left| \begin{array}{l} s^2 + 2s \\ s^3 + \frac{1}{2}s \end{array} \right. \quad \frac{4}{3}s \\ \hline \frac{3}{2}s \quad \left| \begin{array}{l} 2s^2 + 1 \\ 2s^2 \end{array} \right. \quad \frac{3}{2}s \\ \hline 1 \quad \left| \begin{array}{l} \frac{3}{2}s \\ \frac{3}{2}s \end{array} \right. \quad \frac{3}{2}s \\ \hline \frac{3}{2}s \\ \hline 0 \end{array}$$
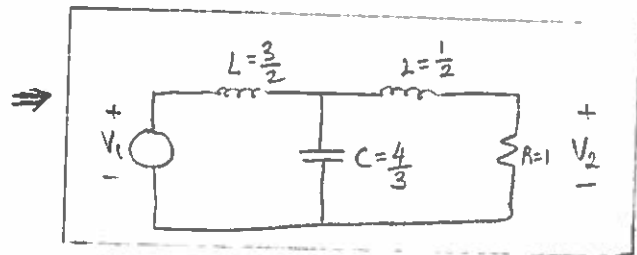
$$\therefore Z_{22}(s) = \frac{1}{2}s + \frac{1}{\frac{4}{3}s + \frac{1}{\frac{3}{2}s}}$$



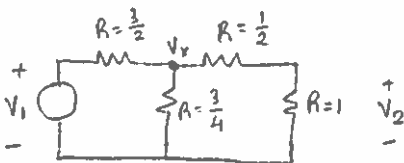b) At  $s=1$

$$\frac{V_2}{V_1}(s=1) = \frac{k}{1+2+2+1} = \frac{k}{6}$$



Solve for  $V_2/V_1$

$$\frac{V_2}{V_1} = \frac{1}{1 + \frac{1}{2}} = \frac{2}{3} \quad R_L = (1 + \frac{1}{2}) \parallel (\frac{3}{4}) = \frac{\frac{3}{2} \times \frac{3}{4}}{\frac{3}{2} + \frac{3}{4}} = \frac{1}{2}$$

$$\frac{V_x}{V_1} = \frac{R_L}{R_L + \frac{3}{2}} = \frac{1/2}{1/2 + \frac{3}{2}} = \frac{1}{4}$$

$$\frac{V_2}{V_1} = \frac{V_2}{V_x} \times \frac{V_x}{V_1} = \frac{2}{3} \times \frac{1}{4} = \frac{1}{6} \Rightarrow \frac{1}{6} = \frac{k}{6} \therefore \boxed{k=1}$$

(6)