

$$g_r = y_r^2(s)$$

$$C = \frac{y_r(s)}{R}$$

$$y_r(s) = y(s) \left[\frac{A y_i(s) - R y_r(s)}{A y_i(s) - R y_r(s)} \right]$$

Example: $y_i(s) = y(s) = \frac{s+1}{s+4}$

$$y(s) = \frac{y(s) + y(-s)}{2}, \quad \mathcal{R}y(s) = \frac{y(s) - y(-s)}{2}$$

$$y(s) = \mathcal{R}y + \mathcal{R}y \quad \text{here } \mathcal{R}y(s) = \frac{s+1}{s+4} + \frac{(-s)+1}{(-s)+4}$$

$$\begin{aligned}
 25r y(r) &= \frac{(r+1)(-r+4) + (r+4)(-r+1)}{(r+4)(-r+4)} \sim \frac{(-r^2 + 4r - r^2 + 4) + (-r^2 - 4r + r + 4)}{-r^2 + 16} \\
 &= \frac{-2r^2 + 8}{-r^2 + 16} = \frac{-2(r^2 - 4)}{-r^2 + 16} = \frac{-2(r-2)(r+2)}{-r^2 + 16}
 \end{aligned}$$

Prove $r = 2$ or $-2 \Leftarrow$ zeros of $25r y(r)$

for the Riemann's function

$$y(-r) = \frac{-r y(r) - r y(r)}{-r y(r) - r y(-r)}$$

$$\begin{aligned}
 \text{If } r \text{ is a zero of } 25r y(r) &\Rightarrow y(r) = 0 \Rightarrow 25r y(r) + 25r y(-r) \\
 &\Rightarrow 25r y(-r) = -y(-r)
 \end{aligned}$$

implies if $E_{-y}(k) = 0$ then $y(-a) = \frac{-a y(-a) + k y(k)}{-a y(k) - k y(-a)}$

gives that zero over zero at $y(-k)$, $a = -k$ cancel

$$\Rightarrow (a+k)(a-k) \text{ cancel numerator \& denominator}$$

$$= a^2 - k^2$$

$$\Rightarrow y_L(a) \text{ no singularities than } y_L(a)$$


$$\therefore \text{ form } y_L(a) = y_L(k) \cdot \frac{a y_L(a) - k y_L(a)}{a y_L(k) - k y_L(a)}$$

choose $k = +a$, $y_L(a) = \frac{k+1}{k+4} \left[\frac{a \left(\frac{a+1}{a+4} \right) - a \cdot \frac{3}{8}}{a \cdot \frac{3}{8} - a \left(\frac{a+1}{a+4} \right)} \right] \Rightarrow \frac{y_L(a)}{\frac{3}{8}} = \frac{a+a - a-a}{\frac{a^2}{2} + a - a - a}$

$$= 2$$

$$y_L(a) = 1$$

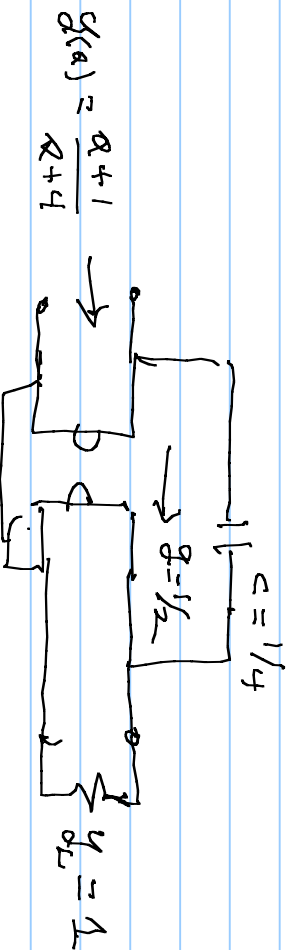
$$C = \frac{g(s)}{Re} = \frac{3/6}{2} = 1/4, \quad g^2 = g(s)^2 = (1/2)^2 \Rightarrow g = +1/2 \text{ or } -1/2$$



here g_L is PR

if g is PR

for $g(s) \Rightarrow$

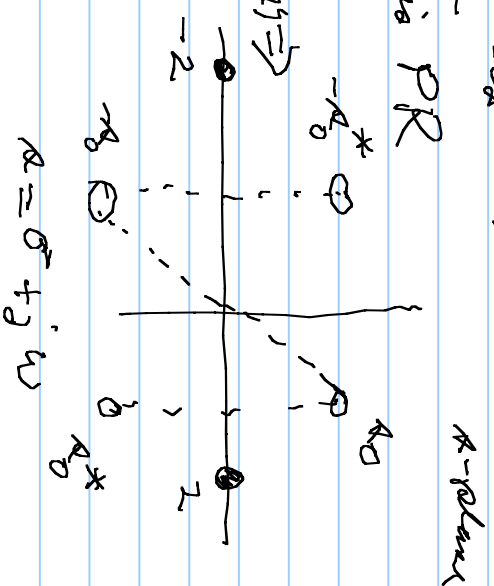

$$2 \text{ER}g = g(s) + g(-s) = 0$$

$$\Rightarrow \sum_{i=1}^n g(s_i) = 0 \text{ then } \sum_{i=1}^n g(-s_i) = 0$$

derive the admittance $Y_{ind}(s)$

(set external inputs sum to 0
column. external sum to 0)



$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = Y_{ind}(s) \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$

$$i_1 = sC_1(v_1 - v_4) + g_1(v_1 - v_3)$$

$$i_2 = sC_2(v_2 - v_4) - g_2(v_2 - v_3)$$

$$i_4 = sC_1(v_4 - v_1) - g_3(v_1 - v_3) + sC_2(v_4 - v_2) + g_2(v_2 - v_3)$$


$$Y_{ind} = \begin{bmatrix} aC_1 & 0 & -g_1 & g_1 - aC_1 \\ 0 & aC_2 & g_2 & -aC_2 - g_2 \\ +g_1 & -g_2 & 0 & -g_1 + g_2 \\ -aC_1 - g_1 & -aC_2 + g_2 & g_1 - g_2 & aC_1 + aC_2 \end{bmatrix}$$

ground node 3 $\Rightarrow v_3 = 0 \Rightarrow$ can delete 3rd row

\therefore also delete 3rd row 3 as $v_3 = -(v_1 + v_2 + v_4)$

$$Y_{del} = \begin{bmatrix} aC_1 & 0 & g_1 - aC_1 \\ 0 & aC_2 & -aC_2 - g_2 \\ -aC_1 - g_1 & -aC_2 + g_2 & a(C_1 + C_2) \end{bmatrix}$$

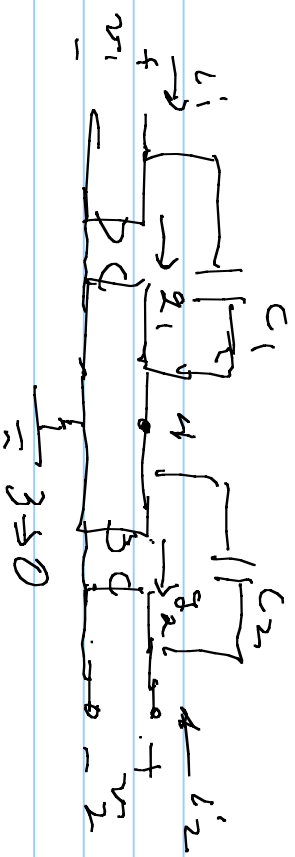if derive the 2-port Y from nodes 1-3 for nodes 2-3



Let $u_1 = 0$ to eliminate
The internal mode 4


$$u_1' = 0 = (-k_{c1} + g_1) v_1 + (-k_{c2} + g_2) v_2 + k_{c1} + c_2 v_2$$

$$v_1 = \frac{-1}{k_{c1} + c_2} [(-k_{c1} - g_1) v_1 + (-k_{c2} + g_2) v_2]$$


$$\begin{aligned} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} &= \begin{bmatrix} k_{c1} & 0 \\ 0 & k_{c2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} - \frac{1}{k_{c1} + c_2} \begin{bmatrix} g_1 - k_{c1} \\ -k_{c2} - g_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \\ &= \begin{bmatrix} y_1 - y_2 & y_2^{-1} y_{21} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \end{aligned}$$

$$A(C_1 + C_2) \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} A C_1 (A C_1 + A C_2) - (g_1 - A C_1) (-A C_1 - g_1) & -(g_1 - A C_1) (-A C_2 + g_2) \\ 0 - (-A C_2 - g_2) (-A C_1 - g_1) & A C_2 (A C_1 + A C_2) - (-A C_2 - g_2) (-A C_2 + g_2) \end{bmatrix}$$

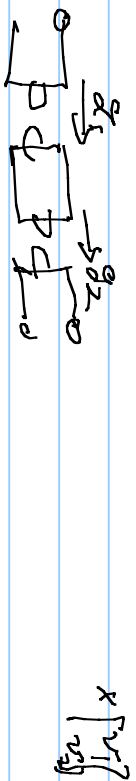Let's see what happens if $C_1 = C_2 = 0 \Rightarrow$ open circuits


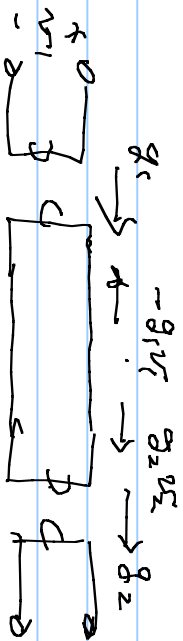
$$\frac{v_1}{v_2} = \frac{[0 - g_1 (-g_1) v_1 - g_1 g_2 v_2]}{[-g_1 g_2 v_1 + g_2^2 v_2]} = \frac{g_1 (g_1 v_1 - g_2 v_2)}{g_2 (-g_1 v_1 + g_2 v_2)} = -\frac{g_1}{g_2}$$



$\Rightarrow -g_1 v_1 = -g_2 v_2$ by KCL

$$\frac{v_2}{v_1} = \frac{g_1}{g_2}$$

$v_2 = \frac{g_1}{g_2} v_1$ $g_2 v_1 + g_1 v_2 = 0 \Rightarrow$ ideal Transformers (MUT)

