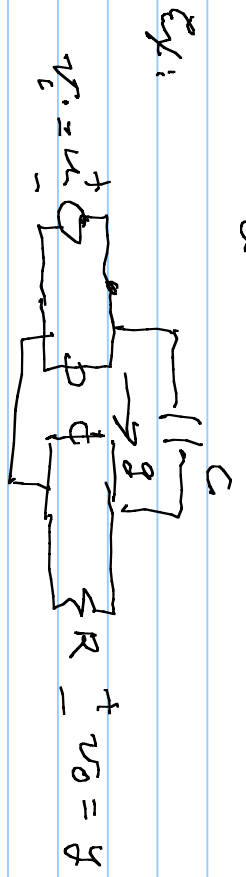



$$\dot{x} = Ax + Bu, \quad y = Cx$$

state variable equations; $E = I_n$ $R = \text{size of state}$

$$\begin{aligned} \dot{x} &\approx \hat{A}x + \hat{B}u \\ y &\approx \hat{C}x + Du + \epsilon, u'' + \dots \end{aligned}$$


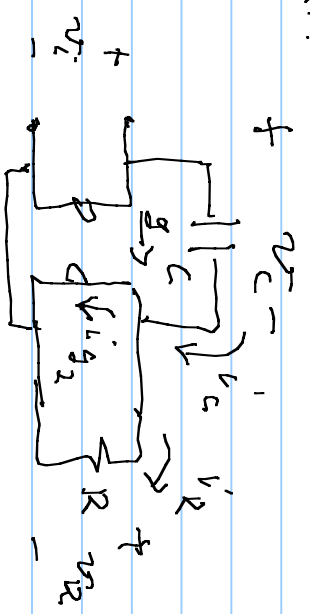
$$i_{g_1} = -g v_c, \quad i_{g_2} = G v_R, \quad G = 1/R$$



$$\dot{v}_c = C \frac{dv_c}{dt} = i_a' + i_R = -g v_c + G (v_c - v_R)$$

$$C \frac{dv_c}{dt} = -G v_c + (G - g) v_c$$

$$\dot{v}_c = -\frac{G}{C} v_c + \left(\frac{G-g}{C}\right) v_c$$

$$y = v_R = R_1 i_R = v_c - v_c \quad \Leftrightarrow \quad y = -v_c + v_c$$

$$\dot{x} = Ax + Bu, \quad y = Cx + Du$$

$$A = -\frac{G}{C}, \quad \frac{G-g}{C} = B, \quad C = 1, \quad D = +1$$

Stärke des Laplace Transform

$$s E X(s) = A \cdot X(s) + B U(s) \Rightarrow (s E - A) X(s) = B U(s)$$

$$X(s) = C X(s)$$

$$Y(s) = C [sE - A]^{-1} B U(s) = T(s), U(s)$$

$T(s)$ = transfer function matrix;

if $x \rightarrow \hat{x}$ = state then

$$Y(s) = \left\{ C [sE - A]^{-1} B + D + E s + E_1 s^2 + \dots \right\} U(s)$$

we have

$$\dot{\hat{x}} = A \hat{x} + B u, \quad y = C \hat{x}$$

Let P = constant nonsingular matrix

$$P \dot{\hat{x}} = P A \hat{x} + P B u, \quad y = C \hat{x}$$

Let Q = constant nonsingular, $x = Q \hat{x}$

$$PEQ \dot{x} = PAQx + PBu, \quad y = CQx$$

$$y(s) = CQ [PEQs - PAQ]^{-1} PB U(s)$$

$$T(s) = CQ [PEQs - PAQ]^{-1} PB$$

$$= CQ [P(EQ - A)Q]^{-1} PB$$

$$= CQ Q^{-1} (EQ - A)^{-1} P^{-1} PB = C (EQ - A)^{-1} B$$

Designing using state variables eqn.

$$\dot{x} = Ax + Bu$$

assume $T(s) = Y(s)$ admittance

$$y = Cx + Du$$

$u =$ input voltage v_i .


$y = v =$ current

1st assume u & v are same ports

$$C_{cap} = 1_k \Rightarrow v_c = A v_c + B v_i = v_{cap}$$

$$v_c = v_i = C v_c + D v_i$$
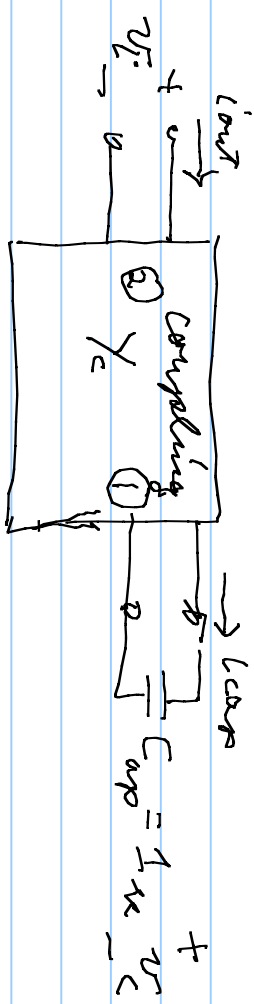
$$\begin{bmatrix} -1_{cap} \\ v_{cap} \\ v_i \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_c \\ v_i \end{bmatrix} = \text{constant admittances}$$



$$v_c = \begin{bmatrix} -A & -B \\ C & D \end{bmatrix}^{-1} = \text{constant} \quad T(s) = C(s^{-1}k - A)^{-1} (B + D)$$

$$E_6: T(s) = y(s) \Rightarrow \text{write } \dot{x} = Ax + Bv, \quad v_{out} = Cx + Dv$$


Then we can design a circuit by forming

$$Y_c = \begin{bmatrix} -A & -B \\ C & D \end{bmatrix} \quad \& \text{ loading in unit capacitors}$$

Then Y_c is a constant; realize by OTA's of gains

g_{m0j} = gain of j 'th OTA.

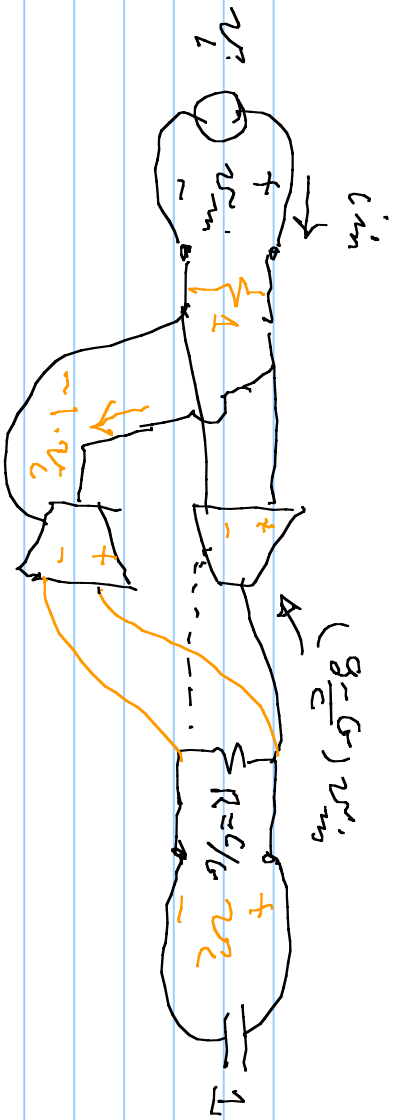
$$\begin{aligned} \dot{x} &= -\frac{g}{C}x + \frac{(g-g)}{C}v_i \Rightarrow Y_c = \begin{bmatrix} g/C & \frac{g-g}{C} \\ -1 & +1 \end{bmatrix} \\ v_{in} &= vx + v_i \end{aligned}$$



If the output is a voltage of another port

$$v_o = Av_i + Bv_i$$

$$v_o = Cv_i + Dv_i$$

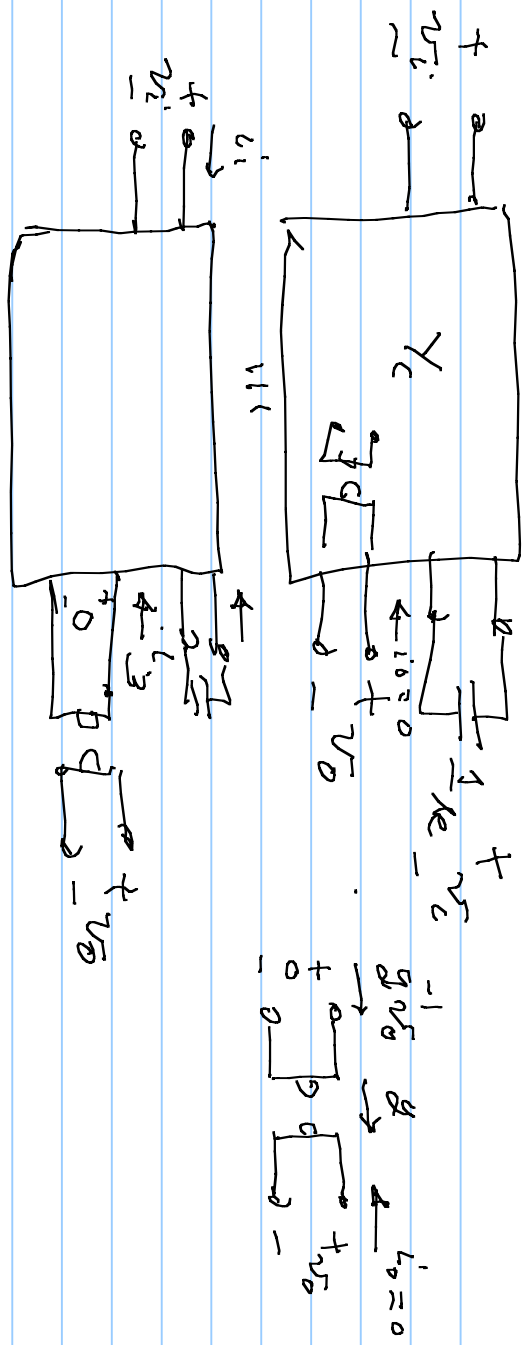

$$Y_c \begin{bmatrix} v_c \\ v_c \\ 0 \end{bmatrix} = \begin{bmatrix} -L_c \\ L_m \\ i_3 = -g^{-1} v_2 \end{bmatrix} = \begin{bmatrix} -X \\ \text{demand case} \\ i_3 = -g^{-1} v_2 \end{bmatrix} = \begin{bmatrix} -A & -B \\ \cdot & \cdot \\ -gC & -gD \end{bmatrix} \begin{bmatrix} X \\ v_c \\ 0 \end{bmatrix}$$

can fill in dots any way she wishes to make
skew symmetric ($M = -M^T$) or zero