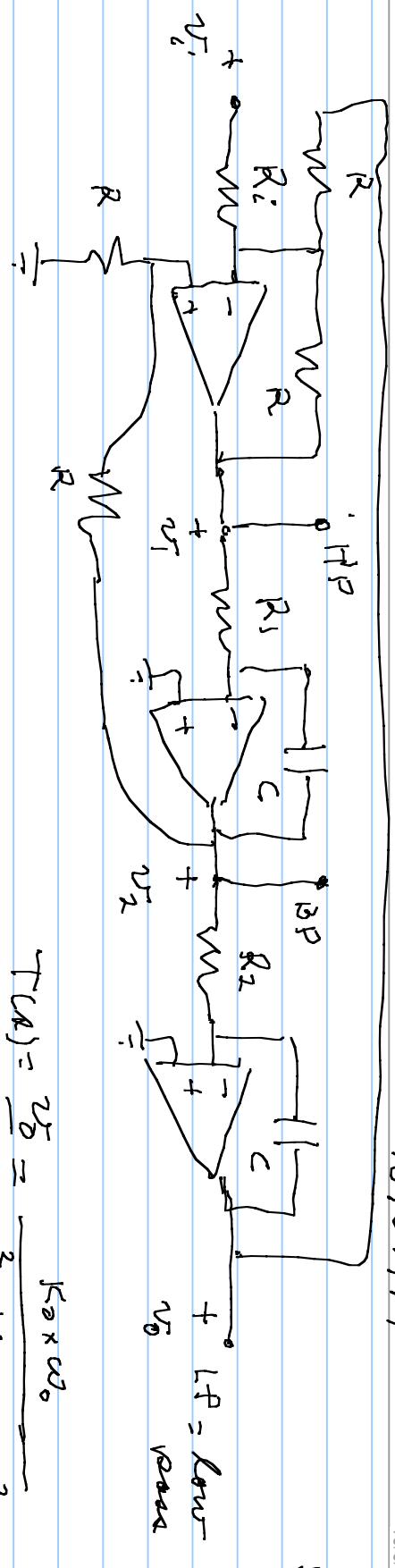



EE 610

10/07/14



$$T(s) = \frac{v_0}{v_i} = \frac{K_0 \times \omega_0}{R^2 + \omega_0 R + \omega_0^2}$$

LP

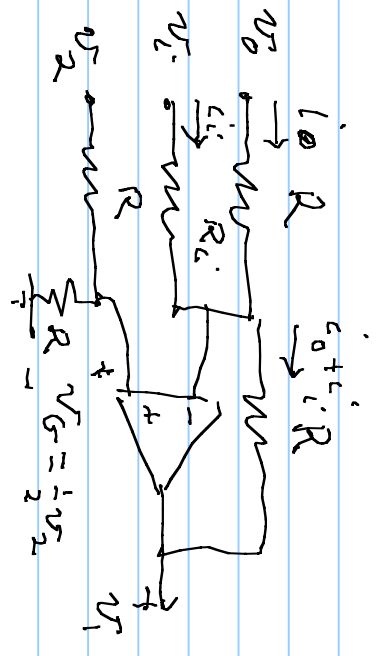

$$v_1 = -R(i_0 + i_1) + v_0, \quad G = 1/R$$

$$i_0 = G(v_0 - v_1), \quad i_1 = G_1(v_1 - v_0)$$

$$v_1 = -v_0 + v_0 - R G_1 v_1 + R G_1 v_0 + v_0$$

$$v_1 = -R_{G_1} \cdot v_1 + (1 + \frac{1}{\alpha} R_{G_2}) v_2 - v_0$$

$$v_2 = -\frac{1}{\alpha C R_1} v_1, \quad v_0 = -\frac{1}{\alpha C R_2} v_2 = \left(\frac{-1}{\alpha C R_1} \right) \left(\frac{-1}{\alpha C R_2} \right) v_1$$

$$v_2 = -\frac{1}{\alpha C R_1} \left[\alpha^2 R_1 R_2 C^2 \right] v_0 = -\alpha R_2 C v_0$$

$$\rightarrow \alpha^2 R_1 R_2 C^2 \cdot v_0 = -R_{G_1} \cdot v_1 + (2 + R_{G_2}) \frac{1}{2} (\alpha C R_2) v_0 - v_0$$

$$[\alpha^2 R_1 R_2 C^2 + \frac{1}{2} (2 + R_{G_2}) C R_2 \cdot \alpha + 1] v_0 = -R_{G_1} \cdot v_1$$

$$\frac{v_0}{v_1} (a) = \frac{-R_{G_1} / (R_1 R_2 C^2)}{\alpha^2 + \frac{1}{2} (2 + R_{G_2}) C R_2 \alpha + \frac{1}{R_1 C \cdot R_2 C}} = \frac{-R_{G_1} / (R_1 R_2 C^2)}{\alpha^2 + \frac{1}{2} (2 + R_{G_2}) \frac{\alpha}{R_1 C} + \frac{1}{R_1 C \cdot R_2 C}}$$

$$\omega_0^2 = \frac{1}{R_1 C \cdot R_2 C} \Rightarrow \omega_0 = \frac{1}{C \sqrt{R_1 R_2}}$$

$$\frac{\omega_0}{Q} \Rightarrow Q = \frac{\omega_0 \cdot R R_C}{(2 + R_G)}$$

all-pass: $T(s) = \frac{N(s)}{D(s)} = \frac{D(-s)}{D(s)} = \frac{R^2 - \frac{\omega_0^2}{Q} s + \omega_0^2}{R^2 + \frac{\omega_0^2}{Q} s + \omega_0^2}$

$$|T(j\omega)|^2 = T(j\omega) T(-j\omega) = \frac{D(-j\omega)}{D(j\omega)} \times \frac{D(j\omega)}{D(-j\omega)} = 1; \quad T(j\omega) = |T(j\omega)| e^{j\Delta T(j\omega)}$$

$$= 1 \times \frac{e^{j\Delta T(j\omega)}}{e^{j\Delta T(j\omega)}} = e^{j\Delta N(j\omega)}$$

$\Delta N(j\omega)$ = are tan $\left(-\omega \cdot \frac{\omega_0}{Q} (\omega_0^2 - \omega^2) \right) \approx e^{j\Delta N(j\omega)}$


$\Delta D(j\omega)$ = are tan $(\omega \omega_0 / Q (\omega_0^2 - \omega^2)) \approx -\Delta N(j\omega)$

$$\Delta T_{r(j\omega)} = 2 \Delta N_{g(j\omega)} = -2 \text{are tan} \left[\omega \frac{2\omega_0}{\omega_0^2 - \omega^2} \right]$$

am

VAF = minimal active filters
(cata variables filters)

Get all poles from VAF & ITI

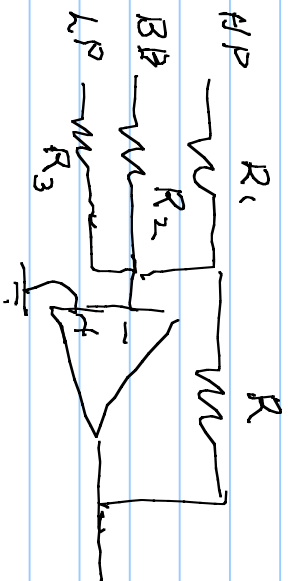

adjoint R & T give desired
numerators

no poles

PR functions = positive real & rational

$$g(s) = \frac{N(s)}{D(s)}$$

Positive real definition

1. Real for $\text{Re } s > 0 = \text{RHP open}$
(real coefficients of PR) \Rightarrow real derivative
2. Analytic in $\text{Re } s > 0$ (other criteria)
(no poles or zeroes in $\text{Re } s > 0$ if PR)
- 3.