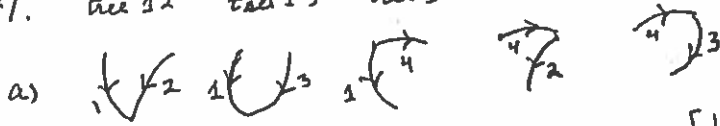


#1. tree 12 tree 13 tree 14 tree 24 tree 34



b) $C_{12} = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 1 & 1 \end{bmatrix}$, $C_{13} = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 1 & 1 \end{bmatrix}$, $C_{14} = \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 1 & 1 & 1 \end{bmatrix}$, $C_{24} = \begin{bmatrix} 1 & 1 & 1 & 0 \\ -1 & 0 & 0 & 1 \end{bmatrix}$, $C_{34} = \begin{bmatrix} 1 & 1 & 1 & 0 \\ -1 & 0 & 0 & 1 \end{bmatrix}$

Derive $C_{12} = TC_{13} = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 1 & 1 \end{bmatrix} = \begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 1 & 1 \end{bmatrix} \Rightarrow 1 = t_{11}, 0 = t_{12}, -1 = -t_{11} + t_{12}$
 $0 = t_{21}, 1 = t_{22}, 1 = -t_{21} + t_{22}$

$\Rightarrow t_{11} = 1, t_{12} = 0 \Rightarrow \text{agree } -1 = -1 + 0 \Rightarrow T = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = I_2$ at $C_{12} = C_{13} \Rightarrow T^{-1} = I_2$
 $t_{21} = 0, t_{22} = 1 \Rightarrow 1 = 0 + 1$

#2. As the poles are all on the jw axis, they must be simple with positive residues

$\therefore y(s) = \frac{k_1 s}{s^2 + 1} + \frac{k_2 s}{s^2 + 4} = \frac{k_1 s^3 + 4k_1 s + k_2 s^3 + k_2 s}{(s^2 + 1)(s^2 + 4)} = \frac{s[(k_1 + k_2)s^2 + (4k_1 + k_2)]}{(s^2 + 1)(s^2 + 4)}$


$\Rightarrow k_1 + k_2 = 1, 4k_1 + k_2 = a \Rightarrow k_2 = 1 - k_1 \Rightarrow 4k_1 + (1 - k_1) = a \Rightarrow a = 3k_1 + 1$

$\therefore a = 3k_1 + 1$ for $k_1 > 0 \Rightarrow 1 < a$ and $k_2 > 0 \Rightarrow k_1 < 1 \Rightarrow a < 3 + 1 = 4; \therefore 1 < a < 4$
 which is the same as poles & zeros alternate (cancellation of $a = 1$ or 4)

For cases synthesis $y(s) = \frac{s^3 + a s}{s^4 + 5s^2 + 4} \Rightarrow \frac{s^3 + a s}{s^4 + 5s^2 + 4} = \frac{s^3 + a s}{(s^2 + 1)(s^2 + 4)} = \frac{1}{s + \frac{1}{5-a} + \frac{(5-a)^2 s}{5a - a^2 - 4} + \frac{1}{4(5-a)}}$

all coefficients are > 0 for $1 < a < 4$
 $(5a - a^2 - 4) = (4-a)(1+a)$

\therefore Ladder circuit

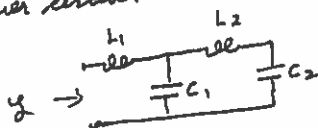

$L_1 = 1, L_2 = \frac{(5-a)^2}{5a - a^2 - 4}$
 $C_1 = \frac{1}{5-a}, C_2 = \frac{5a - a^2 - 4}{4(5-a)}$

(some absent if $a = 1$ or 4)

#3. $S_1 = \frac{2s^2}{2s^2 + a s + b}, S_2 = \frac{1}{2s^2 + a s + b}$, $D = 2s^2 + a s + b$ must be Hurwitz & $|S_i(j\omega)| \leq 1, i=1,2$
 $\Rightarrow a > 0 \text{ \& } b > 0$


For $S_2(s) = 1/b \leq 1 \Rightarrow b \geq 1$

For $|S_1(j\omega)|^2 \leq 1 \Rightarrow 4\omega^2 \leq (b - 2\omega^2)^2 + (a\omega)^2 \Rightarrow 0 \leq b^2 + (a^2 - 4b)\omega^2 \Rightarrow a^2 - 4b \geq 0, b \geq 1$

For $|S_2(j\omega)|^2 \leq 1 \Rightarrow 1 \leq b^2 + (a^2 - 4b)\omega^2 + 4\omega^4$ is true for $a^2 - 4b \geq 0, b \geq 1$

$\therefore S_1$ & S_2 are BR at $S_i^*(s) = S_i(s^*)$, $i=1,2$, when $a^2 \geq 4b \geq 4$

#4.

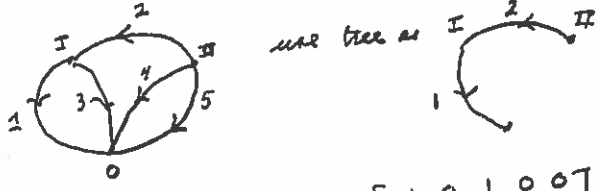

use tree as I II III

$$e = \begin{bmatrix} 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 & 1 \end{bmatrix}, \quad \sigma = \begin{bmatrix} -1 & 0 & 1 & 0 & 0 \\ -1 & -1 & 0 & 1 & 0 \\ -1 & -1 & 0 & 0 & 1 \end{bmatrix}; \quad e^T v_t = v_b, \quad \sigma^T l'_2 = l'_b$$

$= v_t + e$
 $= i + j = i' \text{ then}$

$AV = BE$ for branch 1: $i_3 = i_1 = ACV_1, \quad v_1 = v_1 + e_1 \Rightarrow v_1 = v_b - e_1$

$$\begin{bmatrix} AC_1 & & & & \\ & AC_2 & & & \\ & & 0 & 0 & \\ & & g_m & 0 & G_5 \end{bmatrix} v = \begin{bmatrix} 1 & & & & \\ & 1 & & & \\ & & 1 & & \\ & & & 1 & \\ & & & & 1 \end{bmatrix} l' = \Delta_5 \cdot \sigma^T l'_2$$

$$= Y_{br1} [e^T v_t - e^T e]$$

$$= \begin{bmatrix} AC_1 & & & & \\ & AC_2 & & & \\ & & 0 & 0 & \\ & & g_m & 0 & G_5 \end{bmatrix} \begin{bmatrix} v_{t1} \\ v_{t2} \\ v_{t3} \\ v_{t4} \\ v_{t5} \end{bmatrix} - \begin{bmatrix} AC_1 e_1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & -1 & -1 \\ 0 & -1 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} l'_3 \\ l'_4 \\ l'_5 \end{bmatrix}$$

$$= \begin{bmatrix} C_1 & 0 & 0 & 0 & 0 \\ 0 & C_2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_t \\ l_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 & -1 & -1 & -1 \\ 0 & 0 & 0 & -1 & -1 \\ 0 & 0 & 0 & 0 & 0 \\ -g_m & 0 & 0 & 0 & 0 \\ 0 & -G_5 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_t \\ l_2 \end{bmatrix} + \begin{bmatrix} C_1 e_1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} v_t \\ l_2 \end{bmatrix} = \begin{bmatrix} v_{1b} \\ v_2 \\ l_3 \\ l_4 \\ l_5 \end{bmatrix} = v_t$$

$$y = v_5 = [0 \ 0 \ 0 \ 0 \ 1] e^T v_t = [v_{t1} + v_{t2}] = [1 \ 1 \ 0 \ 0 \ 0] x$$

Can use this to get v_5/e_1 , but it is not semi-state due to e_1 (can peel branch 1 as two branches)

do define a new variable $x_6 = e_1 = u \Rightarrow \hat{x} = \begin{bmatrix} x \\ x_6 \end{bmatrix} \Rightarrow$

$$\begin{bmatrix} C_1 & 0 & 0 & 0 & -C_1 \\ 0 & C_2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \hat{x} = \begin{bmatrix} 0 & 0 & -1 & -1 & -1 \\ 0 & 0 & 0 & -1 & -1 \\ 0 & 0 & 0 & 0 & 0 \\ -g_m & 0 & 0 & 0 & 0 \\ 0 & -G_5 & 0 & 0 & 0 \end{bmatrix} \hat{x} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} u, \quad y = [1 \ 1 \ 0 \ 0 \ 0 \ 0] \hat{x}$$

Can reduce this to get $v_5/e_1 = (\hat{x}_1 + \hat{x}_2)/u$.

Easier: $-i_{c1} = -i_{c2} = AC_1(e_1 - v_I) = AC_2(v_I - v_{II})$ & $i_{R5} = -i_{c2} - g_m v_I = G_5 v_{II}$

$$\Rightarrow AC_1 e_1 - (AC_1 + AC_2) v_I = -AC_2 v_{II}$$

$$\Rightarrow v_I = (AC_2 v_{II} + AC_1 e_1) / (C_1 + C_2) \Rightarrow G_5 v_{II} = AC_1 e_1 - (AC_1 + g_m) \frac{AC_2 v_{II} + AC_1 e_1}{C_1 + C_2}$$

$$= \frac{[AC_1^2 + AC_2^2 - AC_1^2 - AC_1 g_m] e_1 - (AC_1 + g_m) AC_2 v_{II}}{C_1 + C_2}$$

$$\text{or } y = v_5 = v_{II}$$

$$\Rightarrow ((G_5)[C_1(C_1 + C_2)] + [AC_1 + g_m] AC_2) y = AC_1 [AC_2 - g_m] e_1$$

$$\Rightarrow \frac{y}{e_1} = \frac{AC_1 [AC_2 - g_m]}{d[C_1(C_1 + C_2) + AC_1 C_2 + g_m C_2]} = \frac{C_1 [AC_2 - g_m]}{AC_1 C_2 + [g_m C_2 + G_5(C_1 + C_2)]} = \frac{d - g_m/C_2}{d + [g_m/C_1 + G_5(1 + C_2/C_1)]}$$