

610 Fall 2017 – Homework 6 Due Th 10/19/17 **New due date Tu 10/24/17**

1. (50 points, Richards' synthesis, continued)

For the degree three lossless admittance

$$y(s) = (3/2)s(s^2+9)/(s^2+4)$$

- a) Compare synthesis using a Richards' function at $k=1$ and at $k=3$.
b) Assume this is an impedance $z(s) = (3/2)s(s^2+9)/(s^2+4)$ and compare its Richards' function synthesis at $k=1$ with that of $y(s)$
2. (25 points, indefinite Y for BJT)

For the grounded emitter transistor the admittance matrix is

$$Y(s) := \begin{bmatrix} g_{\pi} + s \cdot (C_{\pi} + C_{\mu}) & -s \cdot C_{\mu} \\ -s \cdot C_{\mu} + g_m & g_o + s \cdot C_{\mu} \end{bmatrix}$$

- a) Give the Indefinite $Y_{ind}(s)$ and draw the 3-terminal circuit with currents and voltages labelled as the BJT terminals, b,e,c.
b) Ground the base terminal and give the admittance matrix with $v_{eb}=v_1$, $v_{cb}=v_2$ and $i_e=i_1$, $i_c=i_2$. Draw the resulting Pi equivalent circuit.
c) Find the input admittance when the load admittance, $y_L(s)$, is connected from collector to ground.
3. (25 points, Bott-Duffin synthesis)
- Using the Bott-Duffin method synthesize

$$Y(s) = [s^2 + (1/2)s + (1/4)] / [s^2 + (1/2)s + 1]$$

{ this is the function of example 8.6-1 of page 363 with $s \rightarrow 2s$ }