

EE 610  
09/22/17

State Equations

$$\dot{x} = Ax + Bu$$

$$\dot{x} = dV/dt = Ax$$

LTI = linear

$$y = Cx + Du$$

$$A = dV/dt$$

Time Invariant

$$A = \sigma + j\omega$$

$$f[s] = \int_{-\infty}^{\infty} f(t) e^{st} dt$$

Capacitor  $i = C dV/dt$ ,  $C = \text{const} = \text{capacitance}$

at solving ODE


$$C \frac{dV}{dt} = i$$

if  $C=1$ ,  $dV = dx = \text{current}$ ,  $x = \text{voltage}$

$$\dot{x}_1 = 3x_2$$

$$\dot{x}_2 = 5x_1 - 2x_2$$

$$[x_1(0), x_2(0)]$$

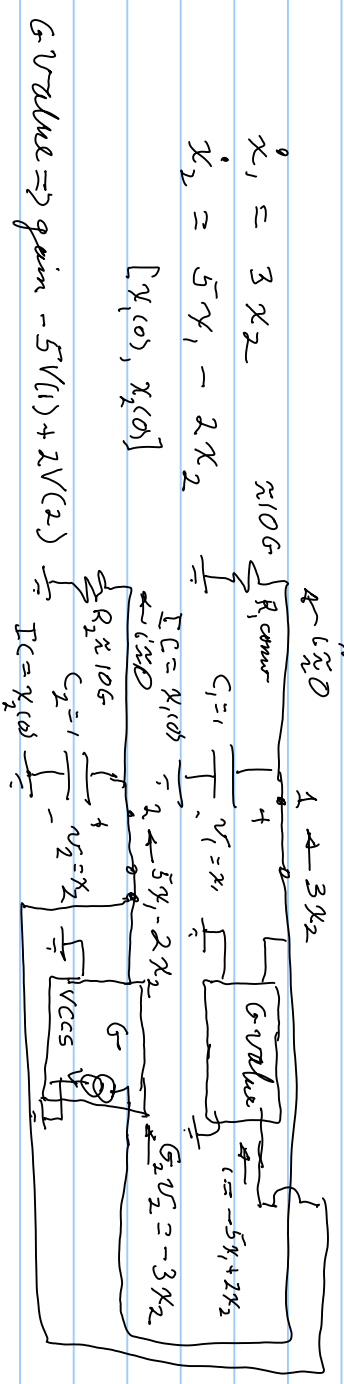

G value  $\Rightarrow$  gain  $-5V(1) + 2V(2)$

$$\dot{x}_1 = 3x_1 x_2 \quad \leftarrow \text{G value} \quad \dot{v} = 3V(1) * V(2)$$

$$\dot{x}_2 = -2x_1$$

can't do with  
G itself or  $\mathcal{A}(G)$   
only allows constants

semi-state eqs.  $E \dot{x} = Ax + Bu$

LTI  $y = Cx$

$$x = \begin{bmatrix} v_f \\ \cdot \\ v_r \end{bmatrix} = \begin{matrix} \text{semi-} \\ \text{state} \\ \text{v-vectors} \end{matrix}$$

$E$  is singular

$$v_b = \begin{bmatrix} 0 \\ \vdots \\ 1 \end{bmatrix}^T$$

$$v_b = \begin{bmatrix} 0 \\ \vdots \\ 1 \end{bmatrix}^T$$

But state - variable

$$\dot{x} = Ax + Bu$$

$x = \text{state}$

$$y = Cy + Du + \underbrace{E \dot{v} + F \ddot{v}}_{\cdot}$$

$\Rightarrow r$ -vector

if ignores

$$\text{then } \mathcal{A}^{-1} X(a) = A X(a) + B V(a) \Rightarrow (\mathcal{A}^{-1} - A) X = BV$$

$$Y(a) = CX(a) + DV(a)$$

$$y = CX + DV$$

$$\Rightarrow y = DV + C(\mathcal{A}^{-1} - A)^{-1} B V = [D + C(\mathcal{A}^{-1} - A)^{-1} B] \cdot V$$

$$Y(s) = T(s), U(s) = D + C(sI - A)^{-1}B; \quad \text{as } s \rightarrow \infty \Rightarrow T(s) = D$$

$s \neq \infty$

can not get  $T(s) = a$  unless  $E \neq 0 + F \neq 0 + \dots$

Ex:

$$\begin{bmatrix} a & 0 \\ 0 & 0 \end{bmatrix} x = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} x + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u \quad x = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

$$y = \begin{bmatrix} a & b \end{bmatrix} x$$

$$\Rightarrow x_2 = u, \quad ax_1 = x_2 = u \Rightarrow y = \begin{bmatrix} a & b \end{bmatrix} \begin{bmatrix} 1/a u \\ u \end{bmatrix} = \frac{a}{a} u + bu$$

$$E \dot{x} = Ax + Bu \quad \Rightarrow (sE - A)x = Bu \Rightarrow x = (sE - A)^{-1}Bu$$

$$y = Cx = C(sE - A)^{-1}Bu$$

$$T(s) = C_x (sE - A)^{-1} B \quad \text{where } sE - A \text{ is nonsingular}$$

$$E = \begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix}, \quad A = I_2 \Rightarrow \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} s-1 & 0 \\ 0 & s-1 \end{bmatrix}$$

inverse  $\times$  original = identity  $\begin{bmatrix} -1 & -a \\ 0 & -1 \end{bmatrix} \times \begin{bmatrix} -1 & a \\ 0 & -1 \end{bmatrix} = \begin{bmatrix} +1 & -a+a=0 \\ 0 & 1 \end{bmatrix} = I_2$

$$C_u \begin{bmatrix} -1 & -a \\ 0 & -1 \end{bmatrix} B \quad \text{choose } C_u = \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix}, B = \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} -1 & -a \\ 0 & -1 \end{bmatrix} = \begin{bmatrix} 0 & -a \\ 0 & -a \end{bmatrix}, \quad \begin{bmatrix} 0 & -a \\ 0 & -1 \end{bmatrix} \begin{bmatrix} 0 \\ -1 \end{bmatrix} = a$$

$$T(a) = a \quad \text{for} \quad \begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix} \dot{x} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} x + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u, \quad x = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$


$$y = \begin{bmatrix} 1 & 0 \end{bmatrix} x$$

$$T(a) = a$$

$\therefore$  The state equations come naturally from circuits & given LTI ones we will be able to create a circuit. State variable equations are essentially a special case.

$$Av = Bv'$$

resistor & multiplier

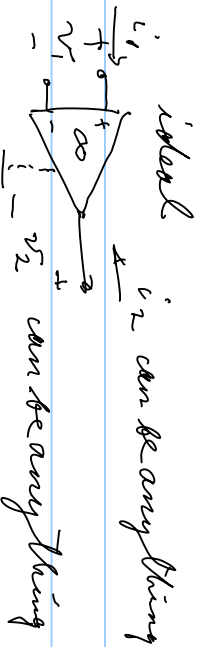

Ans:  $v_1 = \text{arbitrary}$

$i_1 = \text{arbitrary}$


(independent of  $v_1$ )

$v_2 = 0, i_2 = 0$

mutual  
connection  
 $v_1 = 0$

$i_1 = 0$

$\Rightarrow$  multiplier

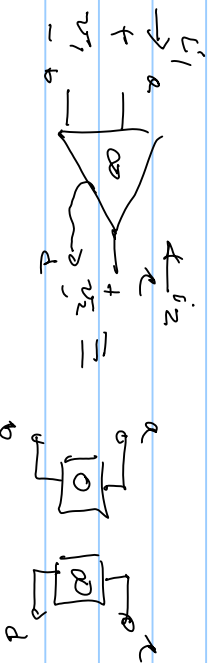

Ans:  $Av = Bi$  for an op-amp (ideal)

$$\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$


both  $A \geq B$  are singular

$\Rightarrow$  not 2-port admittance

But nodes  $\Rightarrow$   $[0 \ 0] [v_1] = [0 \ 0] [i_1]$

multiply  $\Rightarrow$   $\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} [v] = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} [i] \Rightarrow \begin{bmatrix} 1 \\ 0 \end{bmatrix} v = \begin{bmatrix} 0 \\ 1 \end{bmatrix} i$

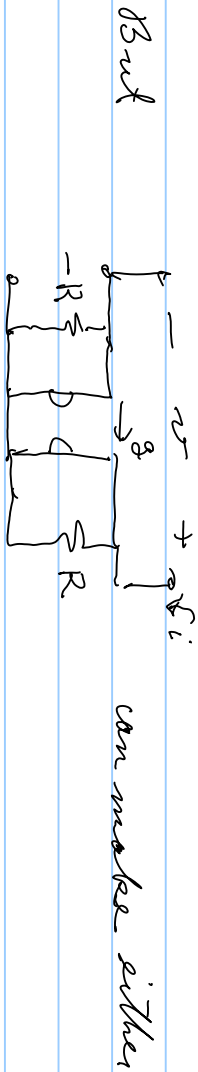$\Rightarrow$  now square  $A \& B \Rightarrow$  often has if have a nodes somewhere with is paired another & vice versa.



$$\begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix} \dot{x} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} x + \begin{bmatrix} 0 \\ -1 \end{bmatrix} u$$

to convert to state variable.  
 equations; keep  $x_2$  & eliminate  $x_1$   
 $y = [1 \ 0] x$

second eq.:  $0 = x_1 - u = x_1 - u$

1st eq., eliminate  $x_1$ ,  $\dot{x}_2 = x_1 - u$

let  $x = x_2$ ,

$$y = x_1 - u =$$

$\left. \begin{array}{l} \dot{x} = -u \\ y = u \end{array} \right\} \begin{array}{l} \text{states} \\ \text{variables} \end{array}$   
e.g.

can manipulate by row & column operations

$$P \in Q = \begin{bmatrix} 1_k & 0 \\ 0 & 0_{b-k} \end{bmatrix};$$

$$\exists \tilde{x} = Qx + Bu$$

$$P \in Q \tilde{x} = P Q Q^{-1} x + P B u$$

$$Q^{-1} x = \tilde{x} \Rightarrow \begin{bmatrix} 1_k & 0 \\ 0 & 0_{b-k} \end{bmatrix} \begin{bmatrix} \tilde{x}_1 \\ \tilde{x}_2 \end{bmatrix} = P Q Q^{-1} x + P B u$$

$\Rightarrow$  solve for  $\tilde{x}_2 = f(\tilde{x}_1)$  to eliminate  $\tilde{x}_2$