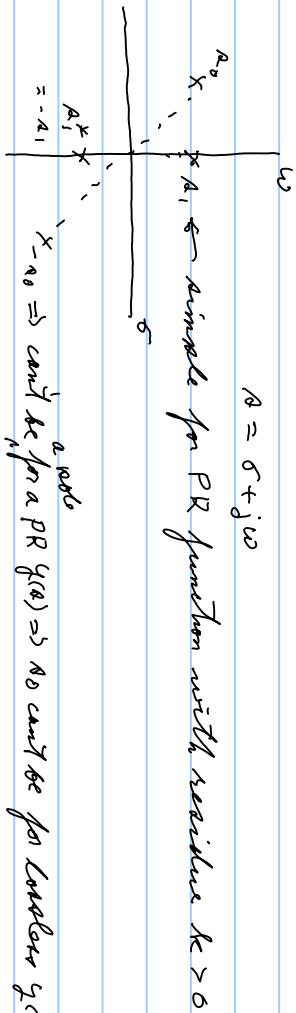


Unless 1-part $y(\omega) + y(-\omega) = 0 \Rightarrow y(\omega) = -y(-\omega) \Rightarrow$ odd in ω

Ev $y(\omega) = \frac{1}{2} (y(\omega) + y(-\omega))$

Od $y(\omega) = \frac{1}{2} (y(\omega) - y(-\omega))$

$y(\omega) = \text{Ev} + \text{Od}$




transfer $y(\omega) = \sum_{i=1}^m \frac{2k_i \omega}{\omega^2 + \omega_i^2} + k_{\infty} \omega$ $k_i > 0 \quad i=1, \dots, m, \infty$

$y(j\omega) = jB(\omega)$ look @ $\frac{dB(\omega)}{d\omega}$

$\frac{dB(\omega)}{d\omega} = \sum_{i=1}^m \frac{2k_i \omega}{\omega_i^2 + \omega^2} + k_{\infty} \omega$

$\frac{dB(\omega)}{d\omega} = k_{\infty} \omega + \sum_{i=1}^m \left[\frac{2k_i \omega}{\omega_i^2 + \omega^2} + (2k_i \omega) \frac{-1}{(\omega_i^2 + \omega^2)^2} (-2\omega) \right] = k_{\infty} \omega + \sum_{i=1}^m \frac{2k_i \omega}{(\omega_i^2 + \omega^2)^2} [\omega_i^2 - \omega^2 + 2\omega^2]$
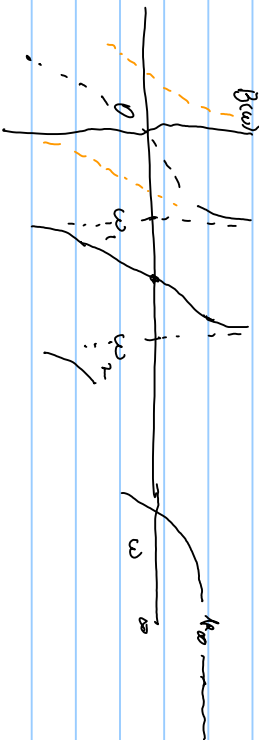
$$\frac{dB(\omega)}{d\omega} = K_{\infty} + \sum_{i=1}^m \frac{2k_{p_i}}{(\omega_i^2 - \omega^2)^2} (\omega_i^2 + \omega^2) \quad \nearrow, 0 \quad \& \quad \infty \text{ at } \omega = \omega_i \Leftrightarrow \text{pole points on } \omega \text{ axis}$$



shows general poles alternate for LPR function

$$y(s) = \text{zeros \& poles \& general terms with } y(s) \rightarrow 0 \Leftrightarrow \text{LPR}$$

$$= \frac{N(s)}{D(s)} \text{ or } \frac{1}{s} \frac{N(s)}{D(s)}$$

$\frac{N(s)}{D(s)}$ can synthesize by 1st & 2nd order

Partial fraction expansion of $y(s)$
 Partial fraction expansion of $z(s) = y(s)$
 Continued fraction expansions (1st about ∞ , 2nd about 0)


$$y(s) = K_{\infty} s + \sum_{k=1}^m \frac{2k_{p_k} s}{s^2 + \omega_k^2} = K_{\infty} s + \left[\underbrace{1}_{z_2(s) = \frac{1}{\sum \frac{2k_{p_i} s}{s^2 + \omega_i^2}}} \right] \leftarrow \text{has a pole @ } \infty$$

Ex: $y(s) = \frac{R(s^2+2)}{(s^2+1/2)} = 1 + \frac{2R}{s^2+1/2} = s + \frac{1}{\frac{2}{3}s + \frac{1}{3R}} =$ continued fraction expansion of $y(s)$ about $s = \infty$

$LPR = \frac{R^3+2R}{R^2+1/2}$


$\frac{R^2+1/2}{R^3+2R} \Rightarrow \frac{R}{R^2+1/2} \Rightarrow \frac{1/2}{R^2+1/2} \Rightarrow \frac{3/2}{R^2+1/2}$

$y = \frac{R(s^2+2)}{s^2+1/2}$

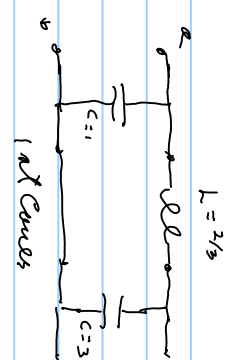

2nd Order, $y(s) = R + \frac{3/2 R}{s^2+1/2} \Rightarrow$

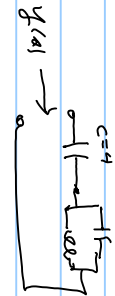1st Order, $z(s) = \frac{s^2+1/2}{R(s^2+2)} = \frac{1/4}{R} + \frac{2R}{s^2+2}$




2nd Cases = continued fraction expansion about $s=0$

$y(s) = \frac{R(s^2+2)}{(s^2+1/2)} = \frac{1}{z(s)}, z(s) = \frac{R^2+1/2}{R(s^2+2)} = \frac{1/2+R^2}{2R+R^3}$

$$Z(s) = \frac{1/2 + s^2}{2s + s^3}$$

continued fraction expansion about $s=0$
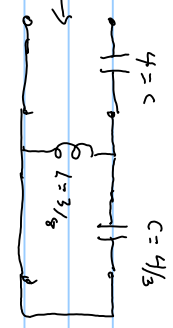
$$\begin{aligned} Z(s) &= \frac{1}{2s + s^3} \\ &= \frac{1}{s(2 + s^2)} \\ &= \frac{1}{s} \cdot \frac{1}{2 + s^2} \\ &= \frac{1}{s} \cdot \frac{1/4}{1/2 + 1/4 s^2} \\ &= \frac{1/4}{s} \cdot \frac{1}{1/2 + 1/4 s^2} \\ &= \frac{1/4}{s} \cdot \frac{1}{(1 - 1/4 s^2)} = \frac{3/4}{s} \cdot \frac{1}{2s + s^3} \end{aligned}$$



2nd Case for the given $Y(s) = \frac{2s + s^3}{1/4 + s^2}$

1st Case \Rightarrow ladder circuits with 0's of transmission @ $s=0 \Rightarrow$ low-pass
 2nd Case \Rightarrow " " " " of " " " " @ $s=0 \Rightarrow$ high-pass

with 1st & 2nd Strokes give minimal realization using $ST[1] = S[S]$, L's & C's

Hurwitz Test: strictly Hurwitz polynomial \Leftrightarrow no zeroes in $\sigma > 0$
 Hurwitz \Leftrightarrow no zeroes in $\sigma > 0$, on $\sigma = 0$ only simple zeroes



$$\begin{aligned} v &= (3 + s), i \\ &= \left(\frac{m}{d} + 1\right) i = \left(\frac{n+d}{d}\right) i \end{aligned}$$

given $P(s) = m(s) + d(s)$
 form $Z(s) = \frac{m}{d}$

$$P(s) = 6s^4 + 5s^3 + 4s^2 + 3s + 2 = (6s^4 + 4s^2 + 2) + (5s^3 + 3s)$$

$z(s) = \frac{5s^3 + 3s}{6s^4 + 4s^2 + 2}$ is this LPR? or is $P(s)$ is of unity?

$$z(s) \rightarrow \frac{5s^3 + 3s}{6s^4 + 4s^2 + 2}$$

$$\frac{\frac{2s^2 + 2}{5}}{\frac{6s^4 + 4s^2 + 2}{5}} = \frac{2s^2 + 2}{6s^4 + 4s^2 + 2} \xrightarrow{\frac{2s}{2s}} \frac{2s^3 + 2s}{5s^4 + 2s^2 + 1} \xrightarrow{\frac{2s}{2s}} \frac{2s^4 + 2s^2}{5s^4 + 2s^2 + 1} \xrightarrow{\frac{2s}{2s}} \frac{2s^5 + 2s^3}{5s^4 + 2s^2 + 1} \xrightarrow{\frac{2s}{2s}} \frac{2s^6 + 2s^4}{5s^4 + 2s^2 + 1} \xrightarrow{\frac{2s}{2s}} \frac{2s^7 + 2s^5}{5s^4 + 2s^2 + 1}$$

as negative (capacitor) or $P(s)$ not of unity



unstable = $i' \rightarrow \infty$ when we initial condition