

Sensitivity

$$S_x^{T(a), y^1} = \frac{y^1}{T} \frac{\partial T}{\partial x}$$



if $T(j\omega) = |T(j\omega)| e^{j\phi}$

$$\text{then } S_x^{T(j\omega)} = \frac{x}{|T(j\omega)|} \cdot \frac{d|T(j\omega)|}{dx} e^{j\phi}$$

$$= \frac{x}{|T(j\omega)|} \left[\frac{d|T(j\omega)|}{dx} e^{j\phi} + |T(j\omega)| \frac{d\phi}{dx} e^{j\phi} \right]$$

$$= \frac{x}{|T(j\omega)|} \cdot \frac{d|T(j\omega)|}{dx} + \frac{x}{e^{j\phi}} \cdot e^{j\phi} \left(\frac{d\phi}{dx} \right)$$

$$= \sum_y \frac{|T(j\omega)|}{x} + j \frac{x}{e^{j\phi}} \frac{d\phi}{dx}$$

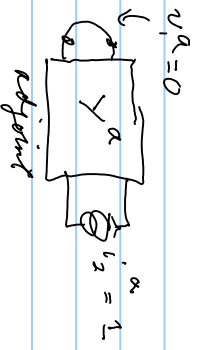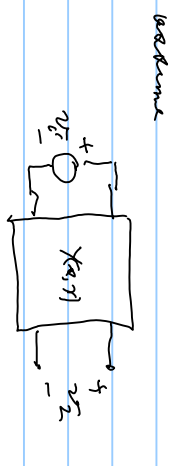

device S_x

assume both have the same graph $v^T i \Rightarrow v_b^T \cdot i_b - v_b^a \cdot i_b$

original \rightarrow adjoint

$$v_b = \begin{bmatrix} v_1 \\ v_2 \\ v_{b-2} \end{bmatrix} \quad i = \begin{bmatrix} i_1 \\ i_2 \\ i_{b-2} \end{bmatrix}$$

, also for adjoints (put a super a on these 2)

inside the 2-part

$$v_b^T i_b = \begin{bmatrix} v_1^T & v_2^T & v_{b-2}^T \end{bmatrix} \begin{bmatrix} i_1^a \\ i_2^a \\ i_{b-2}^a \end{bmatrix} - \begin{bmatrix} v_1^T & v_2^T & v_{b-2}^T \end{bmatrix} \begin{bmatrix} i_1^a \\ i_2^a \\ i_{b-2}^a \end{bmatrix} = v_1^T i_1^a - v_1^T i_1^a + v_2^T i_2^a - v_2^T i_2^a + v_{b-2}^T i_{b-2}^a - v_{b-2}^T i_{b-2}^a$$

$$v_1^T i_1^a - v_1^T i_1^a + v_2^T i_2^a - v_2^T i_2^a + v_{b-2}^T i_{b-2}^a - v_{b-2}^T i_{b-2}^a = 0$$

Therefore


fix x in adjoint circuit so the adjoint circuit has not change when x change
 fix $v_1(x) \Rightarrow$ now take derivatives of all these terms

$$\frac{d(v_1^T i_1^a)}{dx} - \frac{d(v_1^T i_1^a)}{dx} + \frac{d(v_2^T i_2^a)}{dx} + \frac{d(v_{b-2}^T i_{b-2}^a)}{dx} = 0$$

force = 0
 by $y^a = y^T$

choose $v_1 = 1$ then $v_2 = T(A, y) \Rightarrow i_2^a \cdot \frac{d(T(A, y))}{dx} = -v_{b-2}^T \left(-\frac{dy^T}{dx}\right) \cdot v_{b-2}^a$

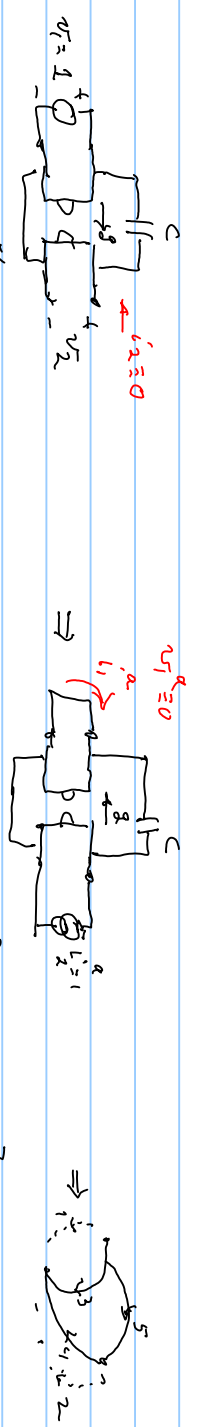choose $i_2 = 1 \Rightarrow \frac{d T_{(4,1)}(v)}{dx} = \frac{dv_2}{dx} = + v_1^T \begin{bmatrix} g & Y_{b,2} \\ -g & -b-2 \end{bmatrix} v_2^T$




define $S_c^{whs} \Rightarrow Y = \begin{bmatrix} ac & -ac+g \\ -ac-g & ac \end{bmatrix} \Rightarrow Y^T = \begin{bmatrix} ac & -ac-g \\ -ac-g & ac \end{bmatrix}$

$\frac{d Y^T}{dc} = \begin{bmatrix} a & -a \\ -a & a \end{bmatrix}$ but need the branch Y not the 2-part Y

$\begin{bmatrix} i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 0 & g & 0 \\ -g & 0 & 0 \\ 0 & 0 & ac \end{bmatrix} \begin{bmatrix} v_3 \\ v_4 \\ v_5 \end{bmatrix}, Y = \begin{bmatrix} 0 & g & 0 \\ -g & 0 & 0 \\ 0 & 0 & ac \end{bmatrix} \Rightarrow Y_{b,2} = \begin{bmatrix} 0 & -g & 0 \\ g & 0 & 0 \\ 0 & 0 & ac \end{bmatrix} \Rightarrow \frac{d Y_{b,2}}{dc} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & a \end{bmatrix}$

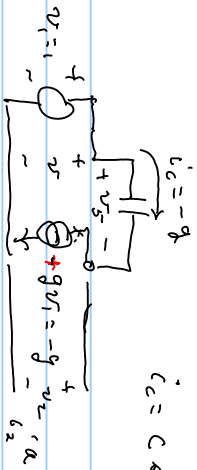$\frac{d v_2}{dc} = \begin{bmatrix} v_3 & v_4 & v_5 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & a \end{bmatrix} \begin{bmatrix} v_3^a \\ v_4^a \\ v_5^a \end{bmatrix} = \begin{bmatrix} 0 & 0 & a v_5^a \\ v_3^a \\ v_4^a \\ v_5^a \end{bmatrix} = a v_5^a \cdot v_5^a$



$$i_c = C \cdot \dot{v}_2 \Rightarrow v_2 = \frac{1}{C} \cdot (fg)$$

$$v_2 = 1 - v_3 = 1 + \frac{g}{C} = \frac{C+g}{C}$$



$$v_2^a = -\frac{1}{C} \cdot 1$$

$$\Rightarrow \frac{dv_2}{dc} = \frac{d}{dc} \frac{1}{C} = \frac{d}{dc} \frac{1}{C+g} = -\frac{1}{C^2} (fg) \left(\frac{-1}{C} \right) = -g/C^2$$

$$R_{T1} = \frac{C \cdot dV/dC}{C} = \frac{g}{C+g} = \frac{g}{C+g}$$

or a check: $\frac{dV_2}{dc} = \frac{d}{dc} \left(1 + \frac{g}{C} \right) = -\frac{g}{C^2} \cdot C = S_x^T$

anmerkungen