


Mohler's $S(z)$ synthesis, S is 1x1 & rational with real coefficients

$$S(z) = \frac{N(z)/D(z)}{D(z)/D(z)} = \frac{S_1(z)}{S_2(z)}, \quad S_1 \text{ & } S_2 \text{ bounded real, BR}$$


choose $d_1(z)$ Hurwitz (no zeroes in $\sigma \geq 0$), $S[D_1]$ & max of $S[D_1]$ or $S[D_1]$

Then to synthesize $S(z)$, synthesizing S_1 & S_2



to create S_2 :

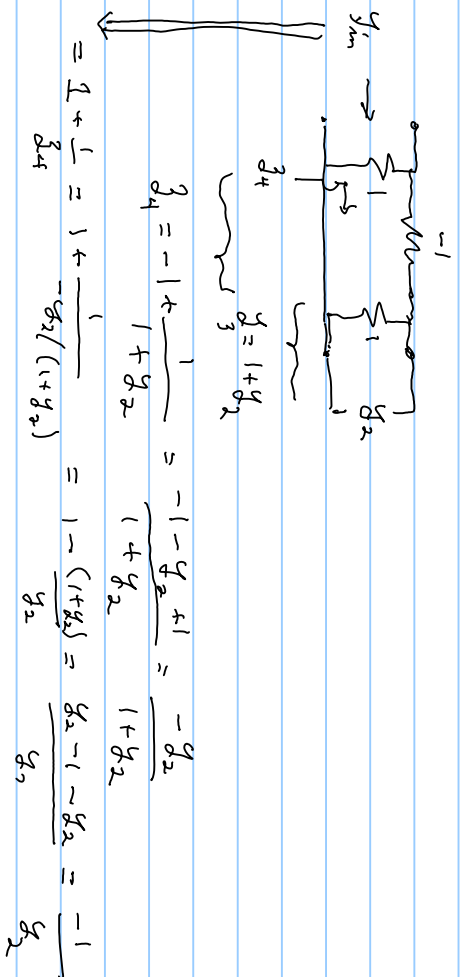

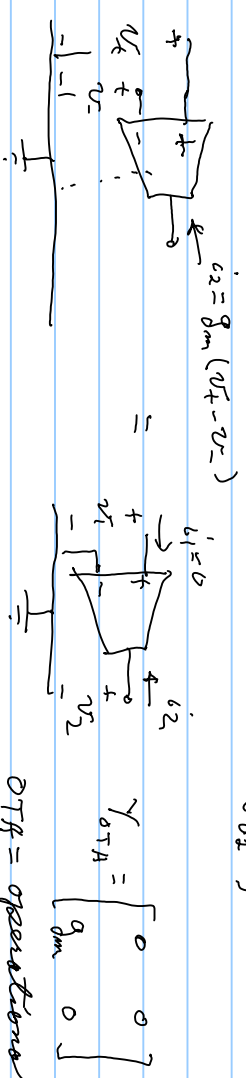
$$S = (1 + Y) (1 - Y)^{-1} \quad S_{in} = (1 + (-1/y_2)) (1 - (-1/y_2)) = \frac{(y_2 + 1)}{(y_2 - 1)} = - \left(\frac{1 + y_2}{1 - y_2} \right) = - \frac{1}{S_2}$$



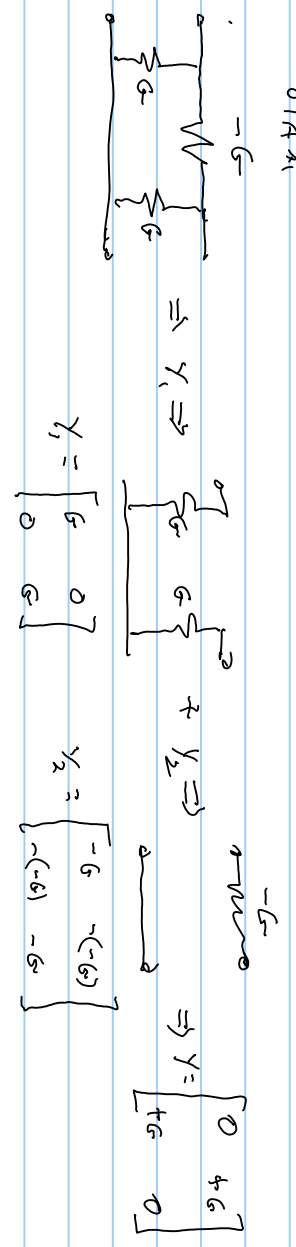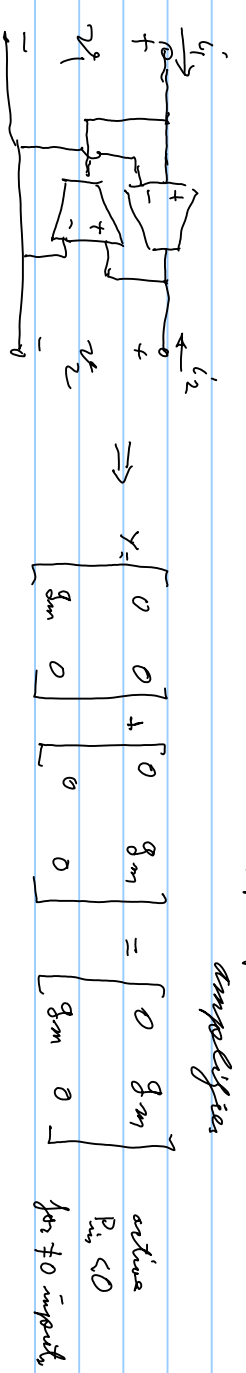OTA = operational transconductance amplifier



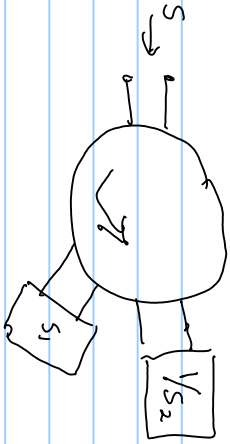

$$S = \frac{1}{s_2} \cdot S_1 \quad \text{gives a net BR } S$$

\Rightarrow get the zeros for S_1, S_2
 & use Root-Locus analysis

Example

$$S = a \quad \text{is not BR} \quad 1 - (j\omega)^2(j\omega) = 1 - \omega^2 \Rightarrow |1 - \omega^2| \rightarrow \infty \text{ as } \omega \rightarrow \infty$$

$$= a/d_1 \quad d_1 = \text{Denominator}, \quad S[n] = \delta[S^a] = 1, \quad \delta[S^i] = 0$$

choose $d_1 = a + 1$

$$\Rightarrow S_1 = \frac{(1 - \delta_1)}{(1 + \delta_1)} \Rightarrow \delta_1 = \frac{(1 - S_1)}{(1 + S_1)} = \frac{1 - \frac{a}{a+1}}{1 + \frac{a}{a+1}} = \frac{a+1-a}{a+1+a}$$

$$= \frac{1}{2a+1} \Rightarrow \delta_1 = \frac{1}{2a+1} \Rightarrow \begin{cases} \delta_{L=2} \\ \delta_{R=1} \end{cases}$$

$$\delta_2 S_2 + S_2 = \delta_2 - 1 \quad S_2 = \frac{\delta_2 - 1}{\delta_2 + 1}$$

$$\delta_2(S_2 - 1) = -S_2 - 1$$

$$\delta_2 = \frac{S_2 + 1}{1 - S_2} = \frac{\left(\frac{1}{a+1}\right) + 1}{1 - \left(\frac{1}{a+1}\right)} = \frac{1 + a + 1}{a + 1 - 1} = \frac{2a + 2}{a} = 2 + \frac{2}{a}$$

$$\begin{cases} \delta_{R=2} \\ \delta_{C=1} \end{cases}$$



other matrices

$$S = \begin{bmatrix} m_{11}/d_1 & m_{12}/d_1 \\ m_{21}/d_1 & m_{22}/d_1 \end{bmatrix} = \begin{bmatrix} d_1/d_1 & 0 \\ 0 & d_1/d_1 \end{bmatrix}^{-1} \begin{bmatrix} m_{11}/d_1 & m_{12}/d_1 \\ m_{21}/d_1 & m_{22}/d_1 \end{bmatrix}$$

\Rightarrow product of S_2^{-1} & S_1


both S_1 & S_2 are BR

area 2 negative
rotation in 4×4 DTFA's
to get S_2^{-1} given S_2

i.e. by Wolberg's scheme can synthesize "almost" any active circuit

M. Ronald

approximation: done pass

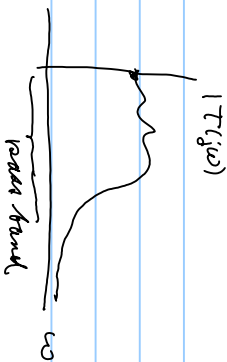

Maximally flat low pass filter $T(s) = \frac{1}{s^n + \alpha_{n-1}s^{n-1} + \dots + \alpha_1 s + \alpha_0}$ can choose $\alpha_0 = 1$ also

$$\frac{d}{ds} \left. \frac{|T(j\omega)|}{\omega^m} \right|_{\omega=0} = 0 \quad \text{for as many integers } m > 0 \text{ as possible}$$

$$T(-s)T(s) = |T(j\omega)|^2; \quad \frac{d}{ds} |T(j\omega)|^2 = 2 |T(j\omega)| \frac{d}{ds} |T(j\omega)|$$

$s = j\omega$ \downarrow $\omega = 0$

$\text{for } \omega = 0$

$$\therefore \text{to force } \frac{d}{ds} |T(j\omega)| = 0 \text{ can force } |T(j\omega)|^2 \Rightarrow 0$$

$$\frac{d}{ds} \frac{1}{|T(j\omega)|} = - \frac{d}{ds} |T(j\omega)| \times \frac{1}{|T(j\omega)|^2} \Rightarrow 0 \text{ implies } \frac{d}{ds} |T(j\omega)| \Rightarrow 0$$

$\neq 0 @ \omega = 0$

$$\therefore \text{can force } \frac{d}{ds} |T(j\omega)|^2 = 0 @ \omega = 0$$

$$\text{But } \frac{1}{T(s)} = s^n + \alpha_{n-1}s^{n-1} + \dots + \alpha_1 s + \alpha_0 \Rightarrow \frac{1}{T^*(j\omega)T(j\omega)} = \frac{1}{T(-j\omega)T(j\omega)}$$

$$\frac{1}{T(j\omega)T(-j\omega)} = (j\omega)^n + \dots + 1) (-j\omega)^n + \dots + 1) = (j^n (-j)^n (\omega^{2n}) + \dots + 1) = \omega^{2n} + b_1 \omega^{2n-2} + \dots + 1$$

$$= f(\omega^2)$$

$$\frac{d}{d\omega} \frac{1}{T(j\omega)T(-j\omega)} = 2n(\omega^{2n-1}) + b_1(2\omega^{2n-3}) + \dots + 2b_1 \omega^{2n-1}$$

Keep differentiating & set to 0 \Rightarrow all these coefficients $b_1, \dots = 0$

$$i: \frac{1}{T(-j\omega)T(j\omega)} = \omega^{2n} + 1 \Rightarrow \frac{1}{T(-s)T(s)} \quad \text{root } s = \omega/j \Rightarrow \text{root } \omega = j s$$

$$\frac{1}{T(-s)T(s)} = (j s)^{2n} + 1 = (-1)^n s^{2n} + 1$$

device to factor $(-1)^n s^{2n} + 1$ into 2 functions

polynomials \times functions

conjugate polynomials

$$s^{2n} + 1 = (-1)^n s^{2n} + 1 \text{ gives the zeros of } \frac{1}{T(-s)T(s)}$$

$$= \frac{1}{T_x T_x}$$

