

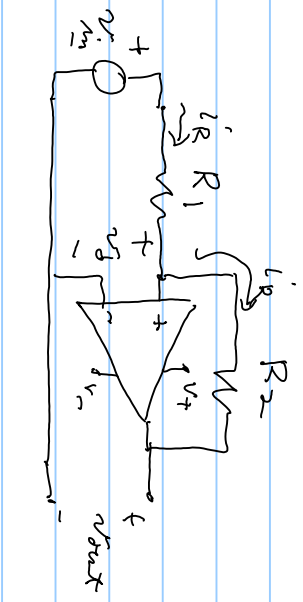
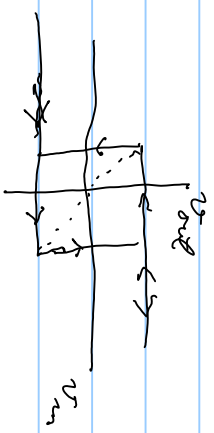


Binary hypothesis




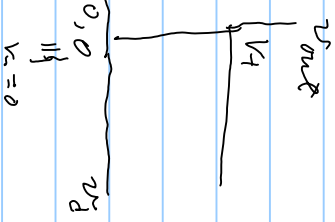


$$v_{out} = V_T \downarrow (v_{in})$$

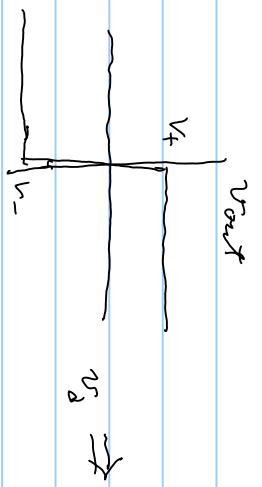



i_{in} of op-amp = 0, $i_R = G_1 (v_{in} - v_d) = G_2 (v_d - v_{out}) \Rightarrow G_1 v_{in} \sim (G_1 + G_2) v_d = -G_2 v_{out}$
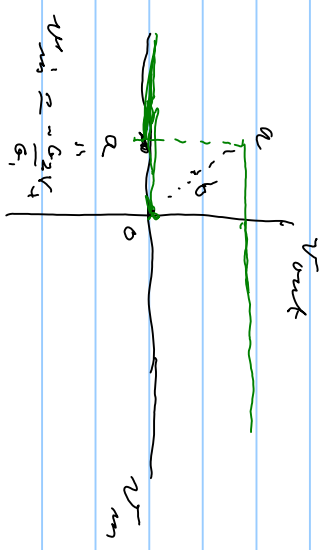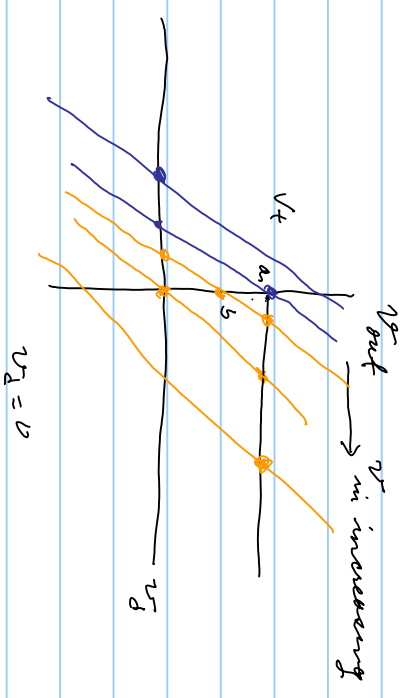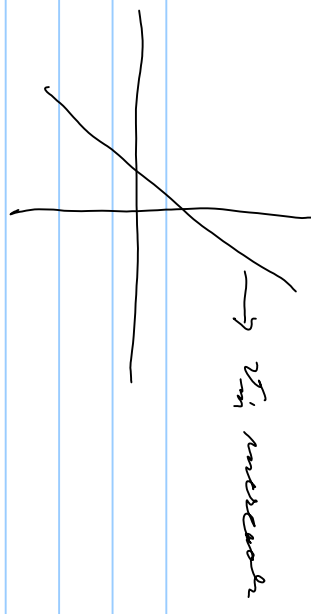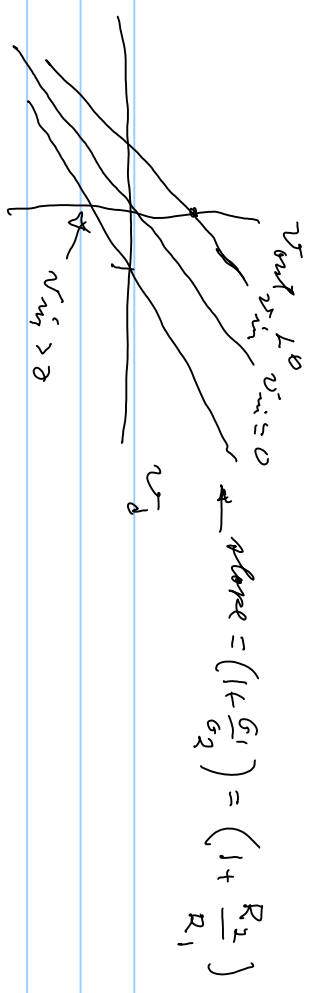
$$v_{out} = \frac{1}{G_2} \left[(G_1 + G_2) v_d - G_1 v_{in} \right] = \left(\frac{G_1 + 1}{G_2} \right) v_d - \frac{G_1}{G_2} v_{in}$$



jump point a: $v_{out} = v_{in} - \frac{G_1}{G_2} v_{in} \Rightarrow v_{in} = \frac{G_2}{G_1} v_{out}$
 $v_{out} = \left(1 + \frac{G_1}{G_2}\right) v_{in} - \frac{G_1}{G_2} v_{in}$
 $v_{out} = v_{in} \left(1 + \frac{G_1}{G_2} - \frac{G_1}{G_2}\right)$

$df_V \neq 0$

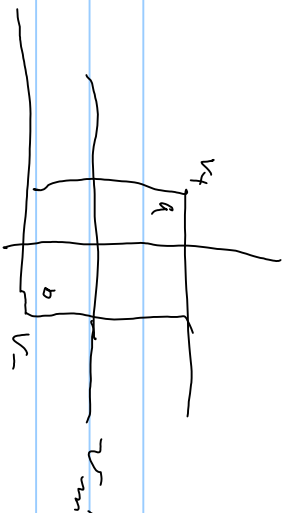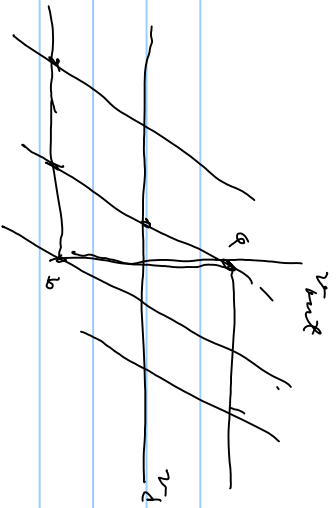


How to use for chaos

Bottom plane




Top plane

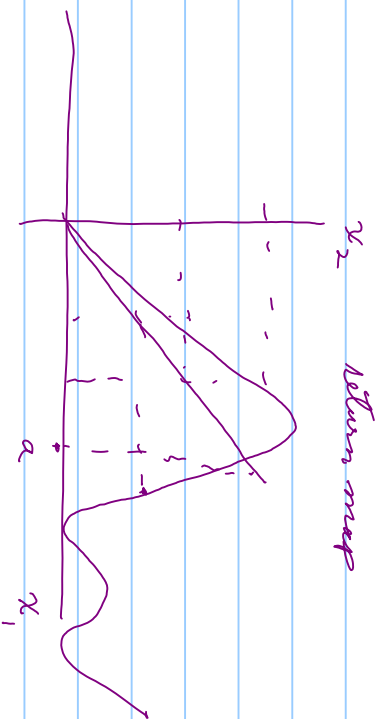

if get a period 3 return map then get
"chaos" as defined by Dev. symbols

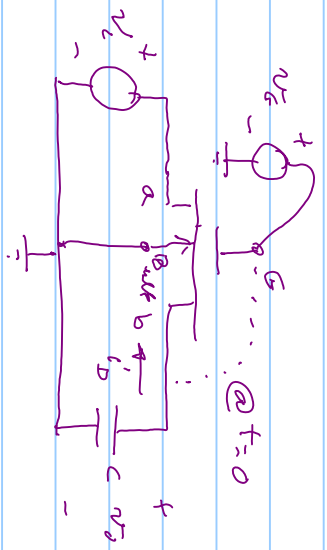
$\Rightarrow \lim_{t \rightarrow \infty} v_{out} \neq \lim_{t \rightarrow \infty} v_{in}$
 if not initial conditions in period 3
 position of return map
 can make the unstable oscillator with the same capacitors.



assume $v_G = V_{DD} > 0$
 @ $t = 0$ let $v_G = V_{DD}$, $v_C(t) = 0$, $t > 0$

$b = \text{obtain } @ t = 0, a = \text{assume}$
 $= 1) \quad = S$
 $v_G = V_{DD}, v_{GS} = V_{DD}, v_{GS} - V_{th} < v_{DS}(t) = v_G(t)$

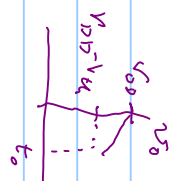$i_D = k(v_{GS} - V_{th})^2 \Rightarrow k(v_{DD} - V_{th})^2$
 $-C \frac{dv_G}{dt} = k(v_{DD} - V_{th})^2$
 $v_G = -\frac{1}{C} \int_0^t k(v_{DD} - V_{th})^2 dt + V_{DD}$
 $= -\frac{1}{C} k(v_{DD} - V_{th})^2 t + V_{DD}$



\Downarrow
 Remain T_{on} is
 saturation

$V_{OS}(t)$

||

for $t > t_0$ then $v_{OS}(t) < V_{BD} - V_{th} = v_{OS} \Rightarrow$ transistor is off, t_{trk}

$$i_D = k(2(v_{OS} - V_{th})v_{DS} - v_{DS}^2) \approx -C \frac{dv_{OS}}{dt} = k(2(V_{BD} - V_{th})v_{OS} - v_{OS}^2)$$

$$\frac{dv_{OS}}{2(V_{BD} - V_{th})v_{OS} - v_{OS}^2} = -\frac{dt}{C/k} \Rightarrow \int_{v_{OS}(t_0)}^{v_{OS}(t)} \frac{dv_{OS}}{v_{OS}(d - v_{OS})} = \int_{t_0}^t \frac{-dt}{C} = -\frac{k}{C}(t - t_0), \quad d = 2(V_{BD} - V_{th})$$

$$\frac{1}{v_{OS}(d - v_{OS})} = \frac{-1}{v_{OS}(v_{OS} - d)} = \frac{1/d}{v_{OS}} + \frac{-1/d}{v_{OS} - d} = \frac{(1/d)(v_{OS} - d)}{v_{OS}(v_{OS} - d)} + \frac{(-1/d)v_{OS}}{v_{OS}(v_{OS} - d)} = \frac{-1}{v_{OS}(v_{OS} - d)}$$

$$\int_{v_{OS}(t_0)}^{v_{OS}(t)} \left[\frac{(1/d)dv_{OS}}{v_{OS}} + \frac{(-1/d)dv_{OS}}{v_{OS} - d} \right] = \frac{1}{d} \ln v_{OS} \Big|_{v_{OS}=v_{OS}(t_0)}^{v_{OS}(t)} + \left[\frac{-1}{d} \right] \ln(v_{OS} - d) \Big|_{v_{OS}(t_0) - d}^{v_{OS}(t) - d} = -\frac{k}{C}(t - t_0)$$

$$-\frac{dk}{C}(t - t_0) = \ln \left(\frac{v_{OS}(t)}{v_{OS}(t_0)} \right) - \ln \left(\frac{v_{OS}(t) - d}{v_{OS}(t_0) - d} \right) = \ln \left(\frac{v_{OS}(t)}{v_{OS}(t_0)} \cdot \frac{v_{OS}(t_0) - d}{v_{OS}(t) - d} \right) \quad t > t_0$$

$$e^{-\frac{dk}{c}(t-t_0)} = \frac{v_0(t)}{v_0(t_0)^{-d}} \cdot \frac{v(t_0)^{-d}}{v(t)}$$

$$\text{② } t = t_0 \Rightarrow e = 1$$

can solve for $v_0(t)$, $t > t_0$ or $t \rightarrow \infty$, $v_0(t) \rightarrow 0$