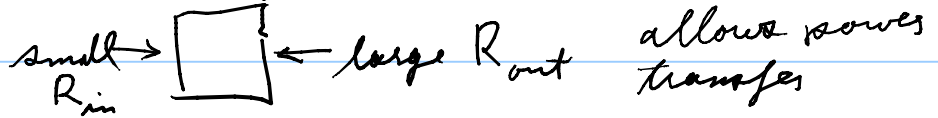


Electronics:

transistors = transfer resistors





symbols


BJT = bipolar junction transistor

MOS = metal oxide silicon

two kinds

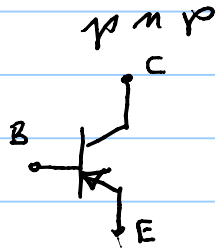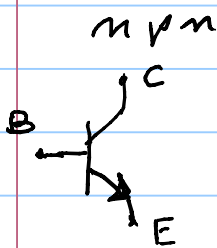


two (of 4) kinds

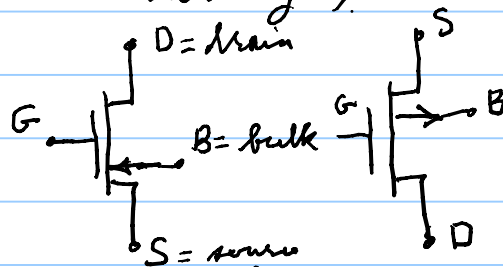


N-channel P-channel

enhancement mode
(other two are "depletion")


an oscillator:

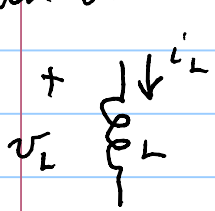
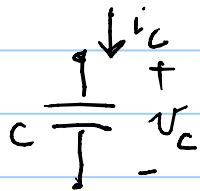
$$v_L = L \frac{di_L}{dt} = L \Delta i_L$$


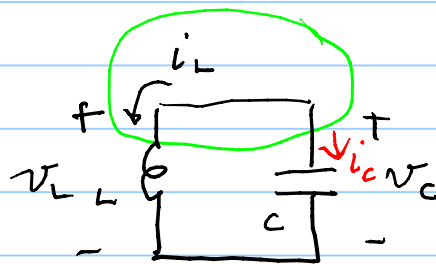
$$i_C = C \frac{dv_C}{dt} = C \Delta v_C$$



KVh: $0 = v_C - v_L \Rightarrow v_L = v_C$

KCL: $0 = i_L + i_C \Rightarrow i_C = -i_L$


1) $L \Delta i_L = v_C$

2) $\rightarrow 1) L \Delta (-C \Delta v_C) = v_C$

2) $C \Delta v_C = -i_L$


3) $L C \Delta^2 v_C + v_C = 0$

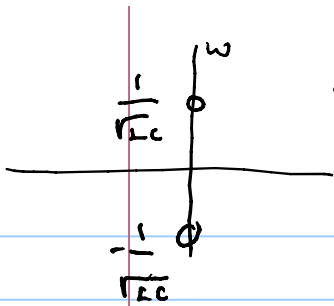3) $\rightarrow (L C \Delta^2 + 1) v_C = 0 \Rightarrow L C \Delta^2 + 1 = 0 \Rightarrow \Delta = \pm j \frac{1}{\sqrt{LC}}$



$$G + j\omega = A$$

But a real circuit has loss:

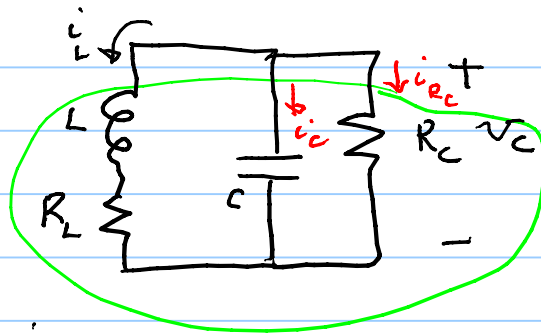

$$G_c = \frac{1}{R_c}$$

$$1) \quad v_c = \omega L i_L + R_L i_L$$

$$\dot{x} = A x$$

$$2) \quad i_L = -\omega C v_c - G_c v_c$$

choose $\begin{bmatrix} v_c \\ i_L \end{bmatrix} = x = \text{state vector}$

$$\begin{bmatrix} \omega C & 0 \\ 0 & \omega L \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix} = \begin{bmatrix} -G_c & -1 \\ 1 & -R_L \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix}$$

$$\Rightarrow \omega \begin{bmatrix} v_c \\ i_L \end{bmatrix} = \begin{bmatrix} -G_c/C & -1/C \\ 1/L & -R_L/L \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix}$$

$$\begin{bmatrix} \omega & 0 \\ 0 & \omega \end{bmatrix} x = \omega \mathbb{1}_2 x = A x \Rightarrow (\omega \mathbb{1}_2 - A) x = 0$$


$\det[\omega \mathbb{1}_2 - A] = 0$ allow a nonzero x

$$\det \begin{bmatrix} \omega + \frac{G_c}{C} & 1/C \\ -1/L & \omega + \frac{R_L}{L} \end{bmatrix} = (\omega + \frac{G_c}{C})(\omega + \frac{R_L}{L}) + \frac{1}{LC} = \omega^2 + (\frac{G_c}{C} + \frac{R_L}{L})\omega + \frac{1}{LC} = 0$$

$+ \frac{G_c R_L}{CL}$

$\text{if } \frac{G_c}{C} = -\frac{R_L}{L} \text{ then can get an oscillator}$

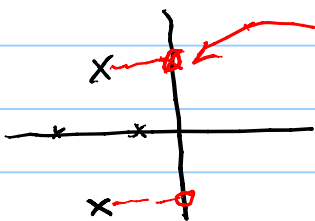$\text{i.e. } R_L = -\frac{L}{C} \cdot G_c$



added
02/01/05

