

$$\frac{G_c}{C} = -\frac{R_L}{L} \quad G_c = -\frac{C}{L} R_L$$



$$R_C = -\frac{L}{C R_L}$$


$$d \begin{bmatrix} v_c \\ i_L \end{bmatrix} = \begin{bmatrix} -G_c/C & -1/C \\ 1/L & -R_L/L \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix} \quad x = \begin{bmatrix} v_c \\ i_L \end{bmatrix}$$

$$\frac{dx}{dt} = Ax \Rightarrow \frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}, \quad x(0) \text{ given}$$

$$i_c = C \frac{dv_c}{dt} = C \frac{dx_1}{dt} = \underbrace{-\frac{G_c}{C} x_1}_{\text{currents}} \underbrace{-\frac{1}{C} x_2}_{x_1 = \text{voltage}} = \underbrace{\frac{C}{L} R_L \frac{1}{C} x_1}_{\text{current into capacitor}} \underbrace{-\frac{1}{C} x_2}_{\text{goes out}}$$

diodes

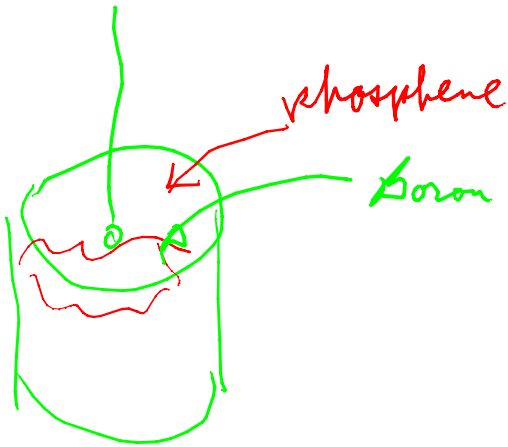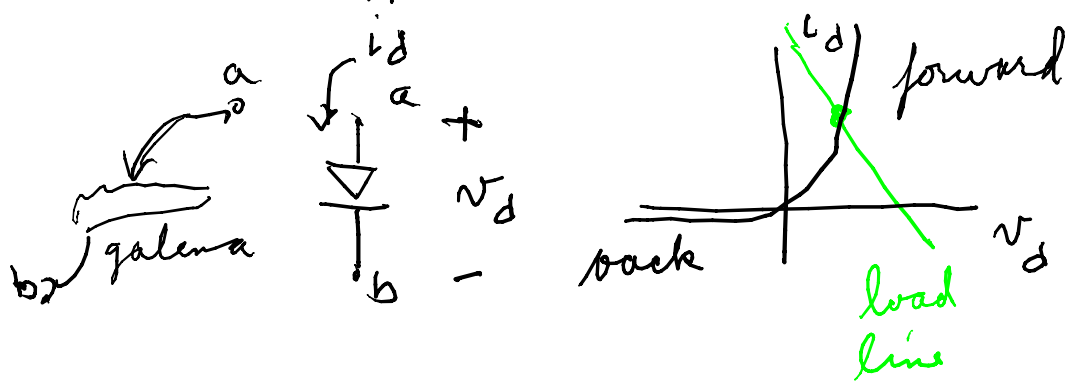


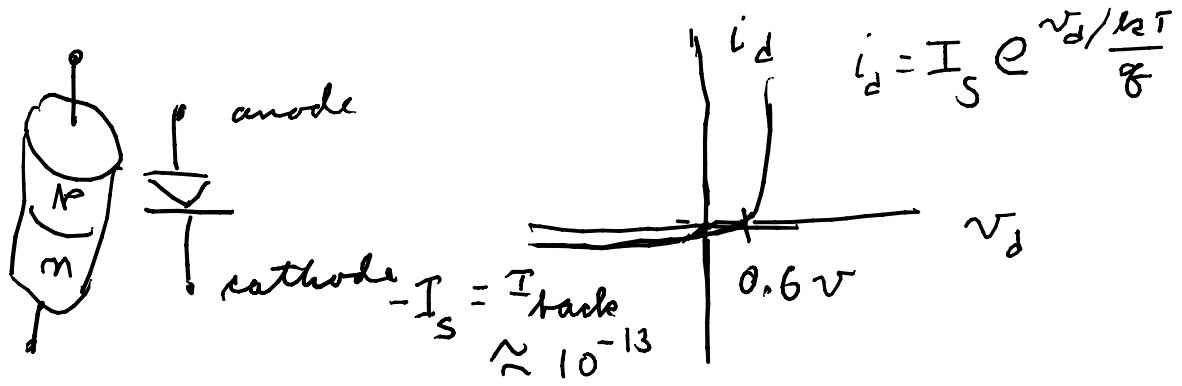


$-I_S =$ saturation current

$V_T =$ thermal voltage $= \frac{kT}{q} \approx 26mV @$ room Temp




$i_d = I_S (e^{v_d/V_T} - 1)$

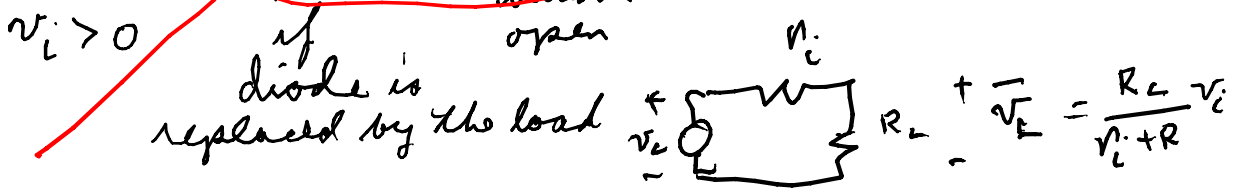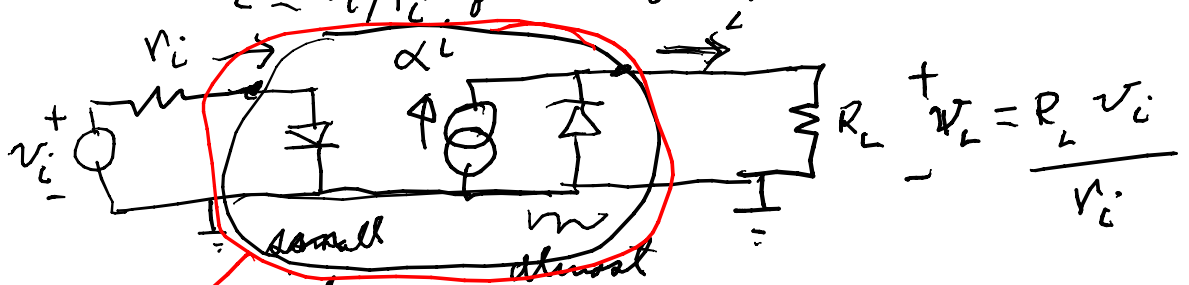transistor = transfer resistor
 $i \approx v_o / r_i$ if diode forward resistance zero



a transistor

$\alpha \approx 1, \alpha < 1$

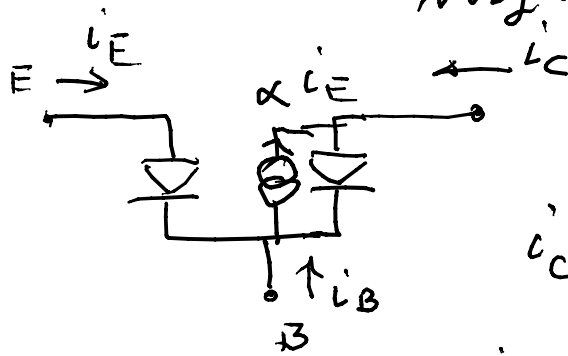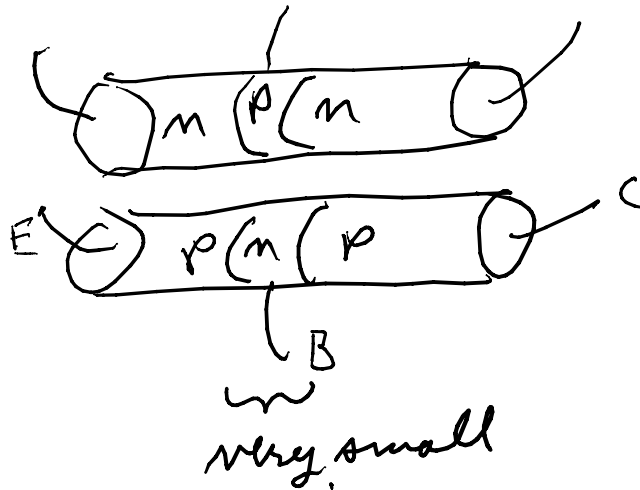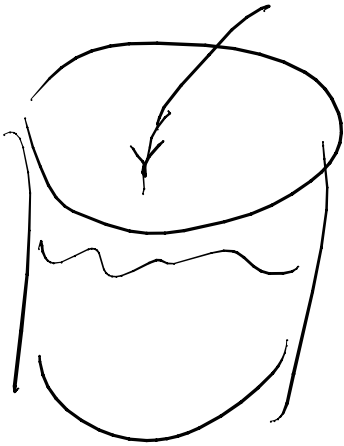

KCL:

$$i_B + i_C + i_E = 0$$

$i_C = \alpha i_E$ if CB diode is
back biased

$$i_B = -i_E - \alpha i_E = -i_C - \frac{1}{\alpha} i_C$$

$$= -\left(\frac{\alpha - 1}{\alpha}\right) i_C$$

$$\therefore i_C = + \frac{\alpha}{1 - \alpha} i_B ; \beta = \frac{\alpha}{1 - \alpha} \text{ large}$$