
 



#2.

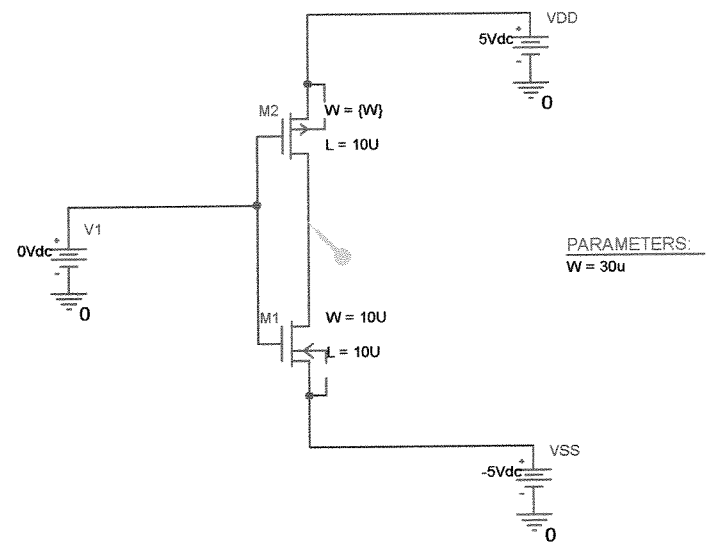(a) Set $V_1=0V$ and the width of the PMOS is a parameter named W . Do a DC sweep with W instead of sweeping any voltage source. Observe the output voltage. The plotted V_o will intersect with the x-axis, which gives us the point where the output voltage is zero. We read the W that makes the $V_o=0$. Here is the W . $W=27.5 \mu m$.



P6

 with $W_p=27.5\mu\text{m}$, I plot V_{out} vs. V_{in} as below





(b):

Now insert $C=50\text{pF}$. To get Fig 4.57, we need to do a transient analysis over time to observe the output voltage with a capacitor load. For a transient analysis, we need a time-varying voltage source as the input voltage to the inverter. One choice is to use a part named VPULSE in the source library. The properties that we have to define for the VPULSE are as follows:


- V1: the first voltage level
- V2: the second voltage level
- TD: delay time before the first pulse
- TR: rise time at the rise edge of the pulse
- TF: fall time at the fall edge of the pulse
- PW: pulse peak width
- PER: the repeat cycle

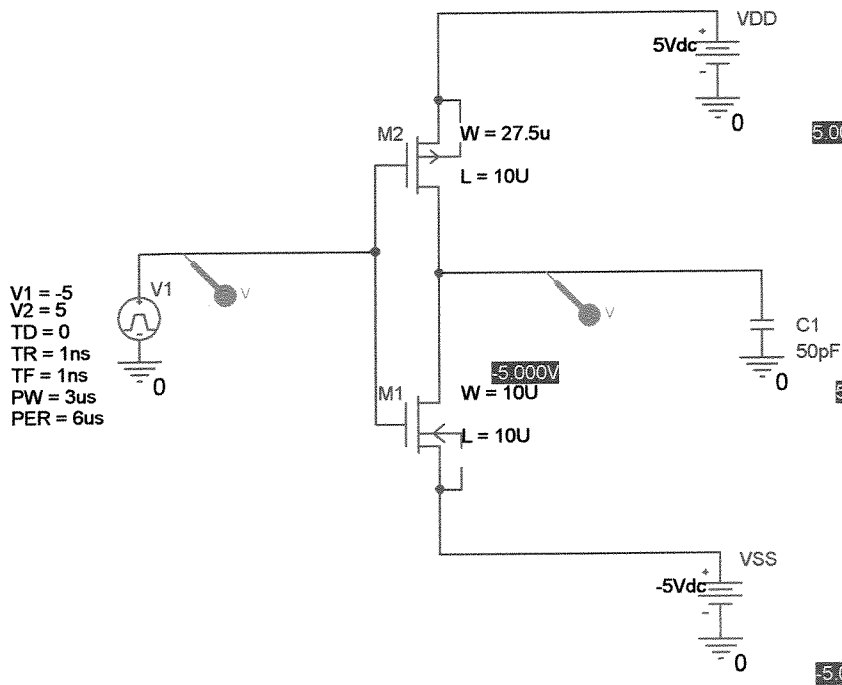
The values I defined are shown in the circuit schematic below. TD and TF are small because I want a nearly perfect square pulse as the input. Note if you set the pulse width too large, you may lose the transient details at the rising and falling edges of the output.



 

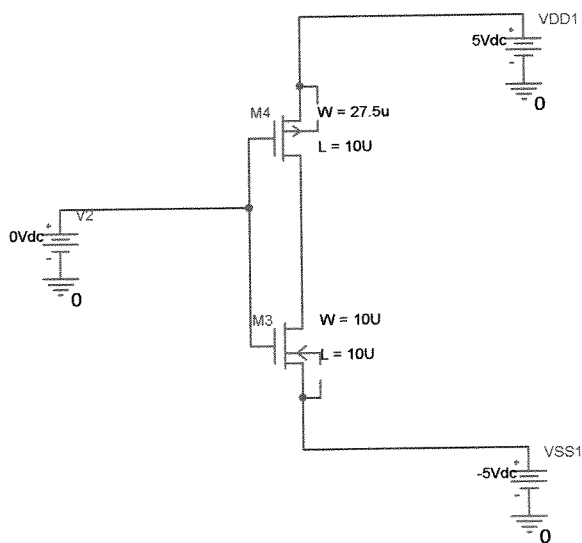(3) To plot Fig. 4. 58, just detach the capacitor since we are doing a DC sweep. Put a DC voltage source at the gates. Sweep this voltage source from VSS to VDD, and plot the drain current of the NMOS.



 

With $\lambda = 0$

#3: $V_t = 1V, L = 1V, \mu_n C_{ox} = 120 \mu A/V^2$
 $V_{GS1} = 1.5V.$

$$120 \mu A = \frac{1}{2} \times 120 \times \frac{W_1}{L} (1.5 - 1)^2$$

$$\Rightarrow W_1 = 8 \mu m$$


$V_{GS2} = 2V,$

$$120 \mu A = \frac{1}{2} \times 120 \times \frac{W_2}{L} (2 - 1)^2 \Rightarrow W_2 = 2 \mu m$$

$V_{GS3} = 1.5V = V_{GS1}$

$$\Rightarrow W_3 = 8 \mu m$$

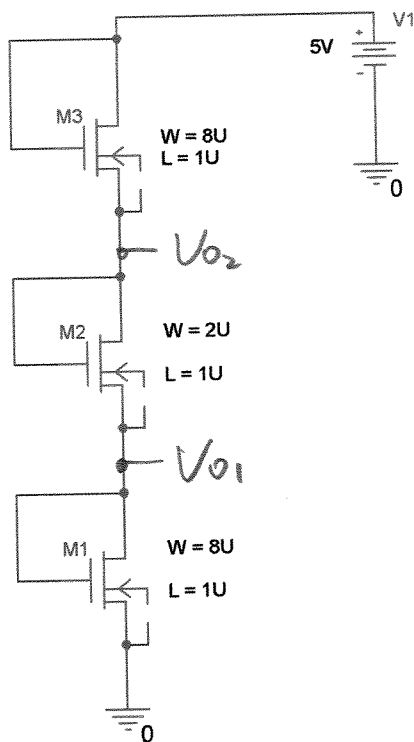
The circuit schematic to simulate is as below:



IF we choose the $L=1\mu\text{m}$ as in the book, and $W_1=8\mu\text{m}$, $W_2=2\mu\text{m}$, and $W_3=8\mu\text{m}$. We got $V_{o1}=1.325\text{V}$, and $V_{o2}=3.675\text{V}$.

Now we simulate the circuit again but with $L=10\mu\text{m}$ (shown in the graph below). To keep W/L the same, we use $W_1=80\mu\text{m}$, $W_2=20\mu\text{m}$, and $W_3=80\mu\text{m}$. We got $V_{o1}=1.325\text{V}$, and $V_{o2}=3.546\text{V}$.

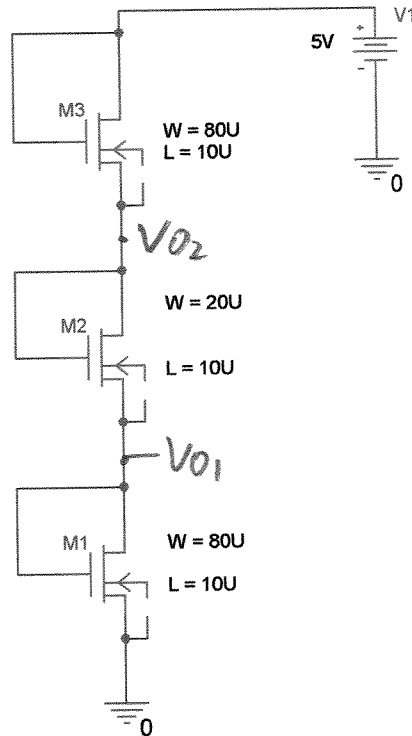The result has discrepancy because in the simulated transistor, we have different k_n' and V_{to} . They are not as given by the problem in the textbook.



If $\lambda \neq 0$, I checked in the library BICMOS12.Lib to find λ for NMOS (MNMOS1S) is 1.84×10^{-2} . So now for M1, $V_{GS1} = 1.5V$, $V_{DS1} = 1.5V$

$$120 \mu A = \frac{1}{2} \times 120 \times \frac{W_1}{L} (1.5 - 1)^2 \times (1 + 1.84 \times 10^{-2} \times 1.5)$$

$$\Rightarrow W_1 = 7.78 \mu m$$

For M2, $V_{GS2} = 2V$, $V_{DS2} = 2V$

$$120 \mu A = \frac{1}{2} \times 120 \times \frac{W_2}{L} (2 - 1)^2 \times (1 + 1.84 \times 10^{-2} \times 2)$$

$$\Rightarrow W_2 = 1.92 \mu m$$

For M3, $V_{GS3} = 1.5V$, $V_{DS3} = 1.5V$

$$120 \mu A = \frac{1}{2} \times 120 \times \frac{W_3}{L} (1.5 - 1)^2 \times (1 + 1.84 \times 10^{-2} \times 1.5)$$

$$\Rightarrow W_3 = 7.78 \mu m$$

For $L = 10 \mu m$, W should be multiplied by 10.