

HW 6 04/19/05 Solutions

ENEE 302 Spring 2005

by Y. Z.

1. a) For PMOS, $|V_{GS}|_P = V_{DD} - V_O$

$$|V_{DS}|_P = V_{DD} - V_O$$

For NMOS, $V_{GSN} = V_O$, $V_{DSN} = V_O$

$$I_{DP} = I_{DN} \Rightarrow$$

$$\frac{1}{2} K_{PP} \frac{W_P}{L_P} (|V_{GS}|_P - |V_{TP}|)^2$$

$$= \frac{1}{2} K_{PN} \frac{W_N}{L_N} (V_{GSN} - V_{TN})^2$$

$$\Rightarrow W_{PO} = \frac{K_{PN}}{K_{PP}} \left[\frac{(|V_{GS}|_P - |V_{TP}|)^2}{(V_{GSN} - V_{TN})^2} \right]^{-1} \cdot W_N \cdot \frac{L_P}{L_N}$$

$$= 5 \cdot \left[\frac{(3 - 1 - 0.5)^2}{(1 - 0.25)^2} \right]^{-1} \cdot 20 \mu \cdot \frac{1}{2}$$

$$= 12.5 \mu$$

b) Now, $\frac{1}{2} K_{PP} \frac{W_{PN}}{L_P} (|V_{GS}|_P - |V_{TP}|)^2 (1 + |\lambda_P| |V_{DS}|_P)$

$$= \frac{1}{2} K_{PN} \frac{W_N}{L_N} (V_{GSN} - V_{TN})^2 (1 + \lambda_n V_{DSN})$$

$$\Rightarrow W_{PN} = W_{PO} \cdot \frac{1 + \lambda_n V_{DSN}}{1 + |\lambda_P| |V_{DS}|_P} = 12.1 \mu$$

(C) Two possibilities for final states:

$$1. \quad V_a = V_b \leq 4.5 \text{ V}$$

$$2. \quad V_a = 4.5 \text{ V}, \quad V_b > 4.5 \text{ V}$$

(For detailed analysis, see solutions for Midterm. Note here $V_{to} = 0.5 \text{ V}$ instead of 1 V .)

Assume possibility 1 happens, then

$$C_{out} \cdot V_b(t=0) = C_{in} \cdot V_x + C_{out} \cdot V_x$$

here V_x is the final value of V_a and V_b ,

$$\begin{aligned} V_x &= \frac{C_{out}}{C_{in} + C_{out}} \cdot V_b(t=0) \\ &= \frac{1 \text{ PF}}{21 \text{ PF}} \cdot 5 \text{ V} \\ &= 0.238 \text{ V} \end{aligned}$$

This result satisfies $V_x \leq 4.5 \text{ V}$,

so this should be the real case that happened. So the final values of V_a and V_b is 0.238 V , and since $V_a = V_b$, you can call either drain or source.

$$\begin{aligned}
 3. \quad a) \quad I_R &= I_{C1} + I_{B1} + I_{B3} \\
 &= I_{C1} + 2I_{B1} \quad (I_{B1} = I_{B3}) \\
 &= \left(1 + \frac{2}{\beta}\right) I_{C1} \quad (I_C = \beta I_B) \\
 &= \left(1 + \frac{2}{\beta}\right) \frac{\beta}{\beta+1} I_{E1} \quad (I_C = \frac{\beta}{\beta+1} I_E)
 \end{aligned}$$

to find I_{E1} ,

$$\begin{aligned}
 I_{E1} + I_{E3} &= I_{C2} + I_{B2} + I_{B4} \\
 \Rightarrow 2I_{E1} &= I_{C2} + I_{B2} + I_{B4} \quad (I_{E1} = I_{E3}) \\
 \Rightarrow I_{E1} &= \frac{1}{2} (I_{C2} + I_{B2} + I_{B4}) \\
 &= \frac{1}{2} \left(1 + \frac{2}{\beta}\right) I_{C2} \quad (I_{B2} = I_{B4}) \\
 &= \frac{1}{2} \left(1 + \frac{2}{\beta}\right) I_{out2} \quad (I_C = \beta I_B)
 \end{aligned}$$

$$\Rightarrow I_R = \frac{1}{2} \left(1 + \frac{2}{\beta}\right)^2 \frac{\beta}{\beta+1} I_{out2}$$

$$\text{We know } I_R = \frac{V_{CC} - V_{BE1} - V_{BE2}}{R}$$

$$\Rightarrow I_{out2} = 2 \cdot \frac{\beta+1}{\beta} \frac{1}{\left(1 + \frac{2}{\beta}\right)^2} \cdot \frac{V_{CC} - V_{BE1} - V_{BE2}}{R}$$

$$\text{where } V_{BE1} = V_T \log \frac{I_{E1}}{1 \text{ mA}} + 0.6 \text{ V}$$

$$V_{BE2} = V_T \log \frac{I_{E2}}{1 \text{ mA}} + 0.6 \text{ V.}$$

For detailed labeling of currents, see
~~sent~~ solutions for Midterm.

(b) If $I_{out2} = 0.3 \text{ mA}$

$$\begin{aligned} \text{then, } I_R &= \frac{1}{2} \left(1 + \frac{2}{\beta}\right)^2 \frac{\beta}{\beta+1} I_{out2} \\ &= 0.208 \text{ mA} \end{aligned}$$

$$I_{e1} = \frac{1}{2} \left(1 + \frac{2}{\beta}\right) I_{out2} = 0.187 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_{be1} &= 0.026 \times \log \frac{I_{e1}}{1 \text{ mA}} + 0.6 \text{ V} \\ &= 0.556 \text{ V} \end{aligned}$$

$$I_{e2} = \frac{\beta+1}{\beta} I_{out2} = 0.337 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_{be2} &= 0.026 \times \log \frac{I_{e2}}{1 \text{ mA}} + 0.6 \text{ V} \\ &= 0.571 \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore R &= \frac{V_{cc} - V_{be1} - V_{be2}}{I_R} \\ &= \frac{5 \text{ V} - 0.556 \text{ V} - 0.571 \text{ V}}{0.208 \text{ mA}} \\ &= 18.62 \text{ k}\Omega \end{aligned}$$

$$(c) \quad I_{out} = I_{out1} + I_{out2}$$

$$= \frac{\beta}{\beta+1} I_{e1} + 0.3 \text{ mA}$$

$$= 0.466 \text{ mA}$$