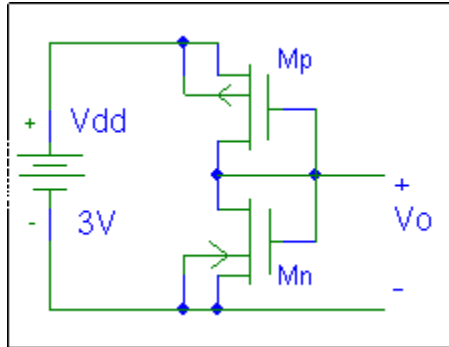


## ENEE 302 Homework 6 due Th April 14, 2005


1. [30 points]



For the above circuit assume  $W_n=L_n=2L_p=20\mu$ ,  $K_{Pn}=5K_{Pp}=5 \times 10^{-4}$ ,  $2V_{TOn}=-V_{TOp}=0.5\text{v}$ ,  $V_{dd}=3\text{v}$ , get  $V_o=V_{dd}/3$ ,

- Assuming  $\lambda_n=|\lambda_p|=0$ , find  $W_p$ , call it  $W_{p0}$ .
- Assuming  $3\lambda_n=|\lambda_p|=0.02/\text{v}$ , find the new  $W_p$ , call it  $W_{p\lambda}$ .
- Compare the results of parts a) and b) and discuss their meaning.


2. [35 points]

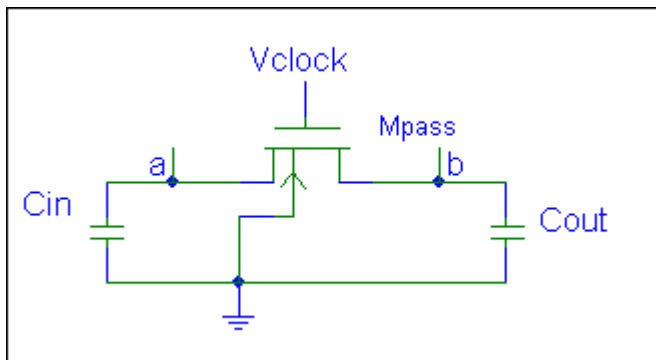

In the above pass transistor circuit  $v_a$  and  $v_b$  are the voltages at nodes a and b with respect to ground. At  $t=0$ , the clock turns from off ( $=0\text{v}$ ) to on ( $=V_{dd}=5\text{v}$ ) and remains stuck at off, while  $v_a(0)=0$  and  $v_b(0)=E=5\text{v}$ . For  $M_{pass}$ ,  $K_P=3 \times 10^{-4}$ ,  $V_{TO}=0.5\text{v}$ ,  $W=2L=60\mu$ ,  $LAMBDA=0.01$ .

- Determine which are the drain and source nodes at  $t=0$ .
- Give the differential equations for  $v_a(t)$  and  $v_b(t)$ .
- When  $C_{in}=20C_{out}=20\text{pF}$  determine the final values for  $v_a(t)$  and  $v_b(t)$ . At the final time which node is the drain and which the source?

3. [35 points]

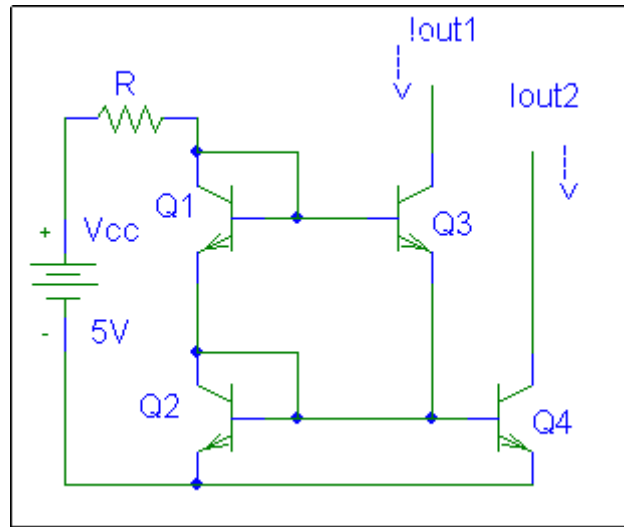

Assume that all transistors are equal with  $\beta=8$ , operate at room temperature (where  $V_T=0.026\text{v}$ ), and that  $V_{BE}=0.6\text{v}$  when  $-I_E=1\text{ma}$ .

- Derive an analytic formula for  $I_{out2}$  in terms of literals ( $\beta$ ,  $V_{cc}$ , and  $R$ ).
- Find  $R$  to give  $I_{out2}=0.3\text{ma}$ .
- For the  $R$  of a) find  $I_{out}=I_{out1}+I_{out2}$ .