
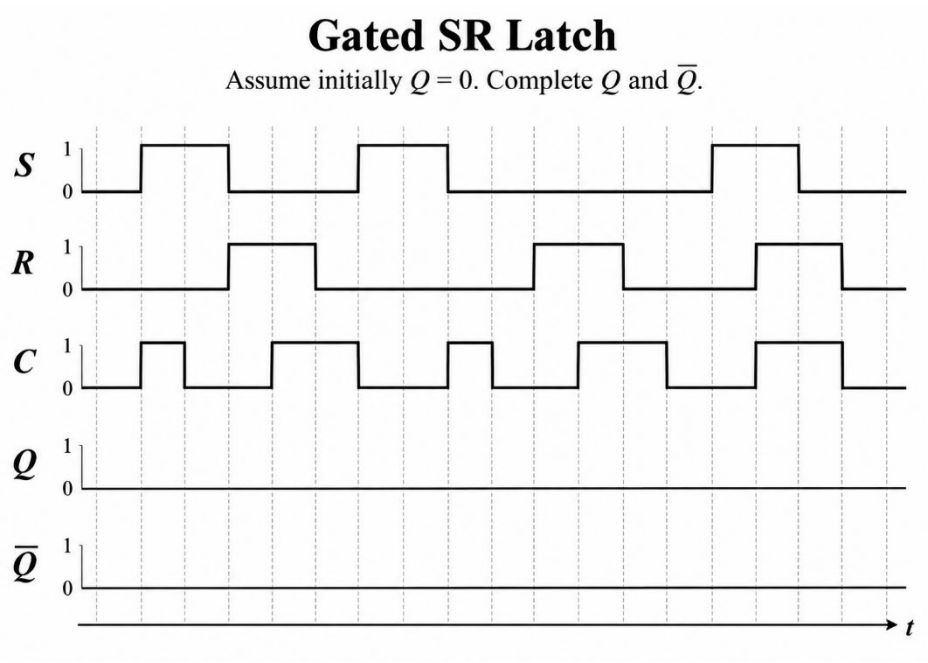
# Homework 5 Supplement

Complete the following timing diagrams:

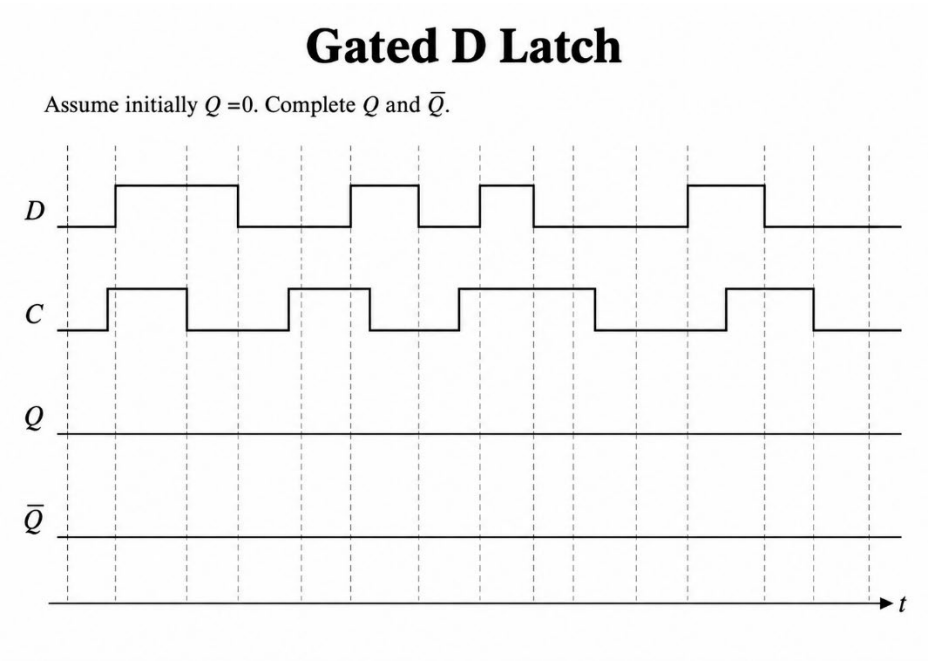


# Homework 5 Supplement
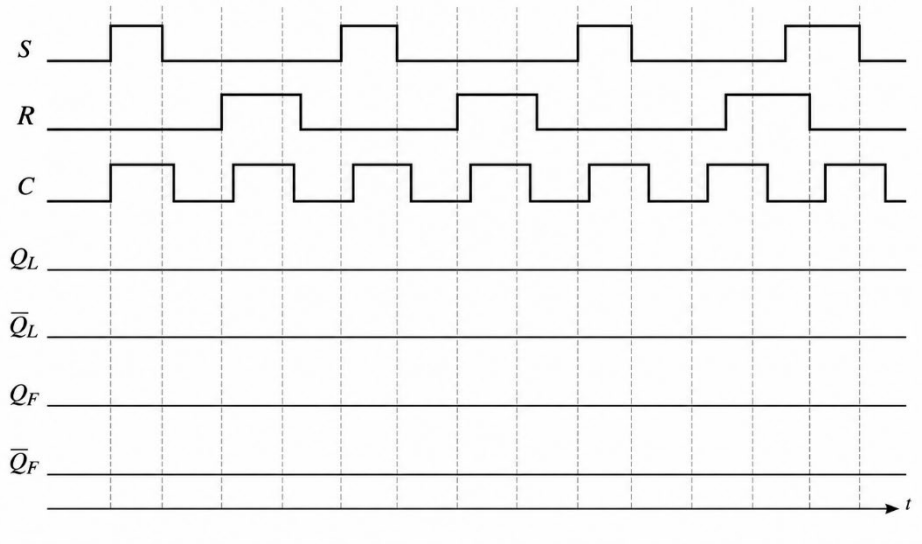
## Leader-Follower SR Flip-Flop

Assume initially $Q_F = 0$. Complete $Q_L$, $\overline{Q}_L$, $Q_F$, and $\overline{Q}_F$.




## Leader-Follower JK Flip-Flop

Assume initially $Q_F = 0$. Complete $Q_L$, $\overline{Q}_L$, $Q_F$, and $\overline{Q}_F$.

