

Digital Logic Design

ENEE 244-020x

Lecture 9

Announcements

- HW3 up on course webpage. Due on Saturday, Oct. 3 @11:59pm on Canvas/ELMS
- Release review problems by Friday 10/2
- Review session in class on Tuesday 10/6
- Exam 1 in class on Thursday 10/8

Agenda


- Last time
 - Using 3,4 variable K-Maps to find minimal expressions (3.2, 3.4)
 - Minimal expressions for incomplete Boolean functions (3.5)
- This time
 - 5 and 6 variable K-Maps
 - Gate Properties (2.8)

Five and Six Variable K-Maps

Five Variable K-Maps

- We can visualize five-variable map in two different ways:

Five Variable K-Maps

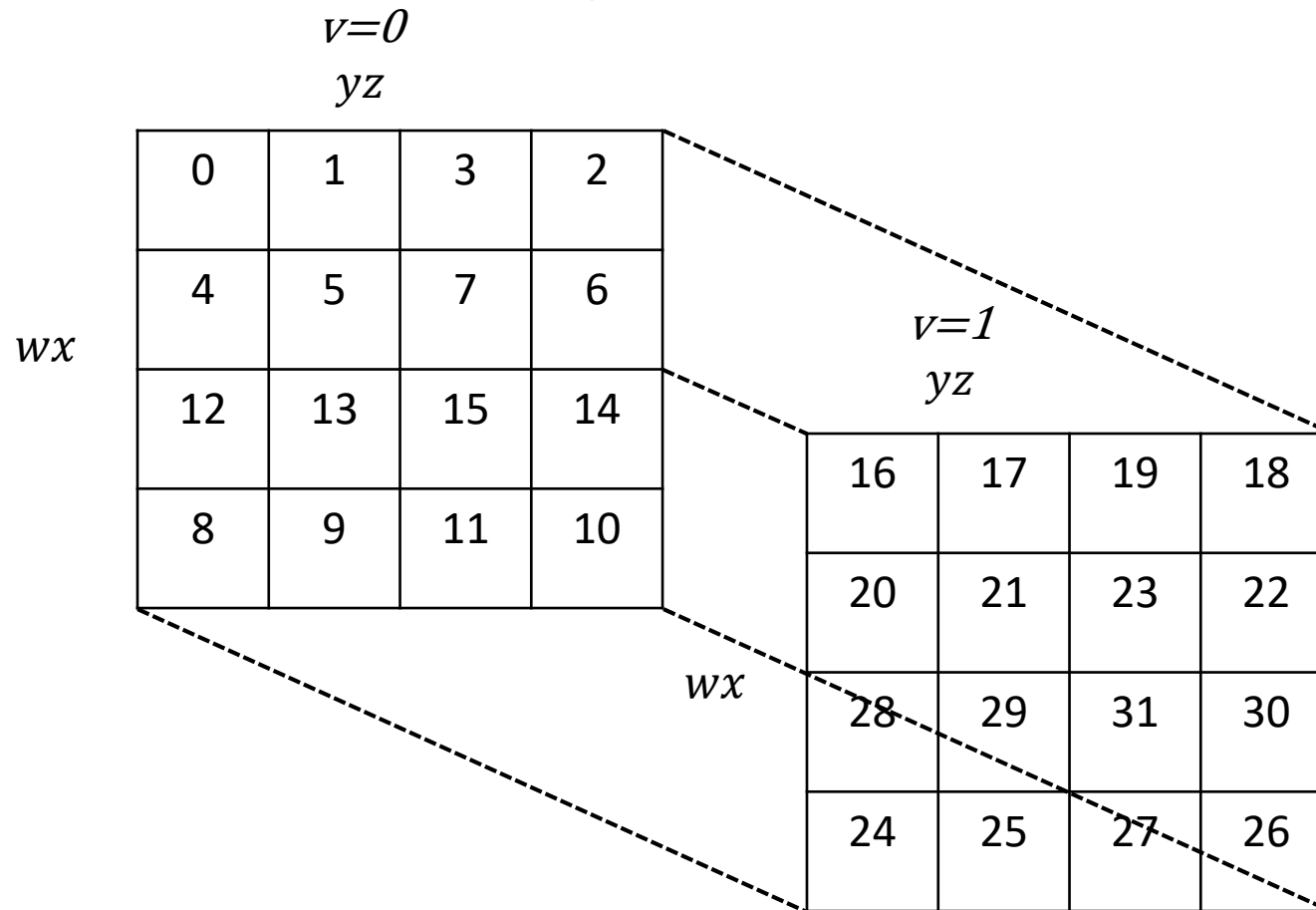

Subcubes: If each layer contains a $2^a \times 2^b$ subcube such that they can be viewed as being directly above and below each other, then the two subcubes collectively form a single subcube consisting of 2^{a+b+1} cells.

Example

$$f(v, w, x, y, z) = \sum m(1, 5, 9, 11, 13, 20, 21, 26, 27, 28, 29, 30, 31)$$

$v=0$
 yz

wx

0	0	1	1	3	0	2	0
4	0	5	1	7	0	6	0
12	0	13	1	15	0	14	0
8	0	9	1	11	1	10	0

wx

$v=1$
 yz

16	0	17	0	18	0	19	0
20	1	21	1	22	0	23	0
28	1	29	1	31	1	30	1
24	0	25	0	27	1	26	1

Example


Step 1: Find all Prime Implicants.

$v=0$
 yz

wx


0	1	0	0
0	1	0	0
0	1	0	0
0	1	1	0

wx

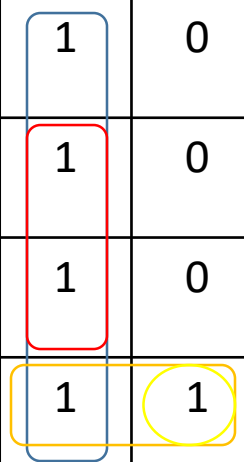

$v=1$
 yz

0	0	0	0
1	1	0	0
1	1	1	1
0	0	1	1

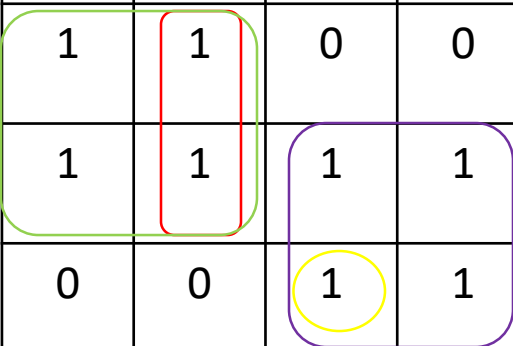

Example

Step 2: Find all Essential Prime Implicants.

$v=0$
 yz

	00	0	1	0	0
wx	01	0	1	0	0
	11	0	1	0	0
	10	0	1	1	0

wx

Essential Prime Implicants:

$$v'y'z$$

$$vxy'$$

$$vwy$$

$v=1$
 yz

	0	0	0	0
	1	1	0	0
	1	1	1	1
	0	0	1	1

wx

Example

Step 2: Find all Essential Prime Implicants.

$v=0$
 yz

	0	1	0	0
	0	1	0	0
	0	1	0	0
wx	0	1	1	0

$v=1$
 yz

	0	0	0	0
	1	1	0	0
	1	1	1	1
	0	0	1	1

Essential Prime Implicants:

$$v'y'z$$

$$vxy'$$

$$vwy$$

Example

Step 2: Find all Essential Prime Implicants.

$v=0$
 yz

	0	1	0	0
	0	1	0	0
	0	1	0	0
wx	0	1	1	0

wx

$v=1$
 yz

0	0	0	0
1	1	0	0
1	1	1	1
0	0	1	1

Final minimal DNF:
 $v'y'z + vxy' + vwy + wx'yz$

Six Variable K-Maps

- We can visualize a six-variable map in two different ways:

Six Variable K-Maps

--	--	--	--	--

Subcubes: If each quadrant has a rectangular grouping of dimensions $2^a \times 2^b$ and each grouping is a mirror image of the other about both the horizontal and vertical mirror-image lines.

Six Variable K-Maps

$uv=00$

yz

	0	1	3	2
wx	4	5	7	6
	12	13	15	14
	8	9	11	10

$uv=01$

yz

	16	17	19	18
wx	20	21	23	22
	28	29	31	30
	24	25	27	26

$uv=11$

yz

	48	49	51	50
wx	52	53	55	54
	60	61	63	62
	56	57	59	58

$uv=10$

yz

	32	33	35	34
wx	36	37	39	38
	44	45	47	46
	40	41	43	42

$w'xyz'$

Subcubes: Subcubes occurring in corresponding positions in consecutive layers collectively form a single subcube.

End of Exam 1 Material/
Beginning of Exam 2 Material

Gate Properties

Gate Properties


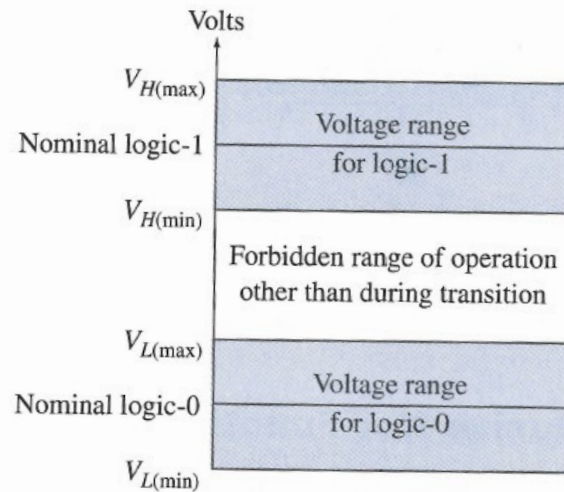


Figure 3.20 Voltage ranges of logic inputs for positive logic.

- The two signal values associated with logic-0 and logic-1 are actually **ranges of values**.
- If signal value is in some low-level voltage range between $V_{L(min)}$ and $V_{L(max)}$ then it is assigned to logic-0. When a signal value is in some high-level voltage range between $V_{H(min)}$ and $V_{H(max)}$ it is assigned to logic-1.


Noise Margins

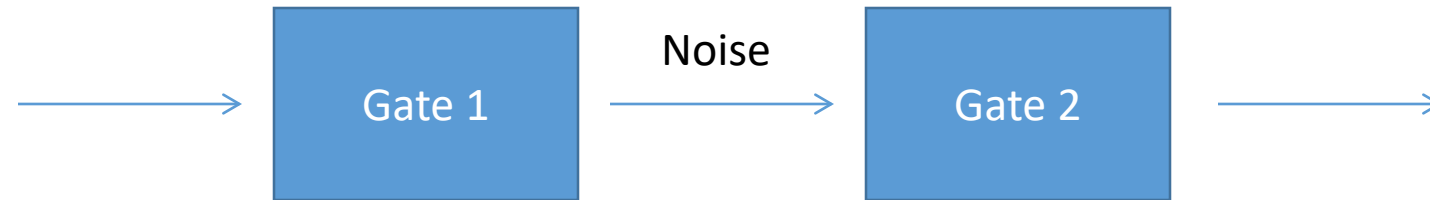- Noise: Random fluctuation in an electrical signal
- Must ensure circuit computes correctly even in the presence of noise.



- The minimal signal value that is acceptable as a logic-1 at the input to a gate is different from the minimal logic-1 signal value that a gate produces at its output.
- Assume output of Gate 1 is exactly at $V_{L(max)}$ and then noise increases the signal further. How will the signal be interpreted?
- Same situation with $V_{H(min)}$.


Noise Margins

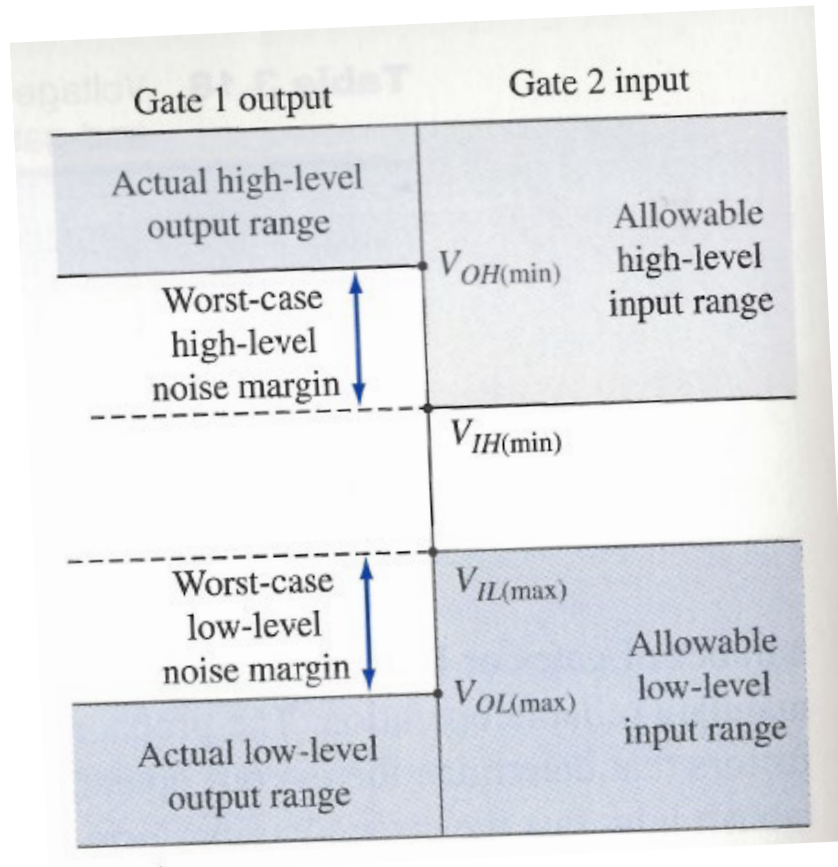

- $V_{L(max)}$ is different for the input/output of a gate!
- Same situation with $V_{H(min)}$.
- Manufacturers normally state a $V_{IL(max)}$, $V_{IH(min)}$, $V_{OL(max)}$, $V_{OH(min)}$ in gate specifications.
- Where $V_{OL(max)} < V_{IL(max)} < V_{IH(min)} < V_{OH(min)}$

Noise Margins

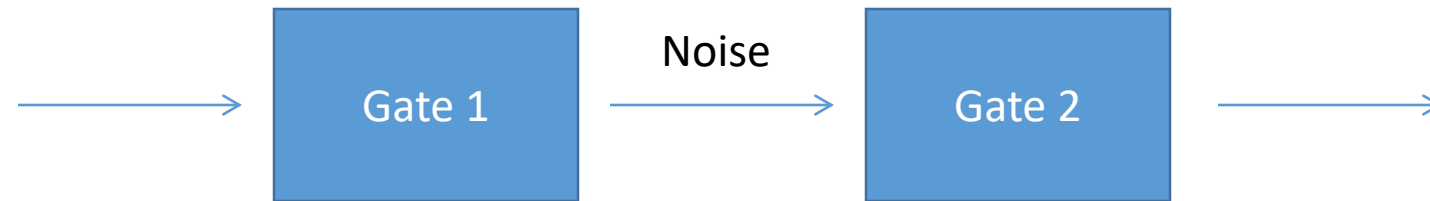- Again consider connecting output of gate to another gate, where noise is induced between the two gates.



- **Worst case low-level noise margin:** Any noise less than $V_{IL(max)} - V_{OL(max)}$ does not affect behavior of Gate 2 on a low-level signal.
- **Worst case high-level noise margin:** Any noise less than $V_{OH(min)} - V_{IH(min)}$ does not affect behavior of Gate 2 on a high-level signal.

Fan-Out

- The signal value at the output of a gate is dependent upon the number of gates to which the output is connected.
- Limitation on number of gates output can connect to. This is known as the **fan-out capability** of the gate. Manufacturers specify this limitation.
- Circuits known as buffers serve as amplifiers for this purpose.




Propagation Delays

- Digital signals do not change instantaneously. Limitation to the overall speed of operation associated with a gate.
- These time delays are called **propagation delays**.
- Time required for output signal to change from high-level to low-level is t_{pHL} .
- Time required for output signal to change from low-level to high-level is t_{pLH} .
- t_{pHL} and t_{pLH} are, in general, not equal. Manufacturers give maximum times in gate specifications.
- General measure used is the average propagation delay time, t_{pd}

$$t_{pd} = \frac{t_{pHL} + t_{pLH}}{2}$$

Propagation Delay Times

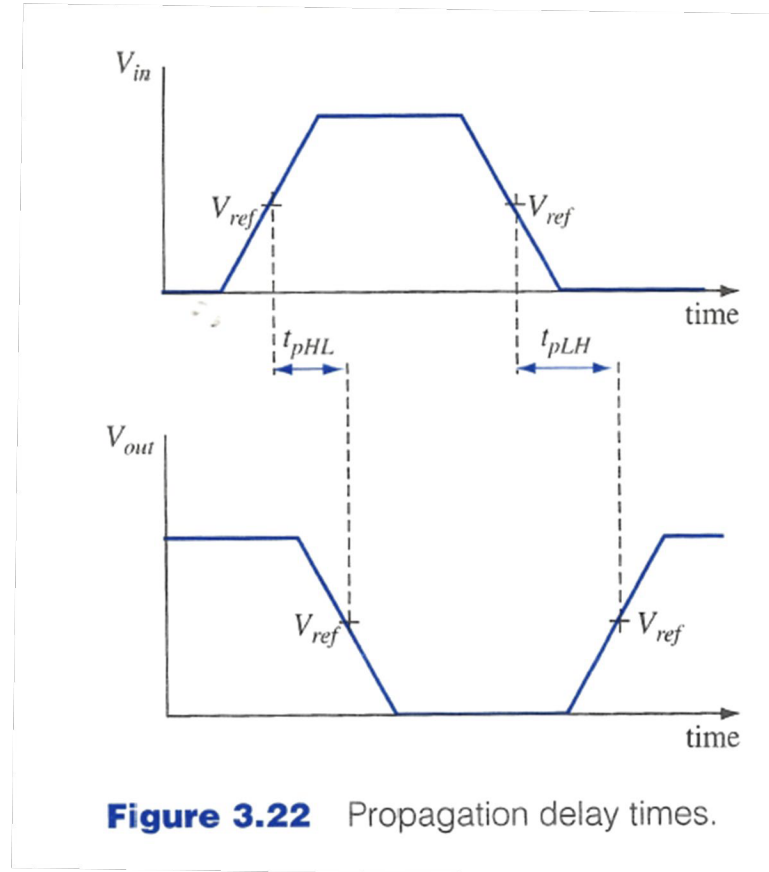

t_{pHL} : Time required for output signal to change from high-level to low-level.

t_{pLH} : Time required for output signal to change from low-level to high-level.

Power Dissipation

- Digital circuit consumes power as a result of the flow of currents. Called **power dissipation**.
- Desirable to have low power dissipation and low propagation delay times.
- These two performance parameters are in conflict with each other.
- Common measure of gate performance is the product of the propagation delay and the power dissipation of the gate.
- This is known as the **delay-power** product.

